

Lecture 2

31 January, 2011

Announcements (1/31/11)

- 401B and 501B:
 - Laboratory Meeting Tues Feb 1, 4⁰⁰-7⁰⁰ pm
- Electricity Test in 2 weeks (Feb 14)
- Today's lecture ... 3⁰⁰-4⁰⁰, 5⁰⁰-6⁰⁰
- 3x5 Cards

Foundations:

Basic Electricity

Basic Neurophysiology

Basic Neuroanatomy

Part I: Basic Electricity

- Prelude
- Atomic Stuff
- Voltage, Resistance, Current, Power, Energy
- DC Series Circuits
- DC Parallel Circuits
- AC Circuits in brief

Prelude: Scale of Measurement

- Deci = 10^{-1}
- Centi = 10^{-2}
- Milli = 10^{-3}
- Micro = 10^{-6}
- Nano = 10^{-9}
- Pico = 10^{-12}
- Fento = 10^{-15}
- Kilo = 10^3
- Mega = 10^6
- Giga = 10^9
- Tera = 10^{12}

Bits, Bytes, Mega, Giga, Tera (explained)

1 bit = a 1 or 0 (b)

4 bits = 1 nybble (?)

8 bits = 1 byte (B)

1024 bytes = 1 Kilobyte (KB)

1024 Kilobytes = 1 Megabyte (MB)

1024 Megabytes = 1 Gigabyte (GB)

1024 Gigabytes = 1 Terabyte (TB)

What's a Trillion \$ (Tera \$)


<http://www.pagetutor.com/trillion/index.html>

Prelude: 3 Great Forces

- **Nuclear** Strong, very short (subatomic) distances ...
- **Electrostatic** Holds all kinds of stuff together in the everyday world
- **Gravitational** Weakest, but impressive over very large distances and with large masses

Electrostatic Forces

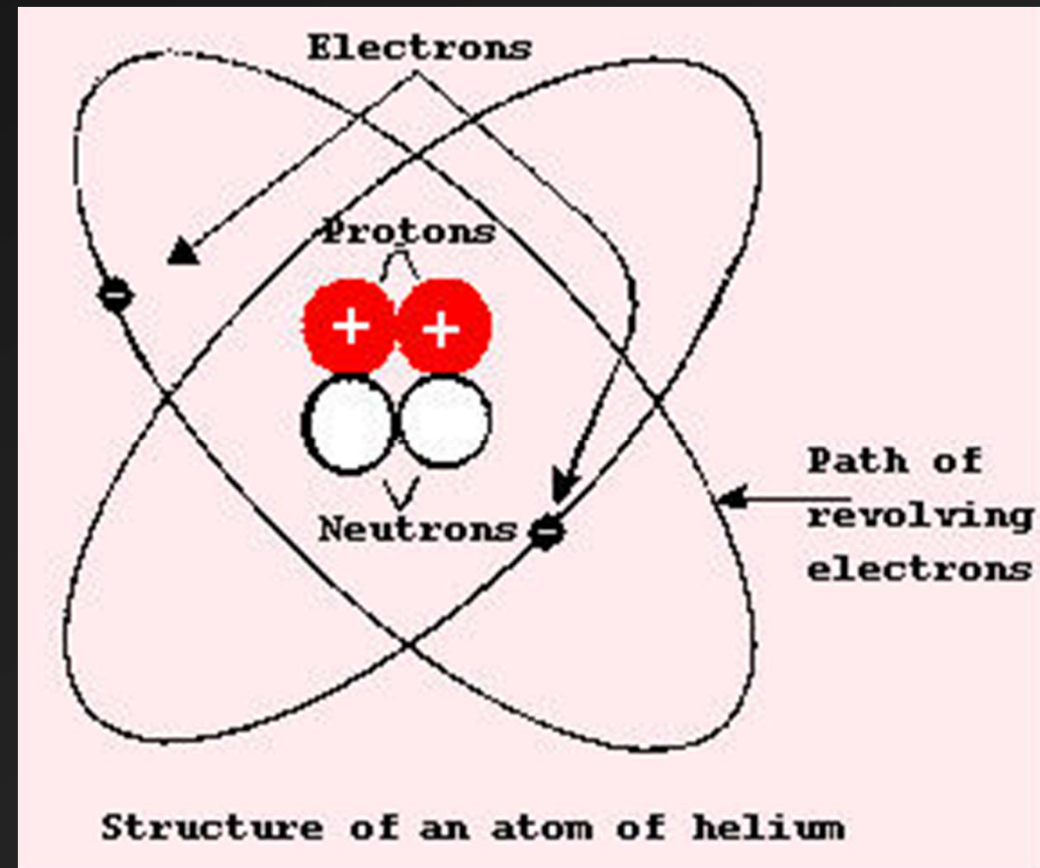
- Due to charged subatomic particles
 - Proton
 - Electron
 - but not Neutron
- The Law:
 - Unlike Charges Attract
 - Like Charges Repel



Free Electrons

➤ Some electrons can be easily displaced


FREE

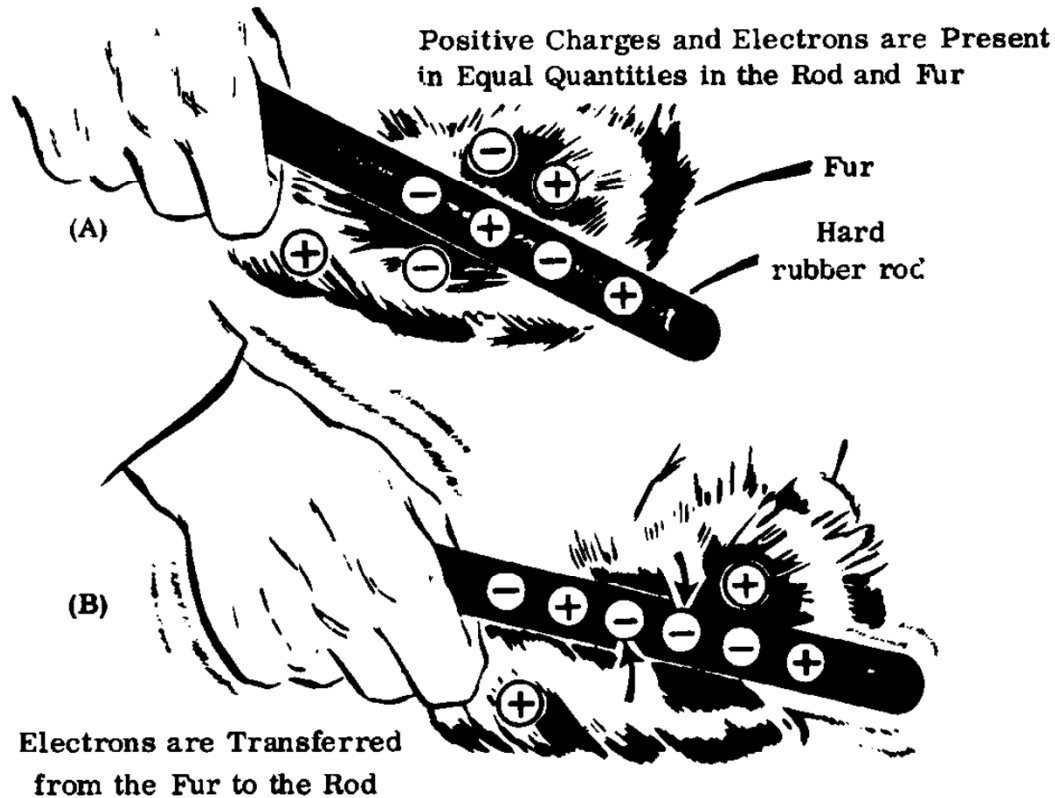


Static Electricity

- Friction with Poor Conductors
- Electrons displaced from one substance to the other (e.g Hair to comb, carpet to body)
- Leads to voltage potential (i.e., difference)

Basic Electricity by Analogy

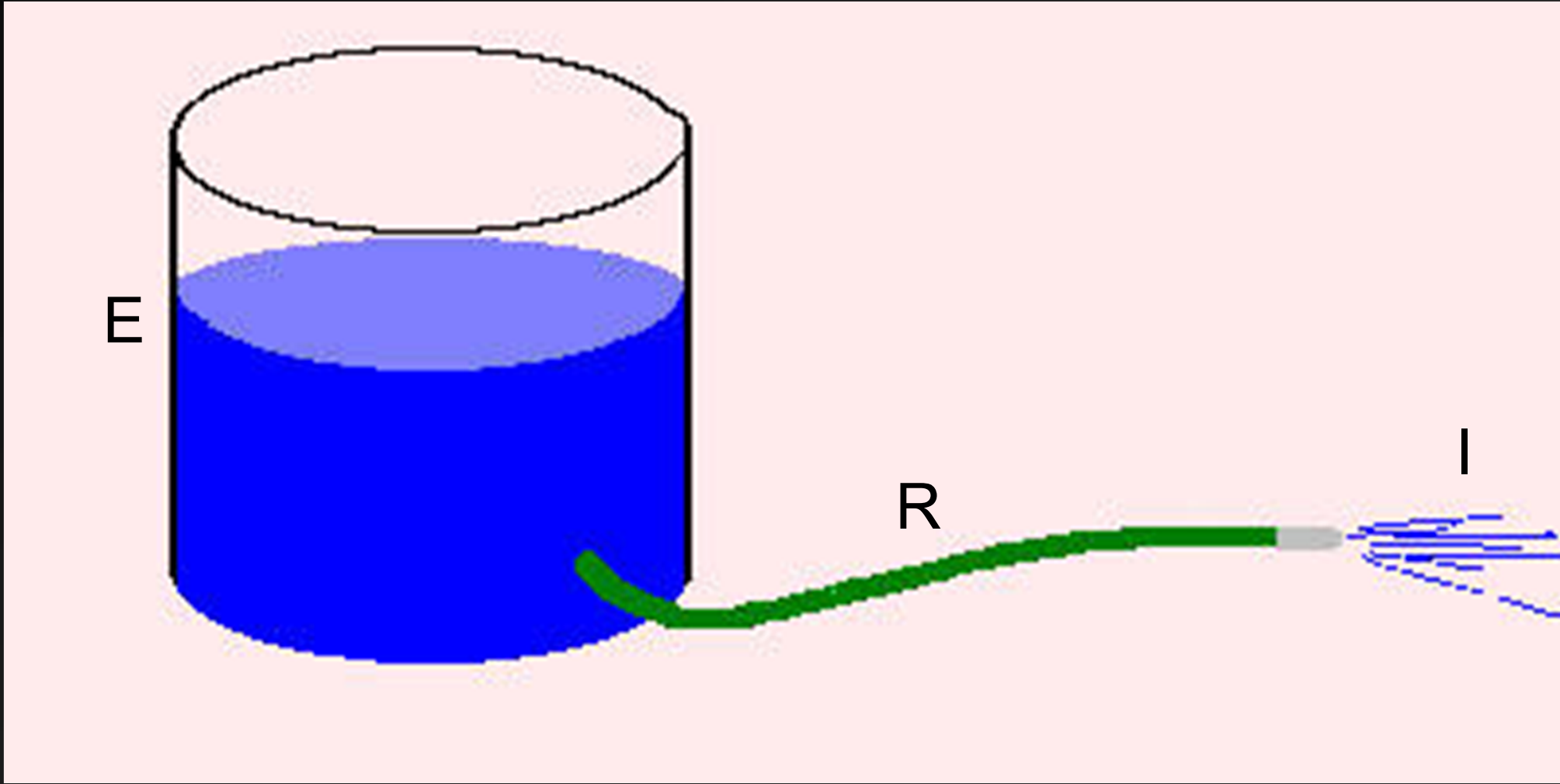

← Direction of Electron Movement

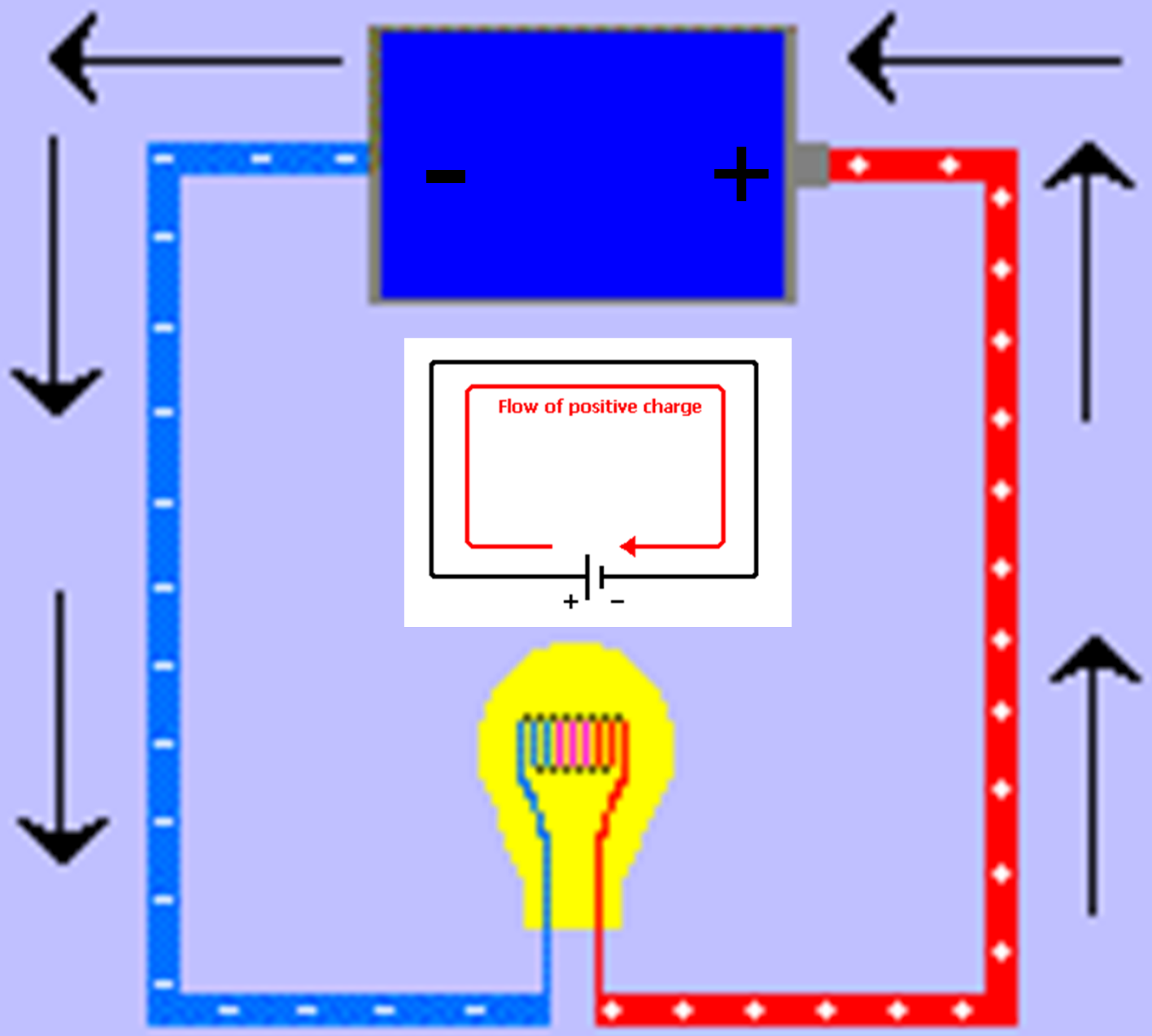

DC
Anyway!

Details Details


Symbol	Term	aka	Unit
E	Voltage	Electromotive Force	Volts (V)
I	Current	Rate of Flow	Amperes (A)
R	Resistance	--	Ohm (Ω)
P	Power	Rate of work	Watt (w)
W	Energy	Ability to do work	Watt-Second (Joule)

Ohm's Law

$$I = \frac{E}{R}$$

$$E = IR$$

$$R = \frac{E}{I}$$

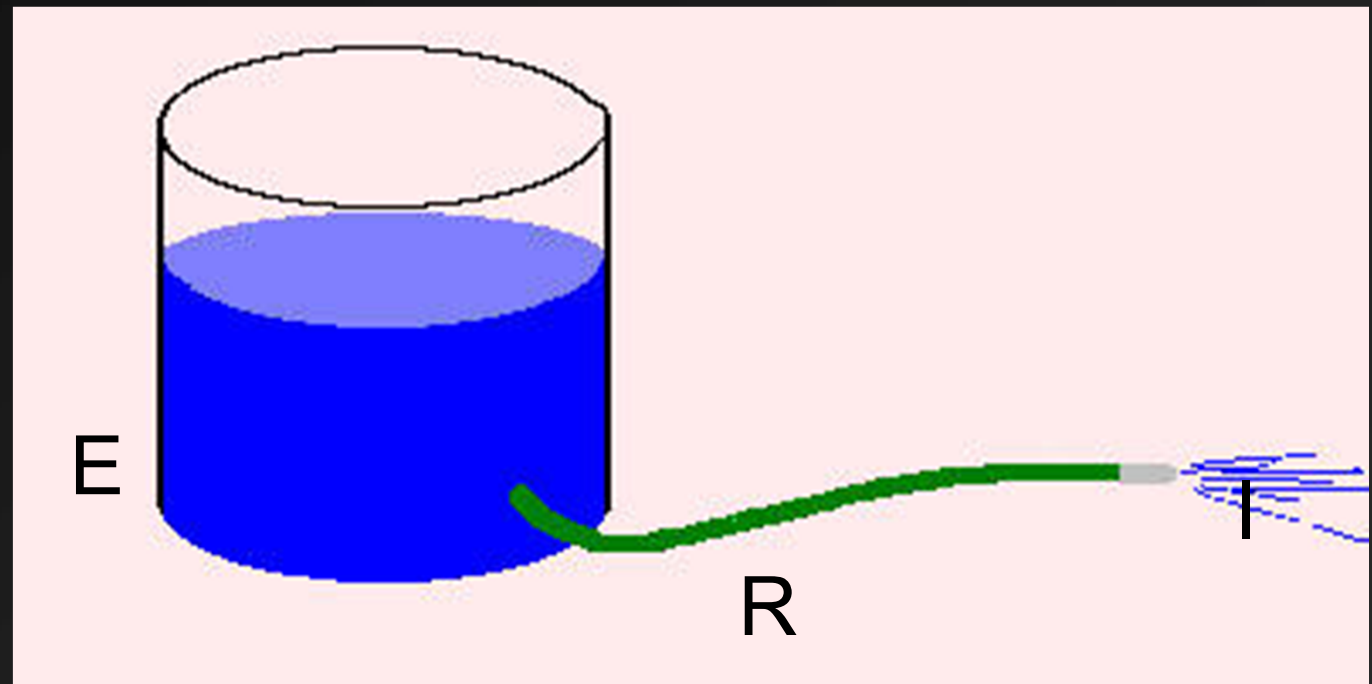


See also: <http://www.falstad.com/circuit/e-ohms.html>


Ohm's Law

$$I = \frac{E}{R}$$


$$E = IR$$

$$R = \frac{E}{I}$$

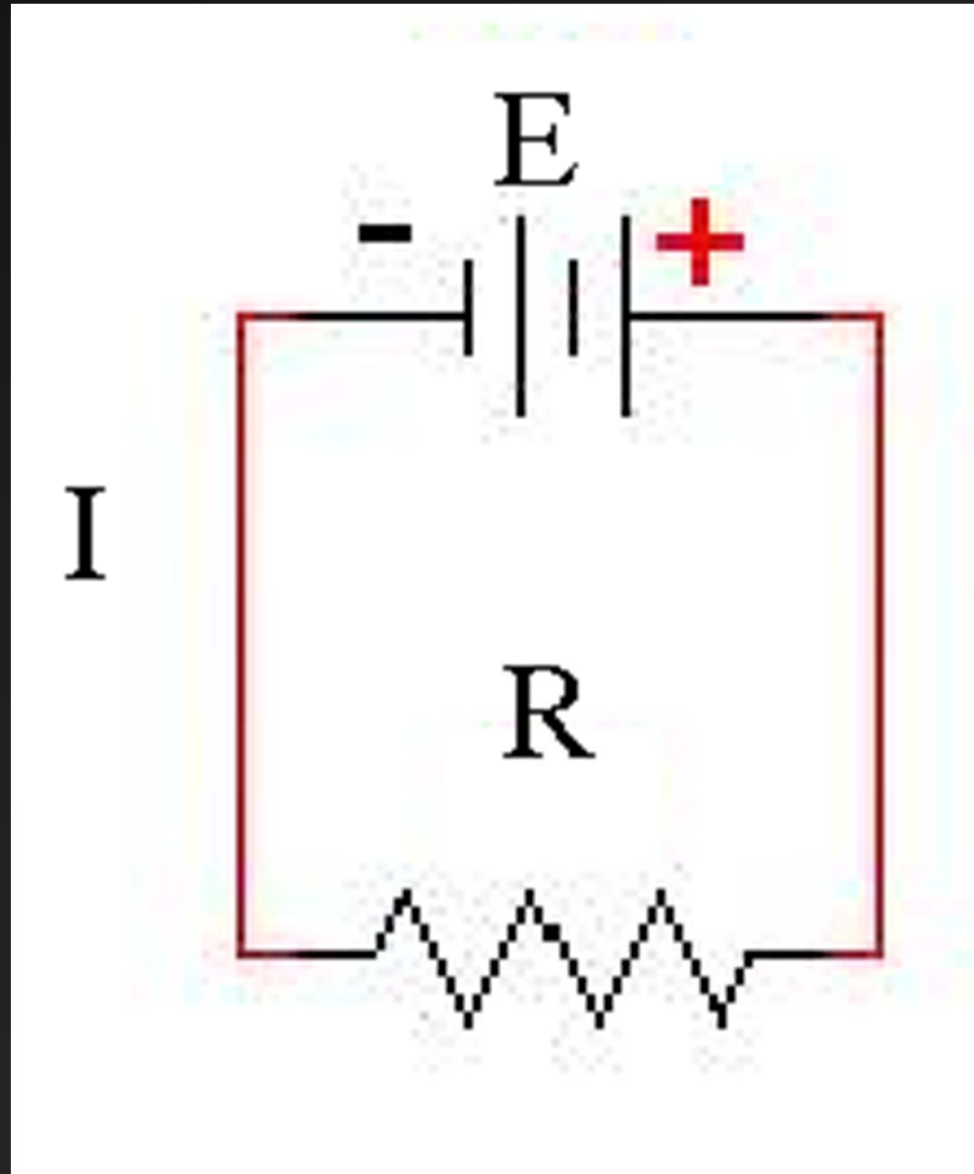


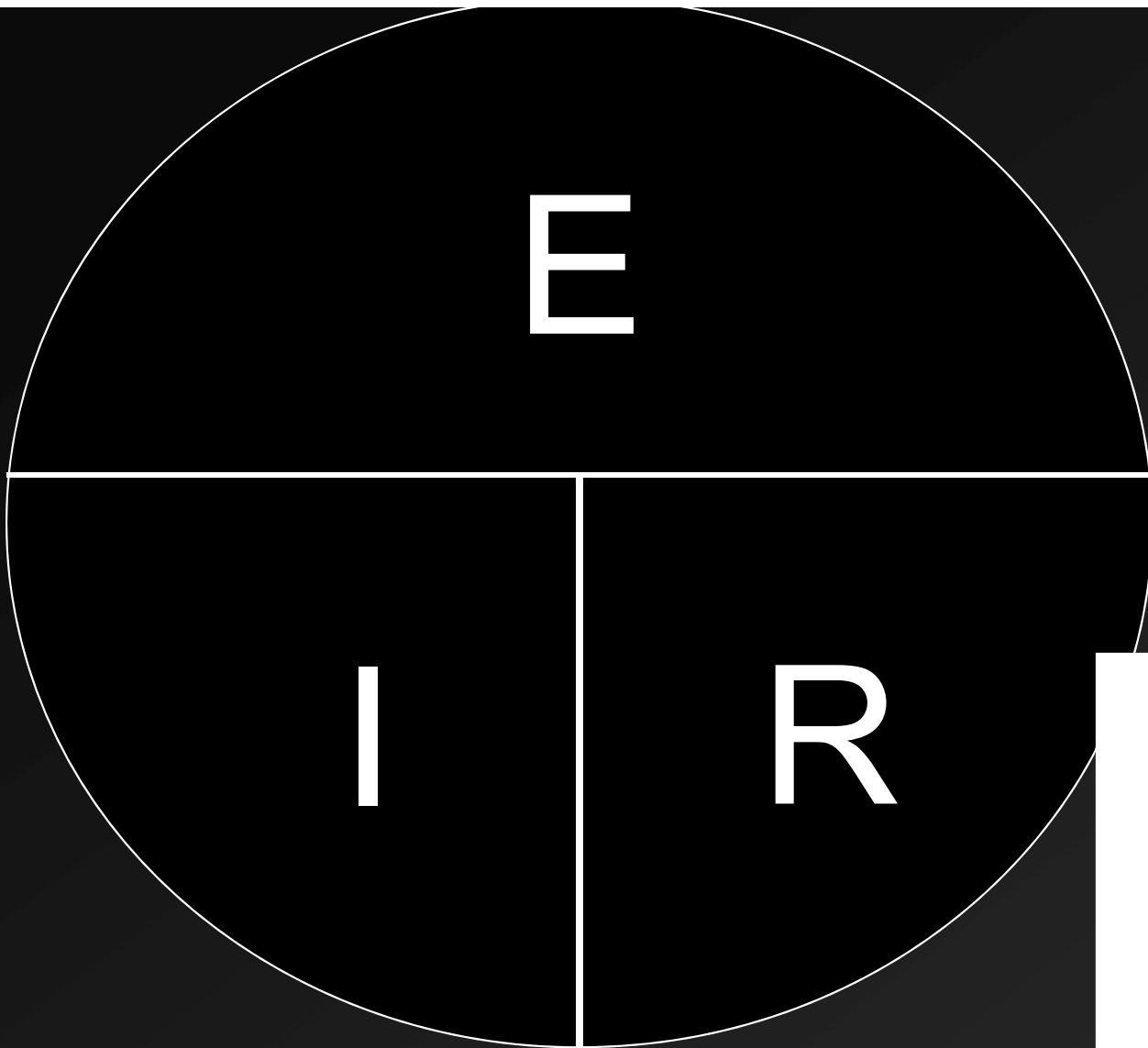

Ohm's Triangle


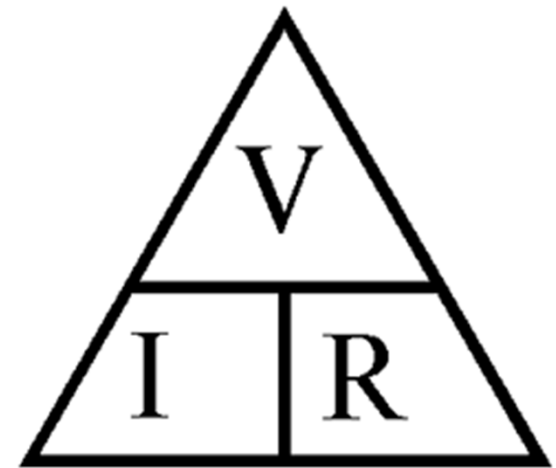


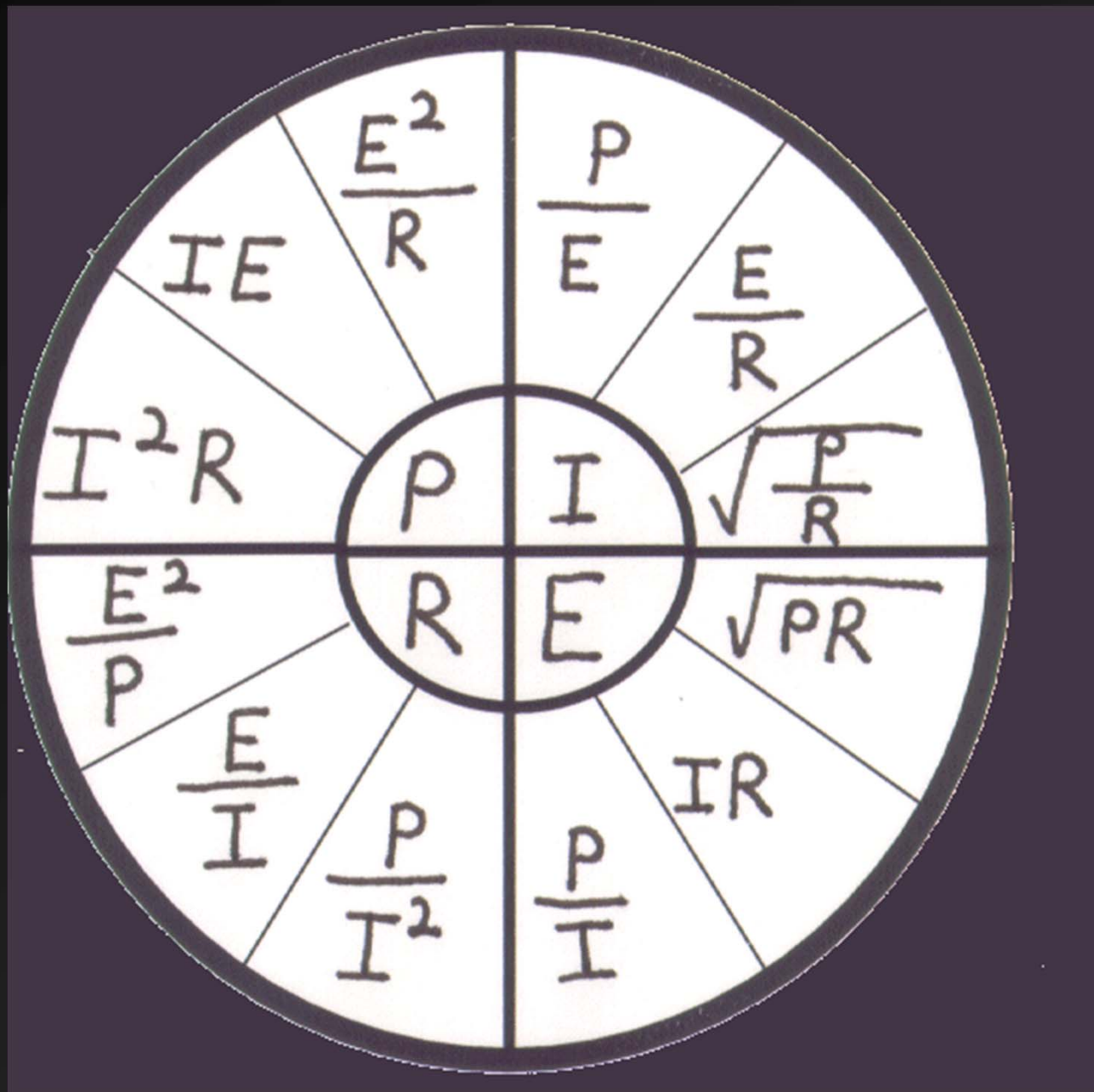Cover the variable you want to find and perform the resulting calculation (*Multiplication/Division*) as indicated.





Basic Circuit

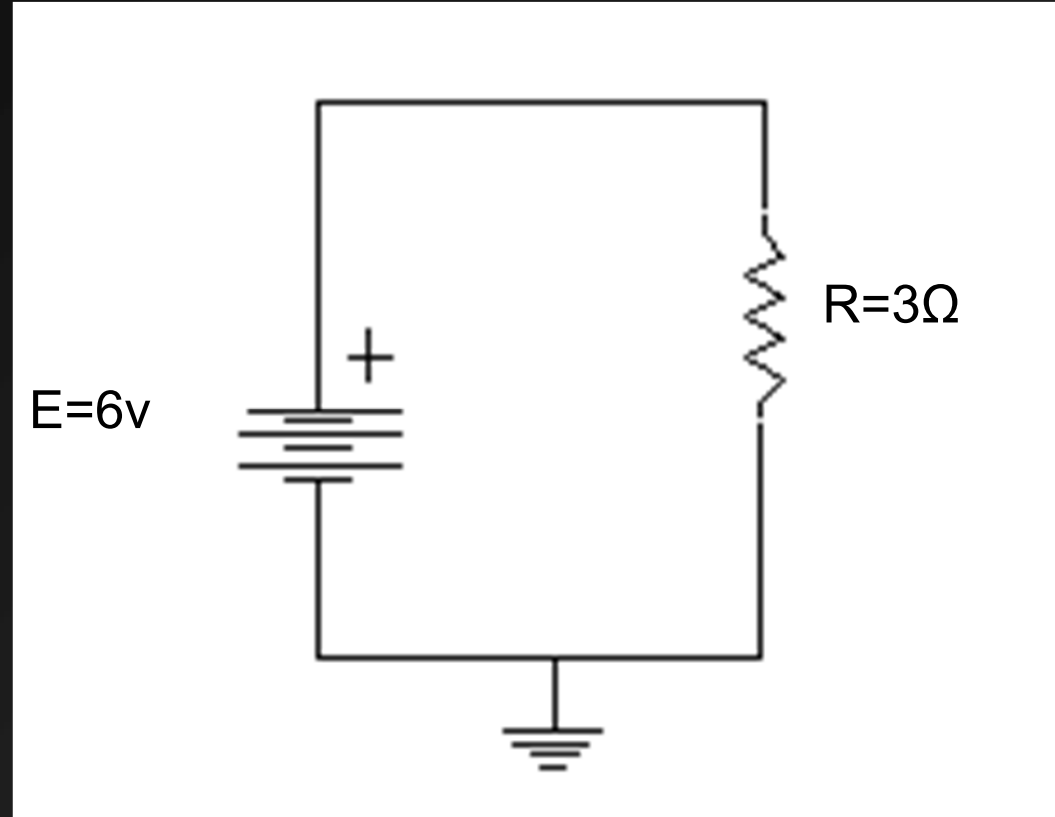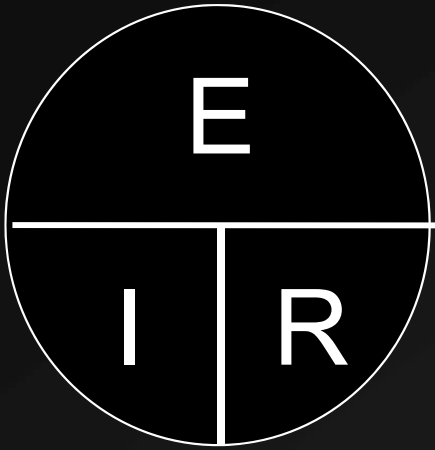

$$I = ?$$

Volt-Ohm Meter Demo




Series Circuit

$$R_T = R_1 + R_2$$

$$I = ?$$


$$E_{R1} = ?$$

$$E_{R2} = ?$$

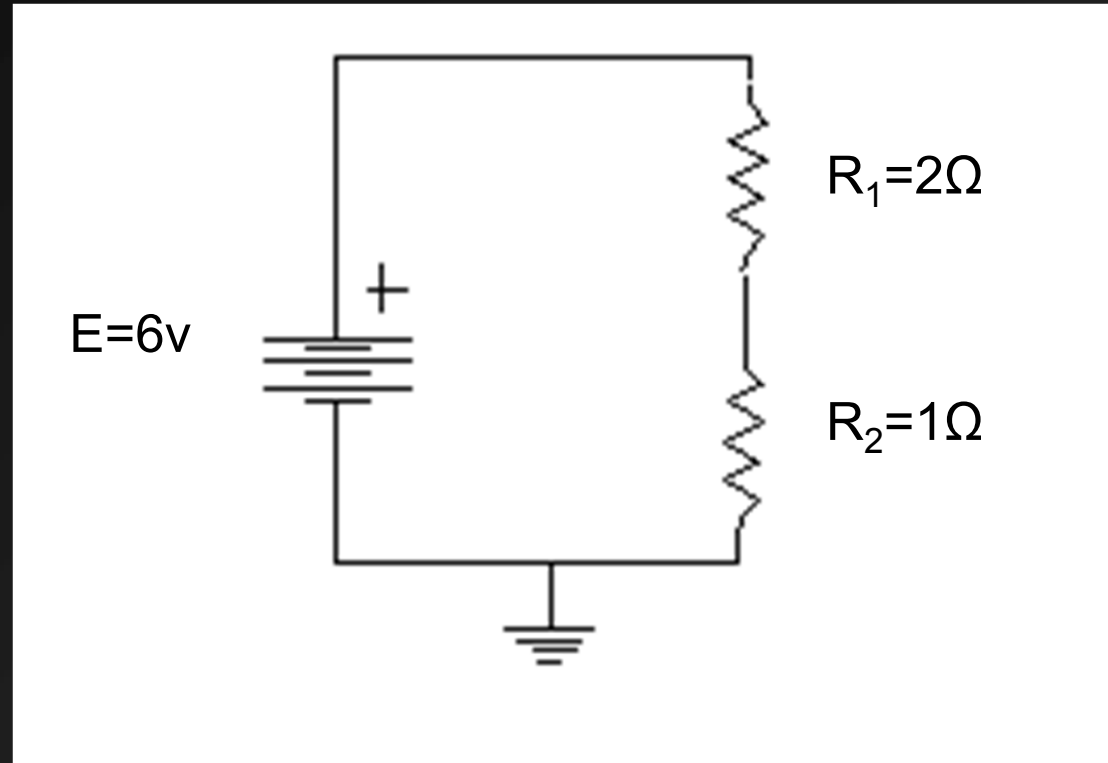


Java Demo


By Analogy: Series Vs Parallel

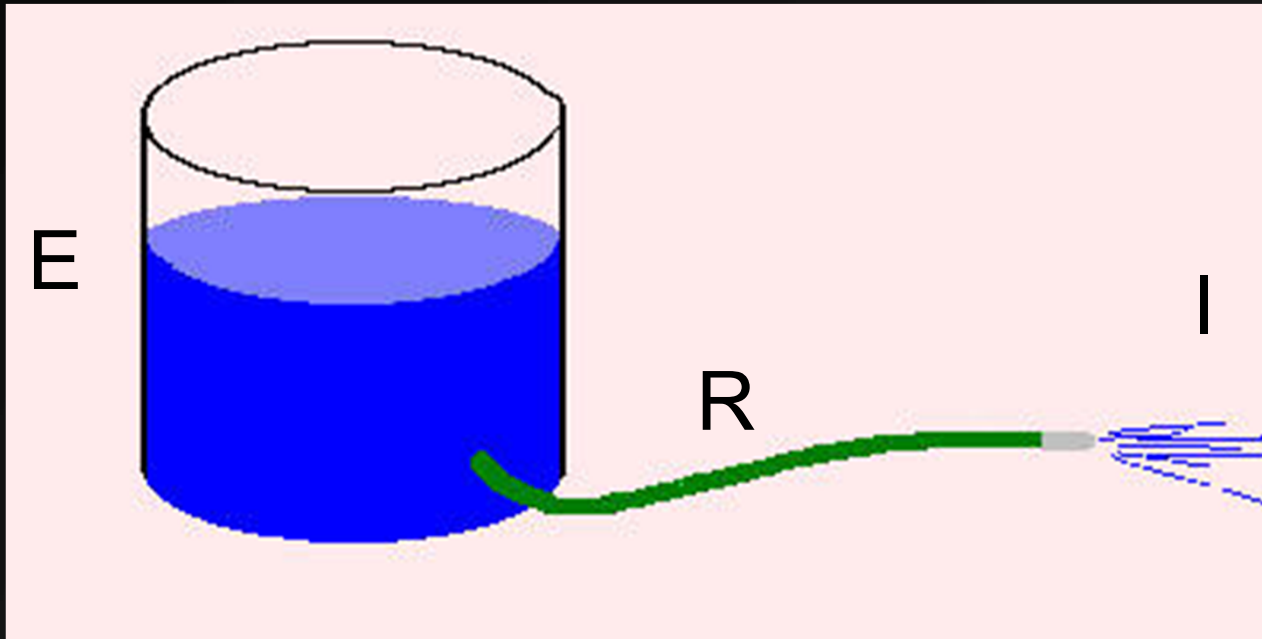
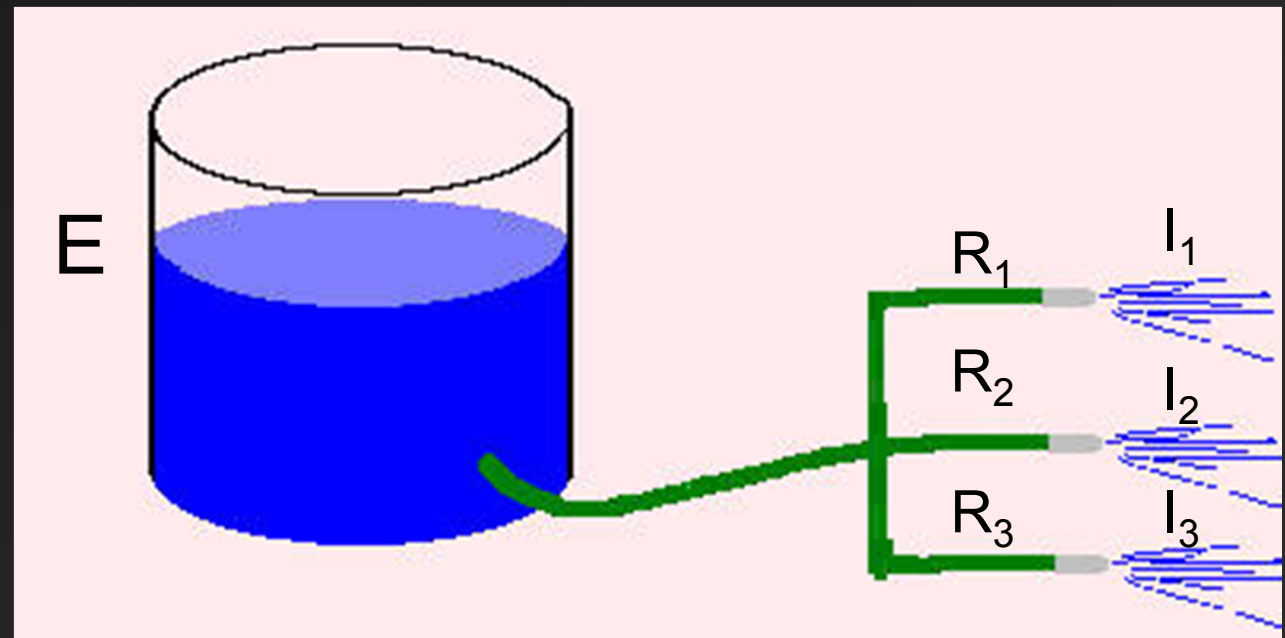
$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$



Parallel Circuit

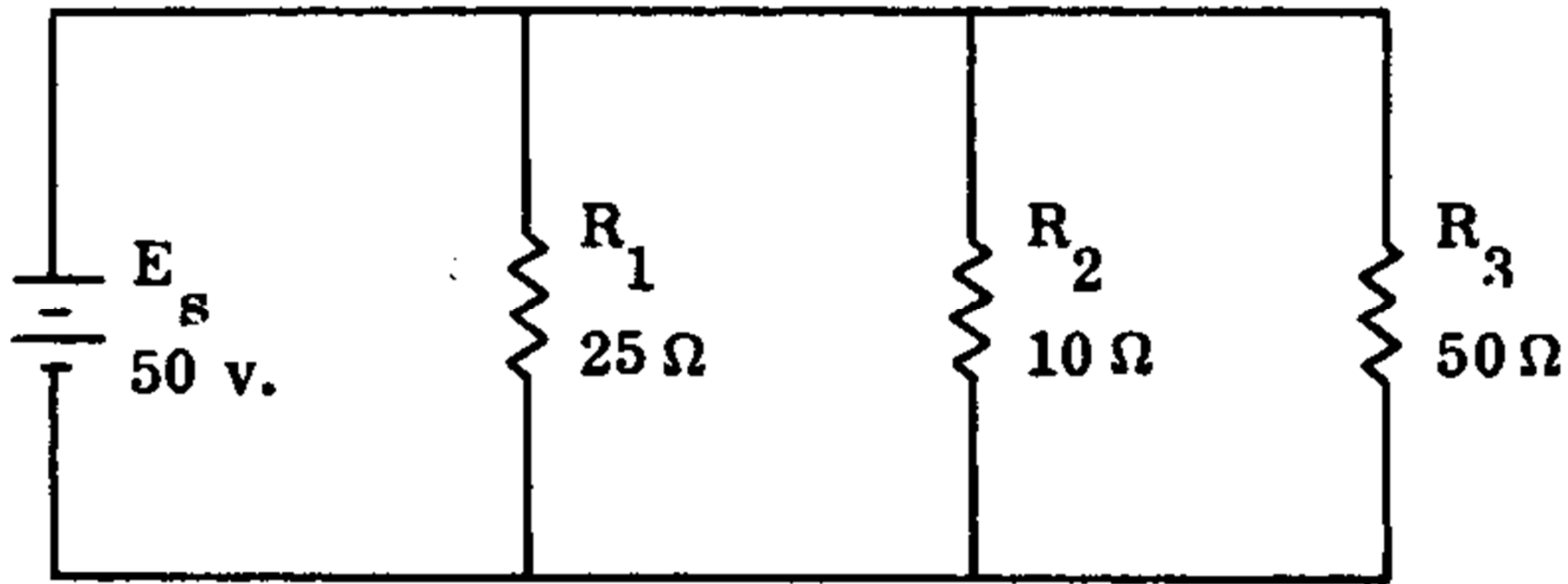

$$R_T = ?$$

$$I_1 = ?$$


$$I_3 = ?$$

$$I_T = ?$$

$$I_2 = ?$$

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$


Complex Circuits

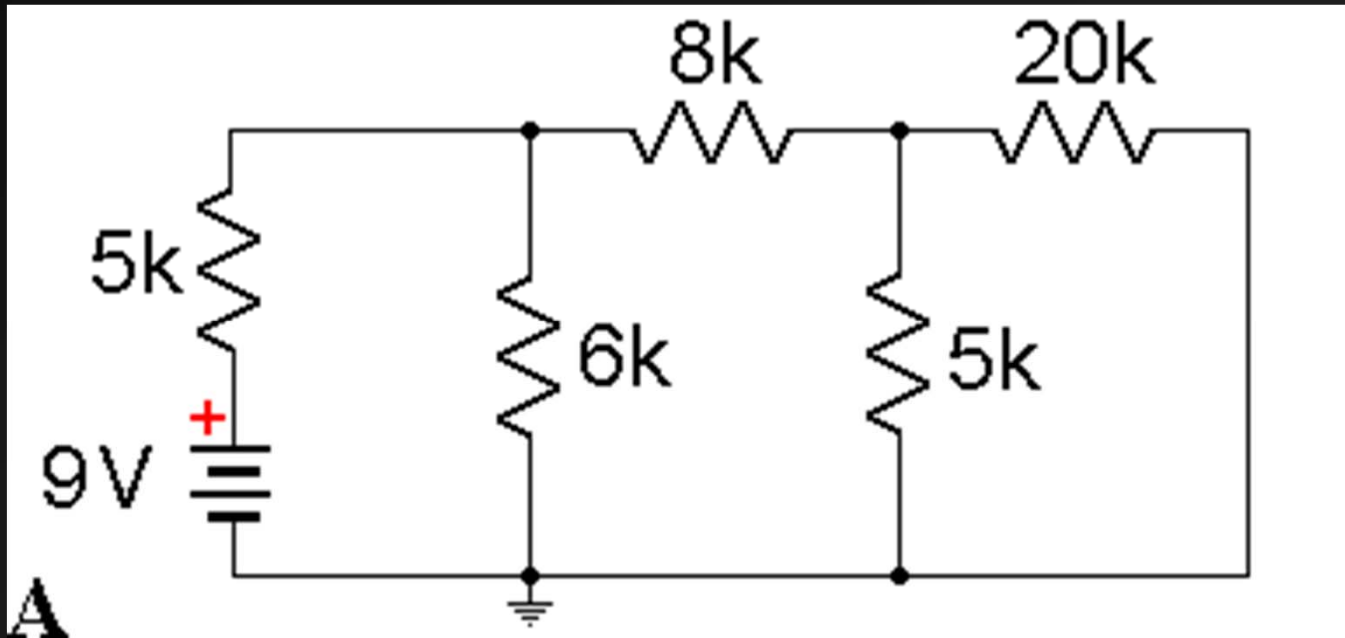

Find the current flowing in the circuit, and the voltage drops.


YIKES! Need to reduce. Start at the parallel combination of 20k and 5k resistors; it is replaced with its effective resistance of 4k
[$1/R_{\text{equiv}} = 1/20 + 1/5 = 1/20 + 4/20 = 5/20 = 1/4$].

Slightly less Complex Circuit

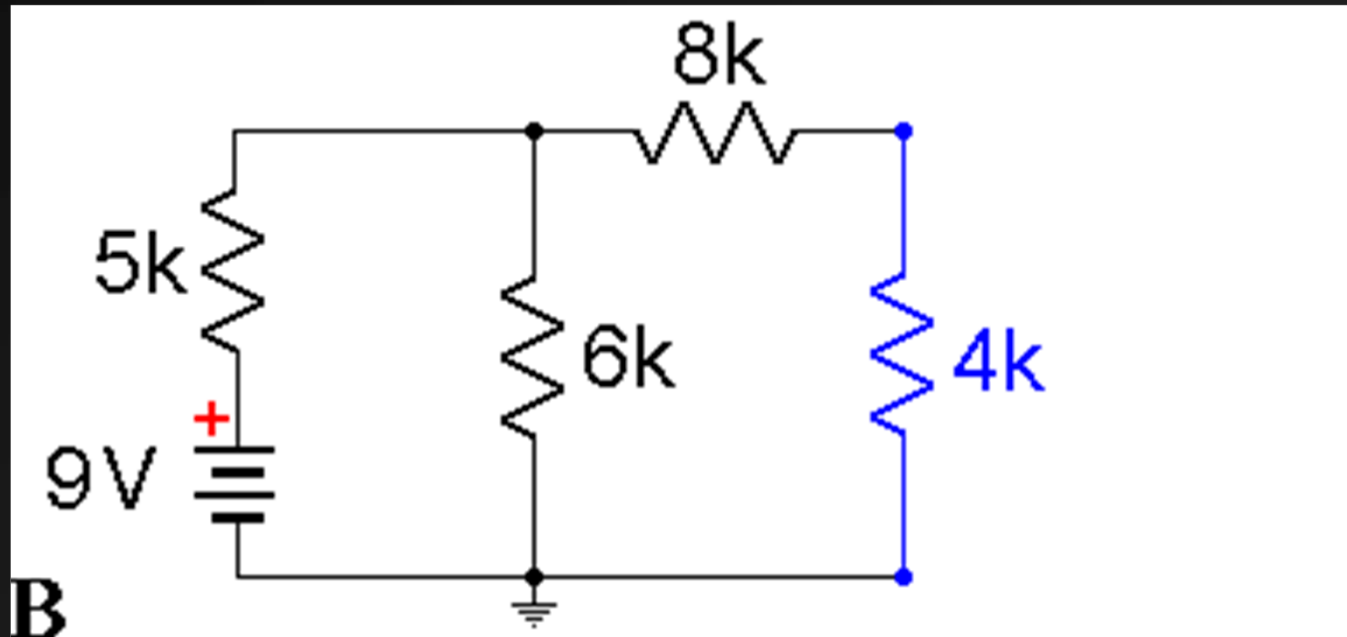


Looking Better. The effective resistance of 4k is in series with the actual resistance of 8k, leading to replacement by its effective resistance of 12k.
[$R_{\text{equiv}} = 4k + 8k$]

Less Complex Still

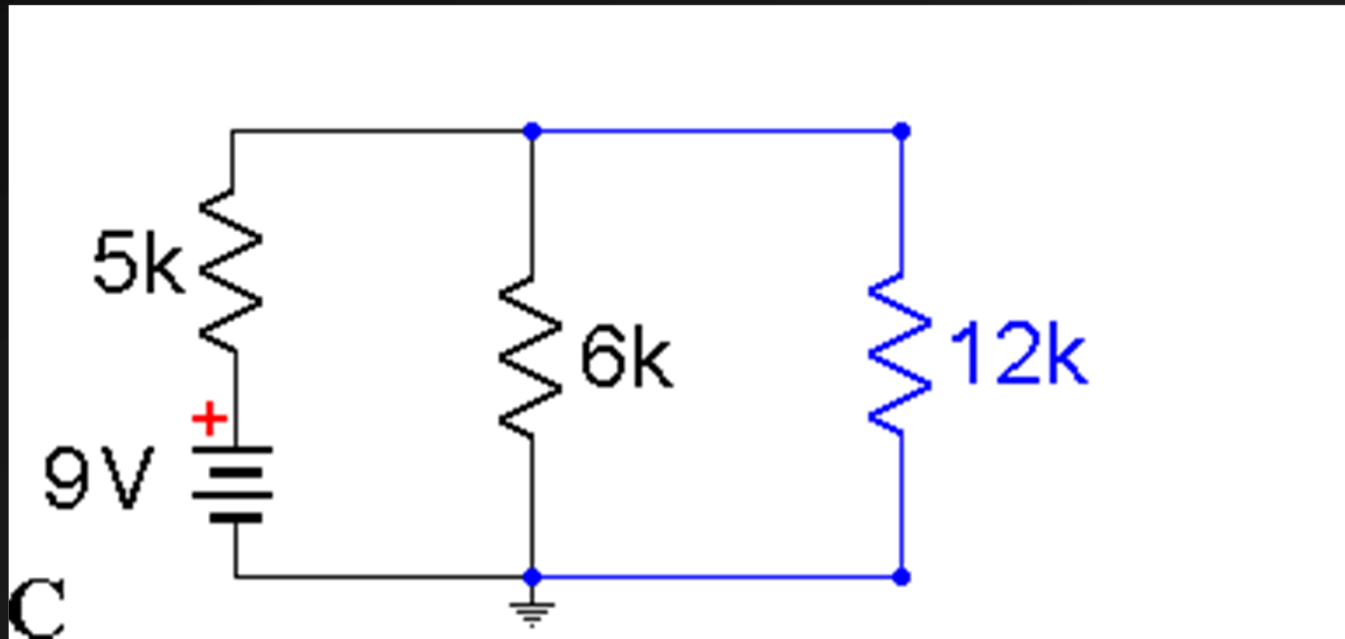

Better Still. Now there is a parallel combination of 12k and 6k resistors; it is replaced with its effective resistance of 4k
[$1/R_{\text{equiv}} = 1/12 + 1/6 = 1/12 + 2/12 = 3/12 = 1/4$].

Now Series: Almost Simple

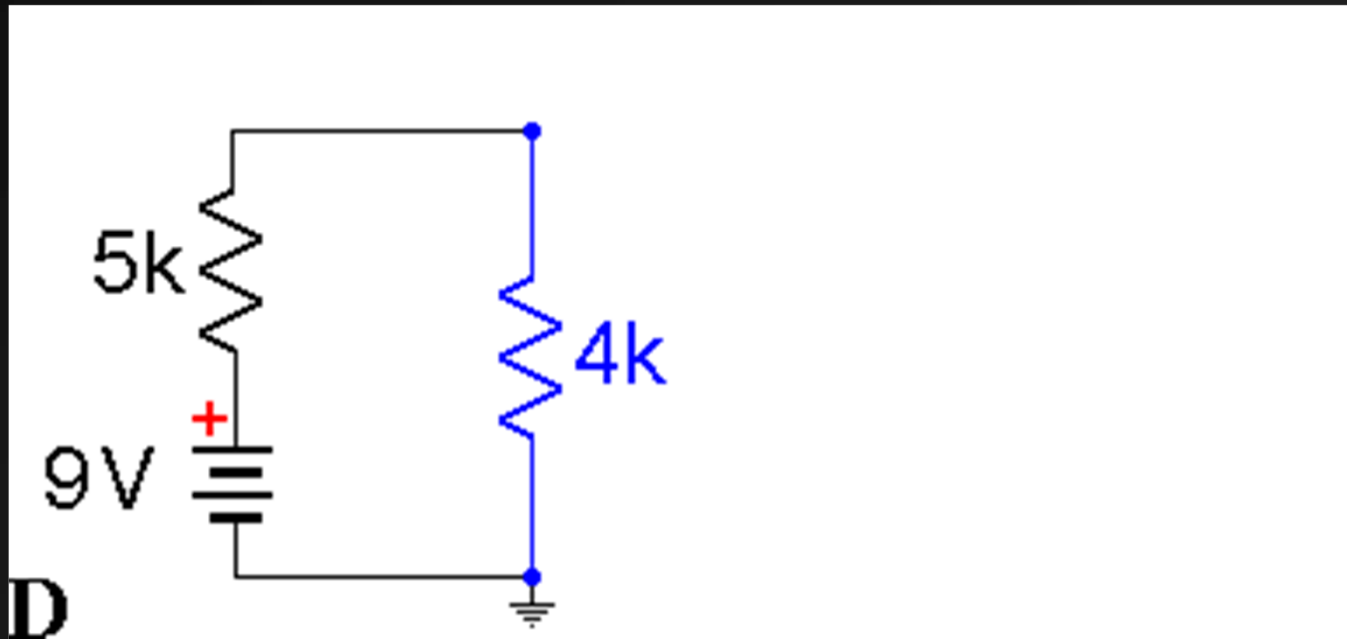


Now we have a simple series circuit!

Finally, the equivalent resistance for the entire circuit is 9k.

$$[R_{\text{equiv}} = 4k + 5k].$$


Now Series: Almost Simple

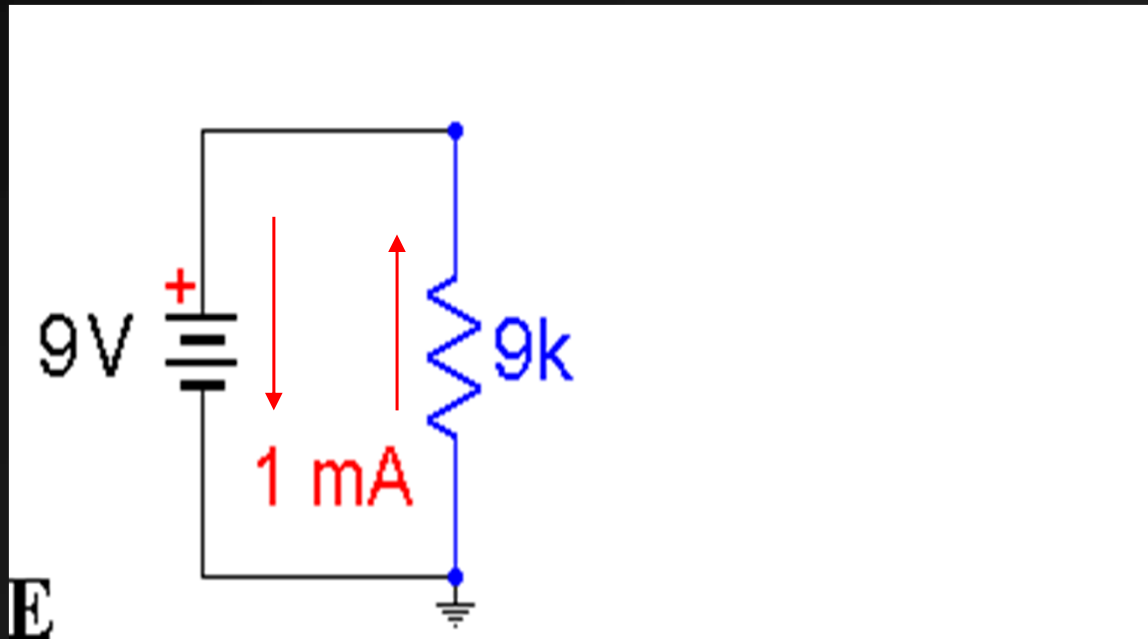

$I = ?$


$$[I = E/R = 9 \text{ V}/9 \text{ k} = 1 \text{ mA}]$$

Working Back: Voltage Drops and Current

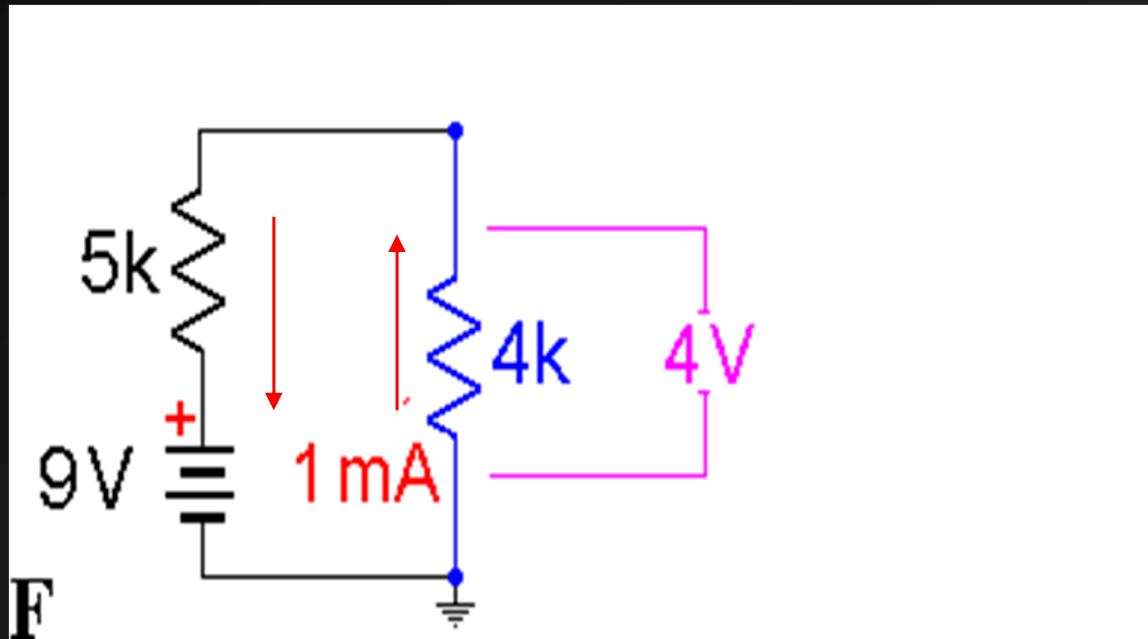

The real 5k resistor and the effective 4k resistance each have 1 mA of current since they are in series. Thus the 4k resistance has 4V of voltage difference across it (by Ohm's law).

Working Back: Voltage Drops and Current

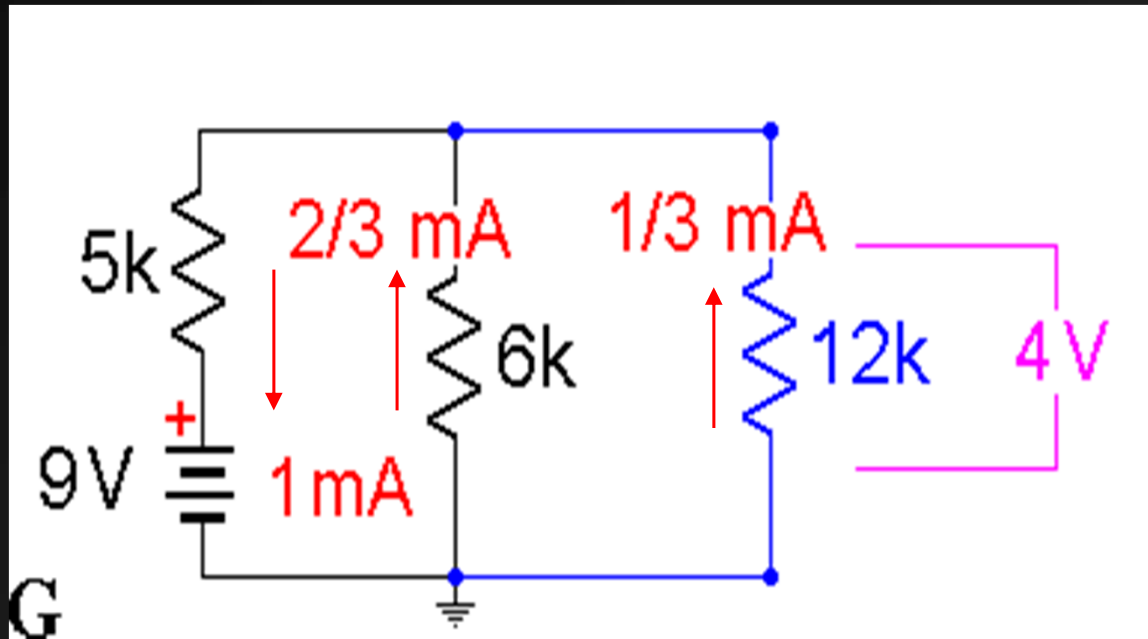


Breaking the 4k resistance into its component parts (in parallel), we find that 2/3 mA of current flows in the 6k resistor and 1/3 mA flows in the effective resistance of 12k.

$$I = E/R = 4/6K = 2/3 \text{ mA}$$

$$I = E/R = 4/12K = 1/3 \text{ mA}$$

Working Back: Voltage Drops and Current

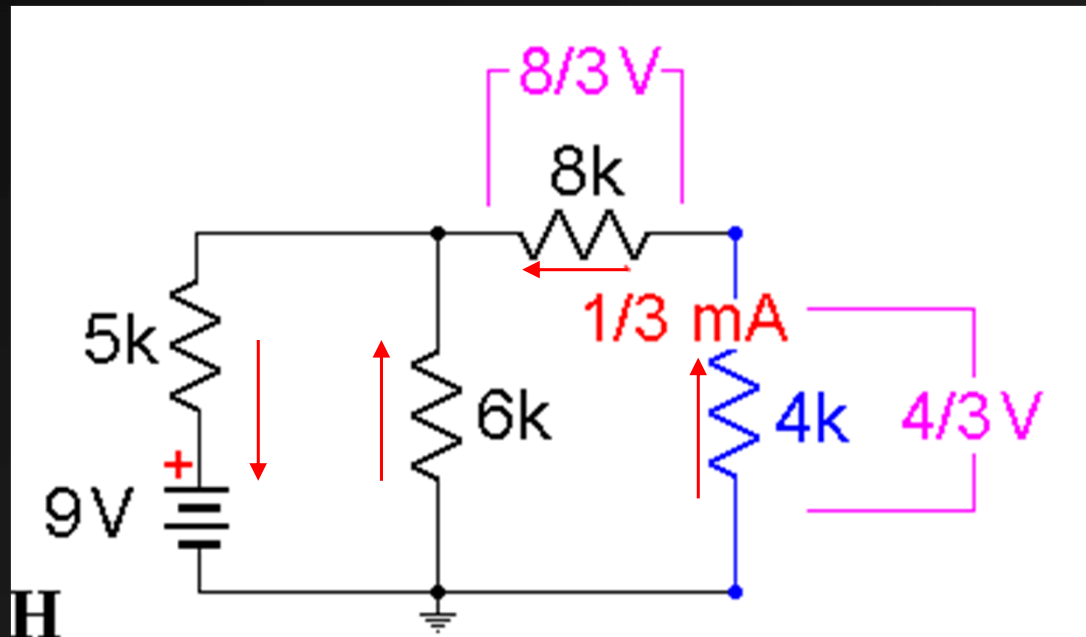


Breaking the 12k resistance into its component parts (in series), we find that there is $8/3$ V across the 8k resistor and $4/3$ V across the effective resistance of 4k.

$$E = IR = 4K\Omega * 1/3 \text{ mA} = 4/3 \text{ V}$$

$$E = IR = 8K\Omega * 1/3 \text{ mA} = 8/3 \text{ V}$$

Working Back: Voltage Drops and Current

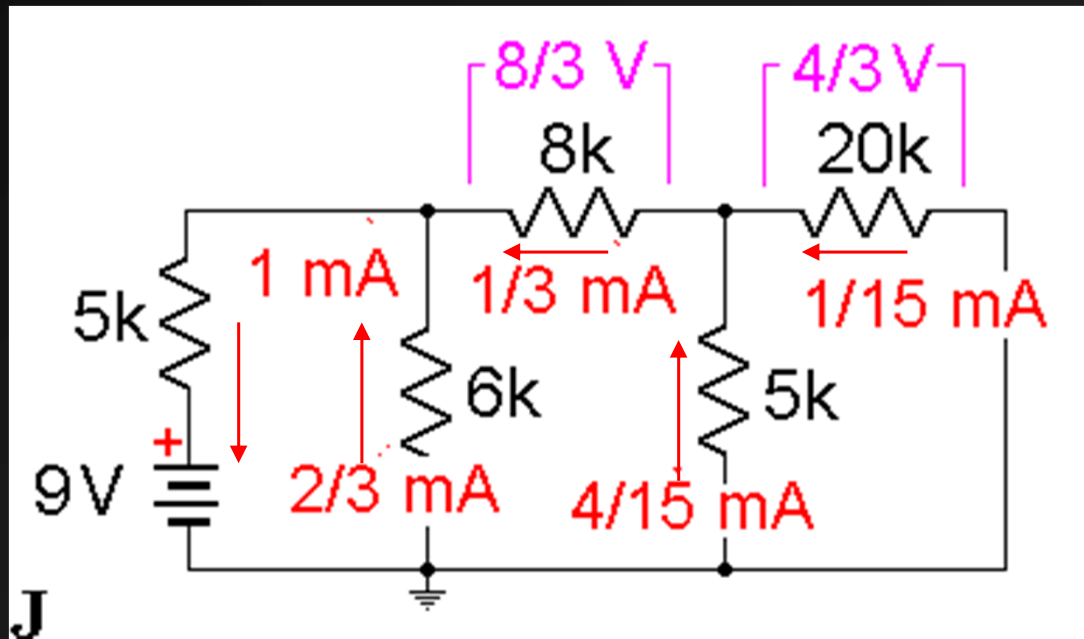


Finally, breaking the 4k resistance into its component parts (in parallel), we find that 1/15 mA of current flows in the 20k resistor and 4/15 mA flows in the 5k resistor.

$$I = E/R = (4/3V)/20K\Omega = 4/60 \text{ mA} = 1/15 \text{ mA}$$

$$I = E/R = (4/3V)/5K\Omega = 4/15 \text{ mA}$$

Working Back: Voltage Drops and Current

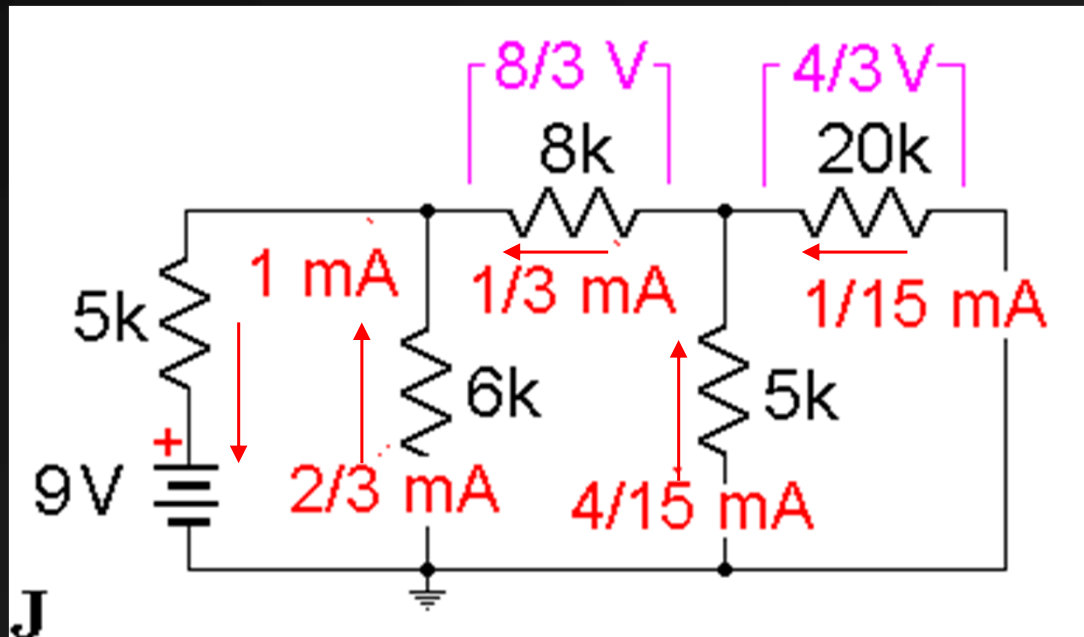


Summarizing:

- | | |
|--|--------|
| 1. Current through the battery? | 1 mA |
| 2. Current through the 8k resistor? | 1/3 mA |
| 3. Voltage difference across the 20k resistor? | 4/3 V |


In Real Life...

B. MARSHALL-GOODELL, L. TASSINARY, AND J. CACIOPPO




a) Series Circuit

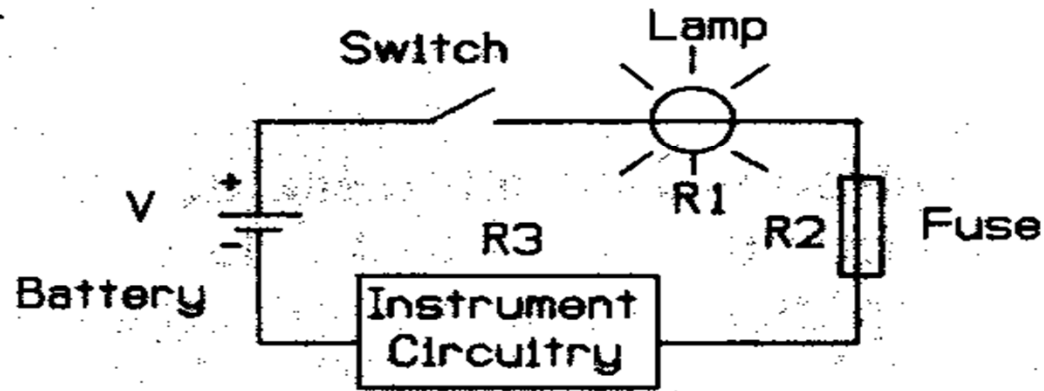

b) Parallel Circuit

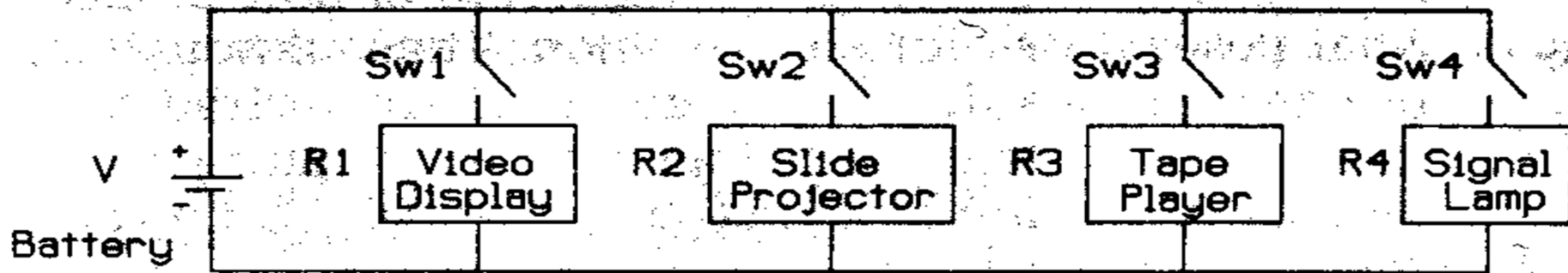

Capacitance

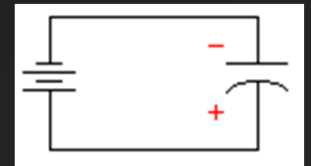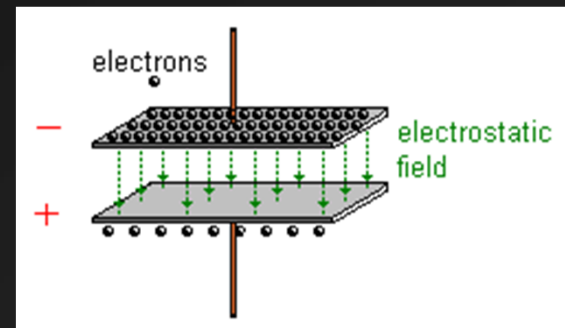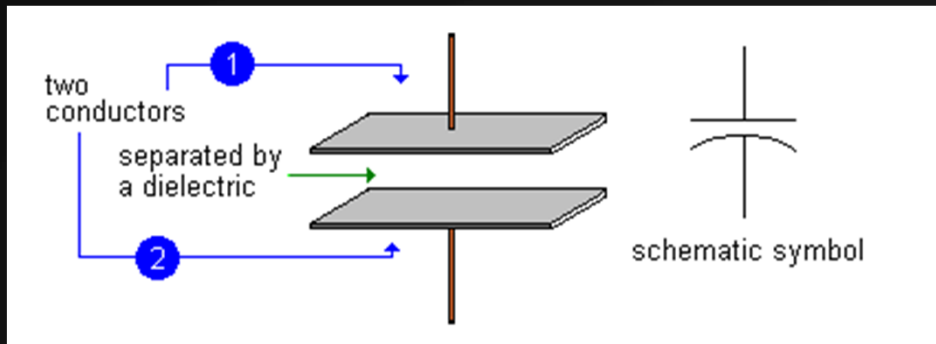

Capacitor = two conductors separated by a dielectric.

Dielectric = material that is a good insulator (incapable of passing electrical current), but is capable of passing electrical fields of force. Examples include glass, porcelain.

Charged Capacitor = more electrons on one conductor plate than on the other.


Capacitance

- Two closely spaced plates – offer essentially no resistance




- As negative charge built up on first plate due to flow of electrons, a positive charge would build up on second plate
 - The current **charges** the plates of the capacitor, **but does not flow through the capacitor**, itself.

Capacitance

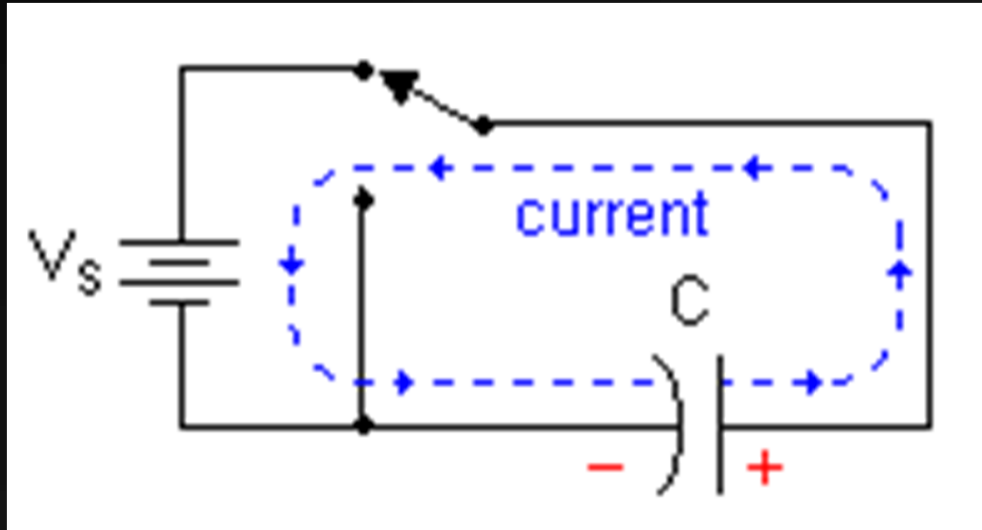

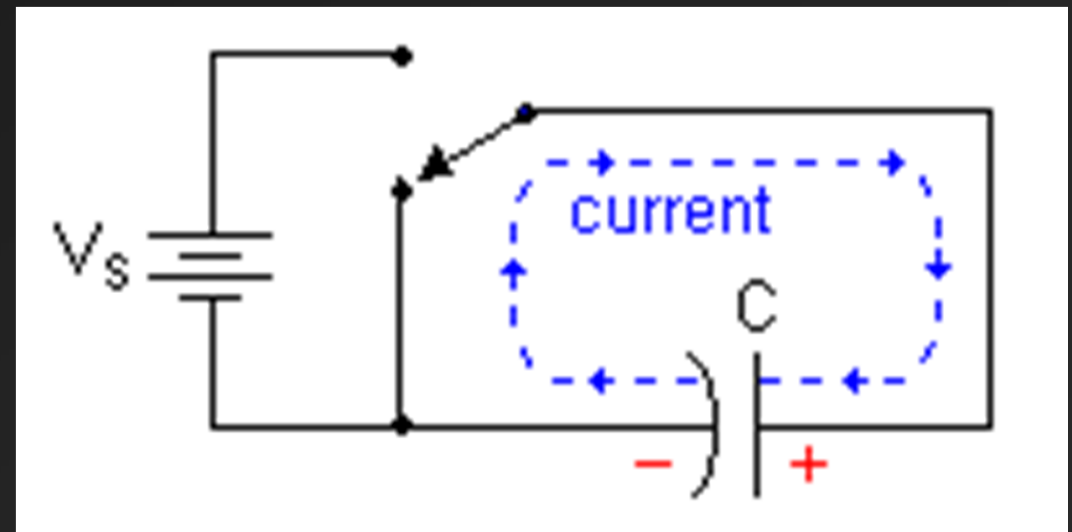Charging – current flows until capacitor is fully charged, then stops



Discharging – current flows in reverse direction until capacitor fully discharged



Capacitance – Size Matters

➤ Which has more capacity?



➤ More capacity, more current flows before capacitor is fully charged

Capacitor Time Constants

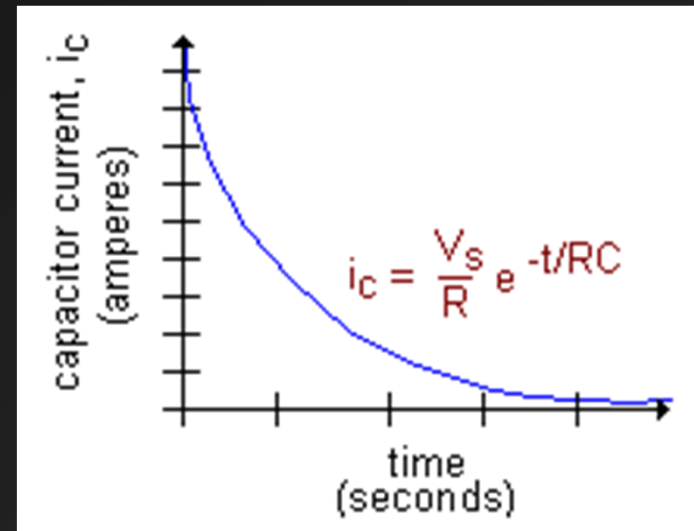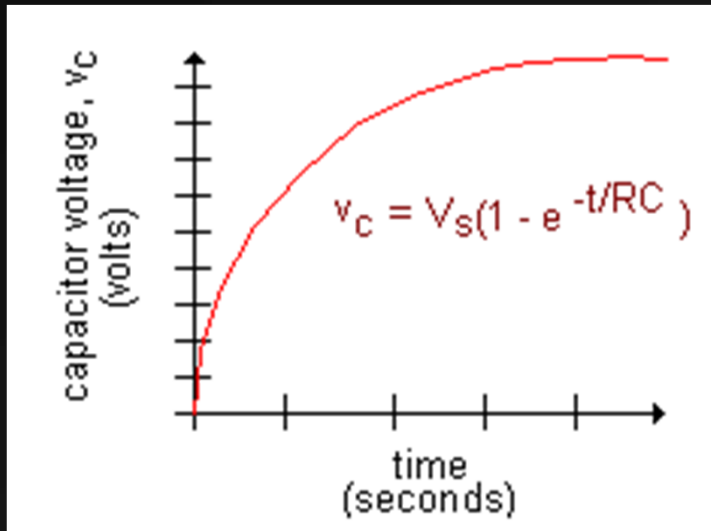

Over time...


Capacitor's voltage increases

Current flow grinds to a halt

The capacitor's time constant $TC =$

- The time in seconds for it to become 63.2% charged
- The time in seconds for current flow have slowed by 63.2% from its starting value


AC Circuits

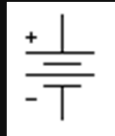

DC Circuit: Current Flow is unidirectional, from
– to +



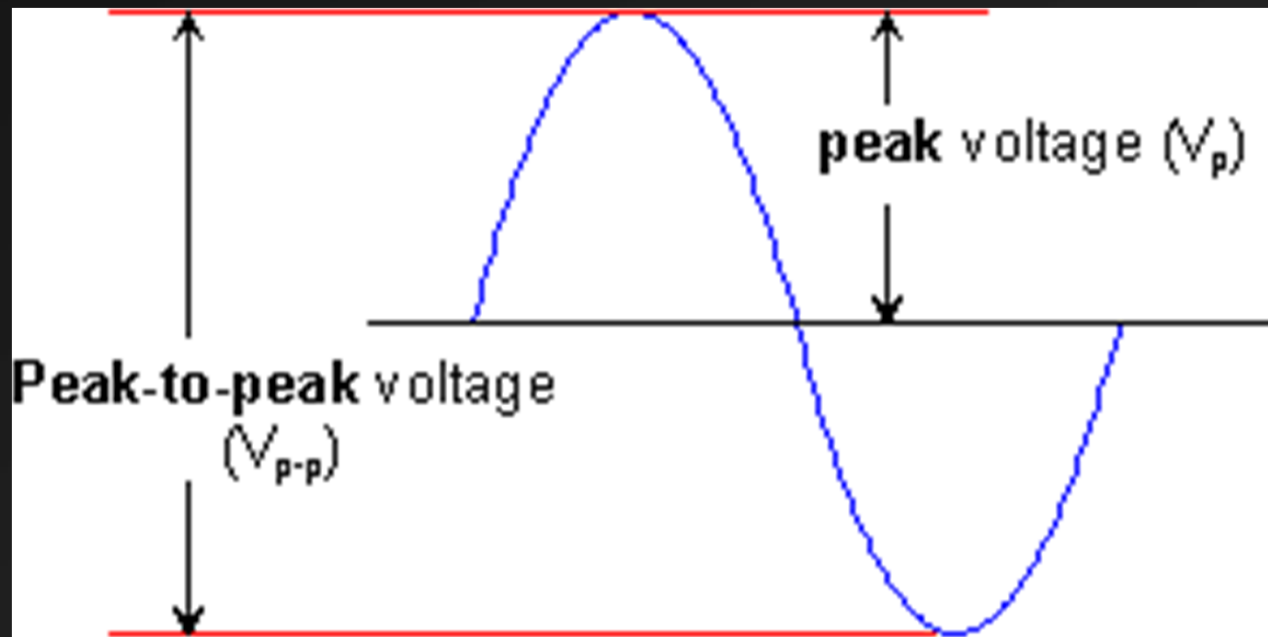AC Circuit: Current Flow switches direction
periodically (at a given frequency in Hz)




AC Circuits and Capacitance

- Slowly alternating signals
 - will fully charge capacitor, and signal will be impeded
- Rapidly alternating signals
 - will not fully charge the capacitor before the direction of flow reverses, allowing signals to pass unimpeded

<http://micro.magnet.fsu.edu/electromag/java/capacitor/>


http://www.vjc.moe.edu.sg/academics/dept/physics_dept/applet/rc/rc.htm

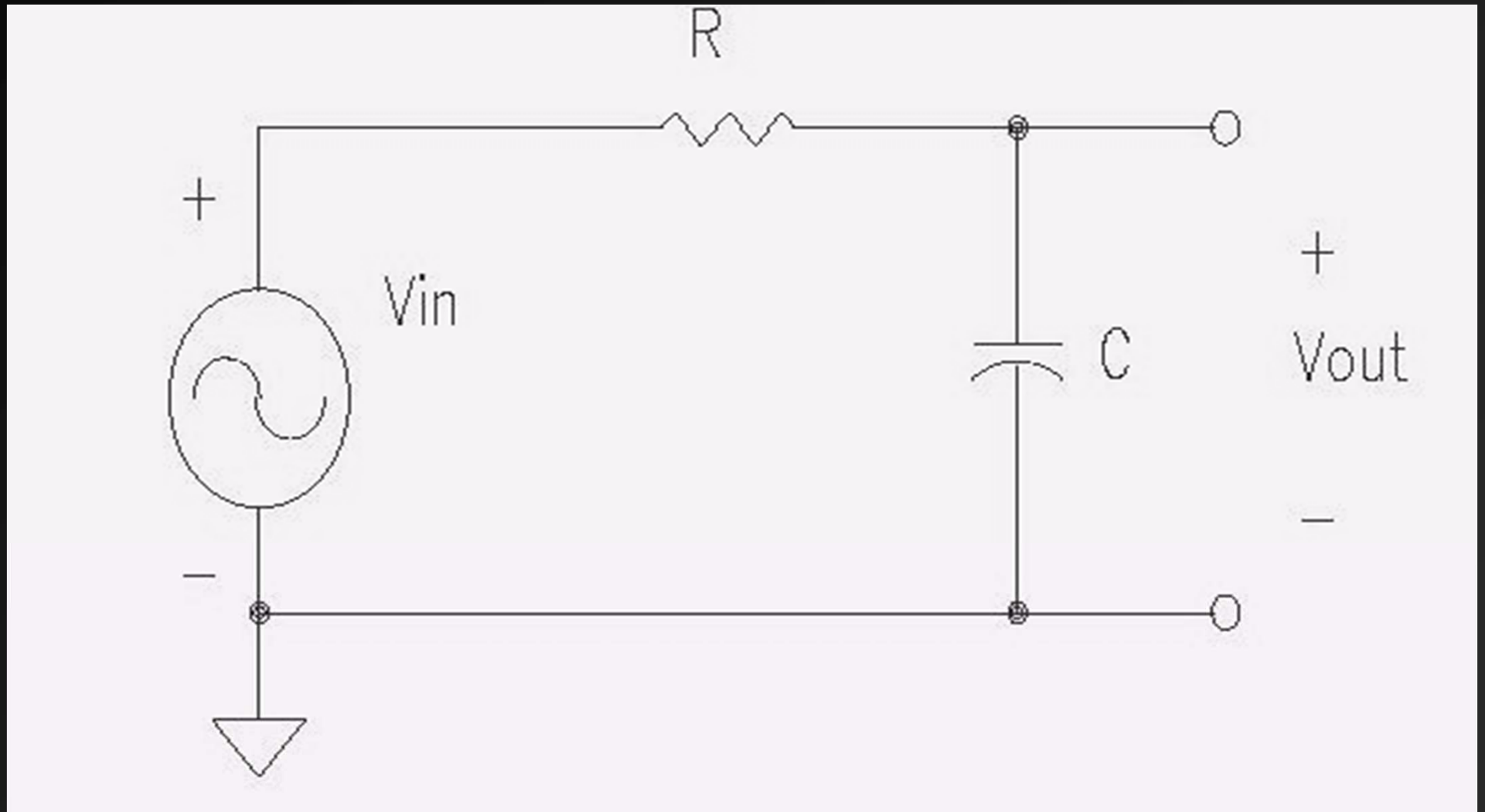Using Capacitors to make Low Pass Filters



What will happen to fast signals; slow signals?

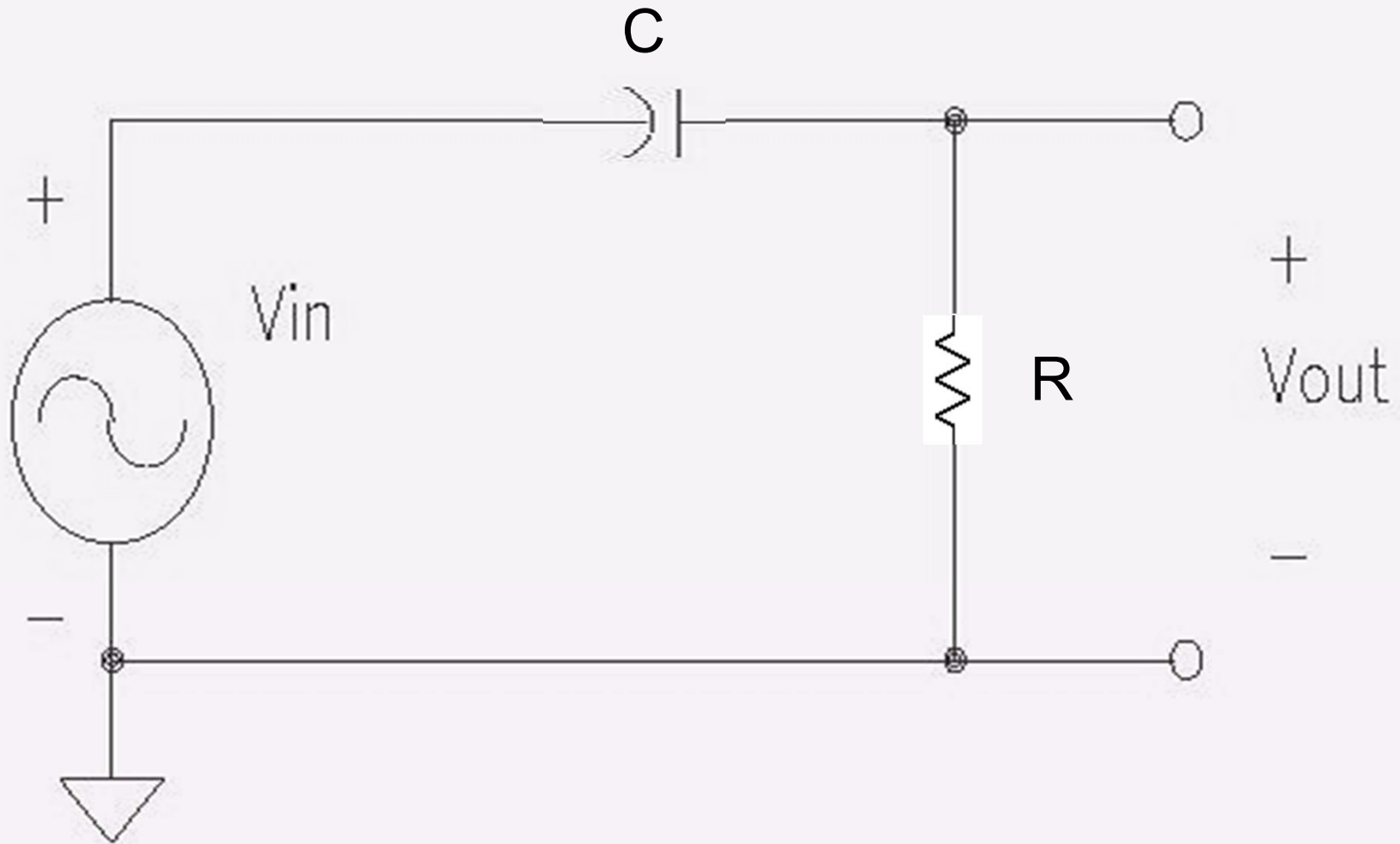Using Capacitors to make High Pass Filters



What will happen to fast signals; slow signals?

