

Lecture 2

1 February, 2016

Announcements (02/01/16)

- 401B and 501B:
 - Laboratory Meeting Tues Feb 2, 4⁰⁰-7⁰⁰ pm
- Electricity Test in 2 weeks (Feb 15)

In 3x5 Time...

For disorders like PTSD, what is the best way (aside from self-report) to measure/gauge the extent of these disorders psychophysiologicaly?

Stage Show Skits (from

www.asc/hyp/art/skits.html

jects that they will begin to notice a bad
n the person sitting next to them.

ing hippies from the 60's.

oming the hypnotist. On the count of three
e the group.

n glasses without the lenses to a subject
n that these are X-ray glasses. Allow the
er the audience.

ree you will all begin to yawn. You will
not be able to stop yawning until you see someone else in
the audience yawning. When you see someone else yawning
in the audience you will then go to sleep.

Foundations:

Basic Electricity

Basic Neurophysiology

Basic Neuroanatomy

Part I: Basic Electricity

- Prelude
- Atomic Stuff
- Voltage, Resistance, Current, Power, Energy
- DC Series Circuits
- DC Parallel Circuits
- AC Circuits in brief

Prelude: Scale of Measurement

- Deci = 10^{-1}
- Centi = 10^{-2}
- Milli = 10^{-3}
- Micro = 10^{-6}
- Nano = 10^{-9}
- Pico = 10^{-12}
- Fento = 10^{-15}
- Kilo = 10^3
- Mega = 10^6
- Giga = 10^9
- Tera = 10^{12}

Bits, Bytes, Mega, Giga, Tera (explained)

1 bit = a 1 or 0 (b)

4 bits = 1 nybble (?)

8 bits = 1 byte (B)

1024 bytes = 1 Kilobyte (KB)

1024 Kilobytes = 1 Megabyte (MB)

1024 Megabytes = 1 Gigabyte (GB)

1024 Gigabytes = 1 Terabyte (TB)

What's a Trillion \$ (Tera \$)

<http://www.pagetutor.com/trillion/index.html>

544 gigadollars

Under the Congressional Budget Office (CBO) forecast, the annual budget deficit will increase, as a share of the nation's gross domestic product, to ~~\$544 billion~~ – the first time it has done so since 2009, when the deficit peaked at ~~\$1.4 trillion~~.

1.4 teradollars

Over the next 10 years, CBO projects that the federal government will add another ~~\$9.4 trillion~~ in debt, and even this is a rather rosy scenario, as it assumes Congress will not ratchet spending up again, and the economy will not experience another recession.

During the first seven years of President Barack Obama's tenure, the national debt has increased ~~\$8.3 trillion~~ (78 percent), and stands at ~~\$19 trillion~~. That translates to nearly ~~\$71,000~~ per household, according to CNSNews.com, relying on U.S. Treasury and Census Bureau data.

9.4 teradollars

8.3 teradollars

19 teradollars


71 kilodollars

Prelude: 3 Great Forces

- **Nuclear** Strong, very short (subatomic) distances ...
- **Electrostatic** Holds all kinds of stuff together in the everyday world
- **Gravitational** Weakest, but impressive over very large distances
and with large masses


Electrostatic Forces

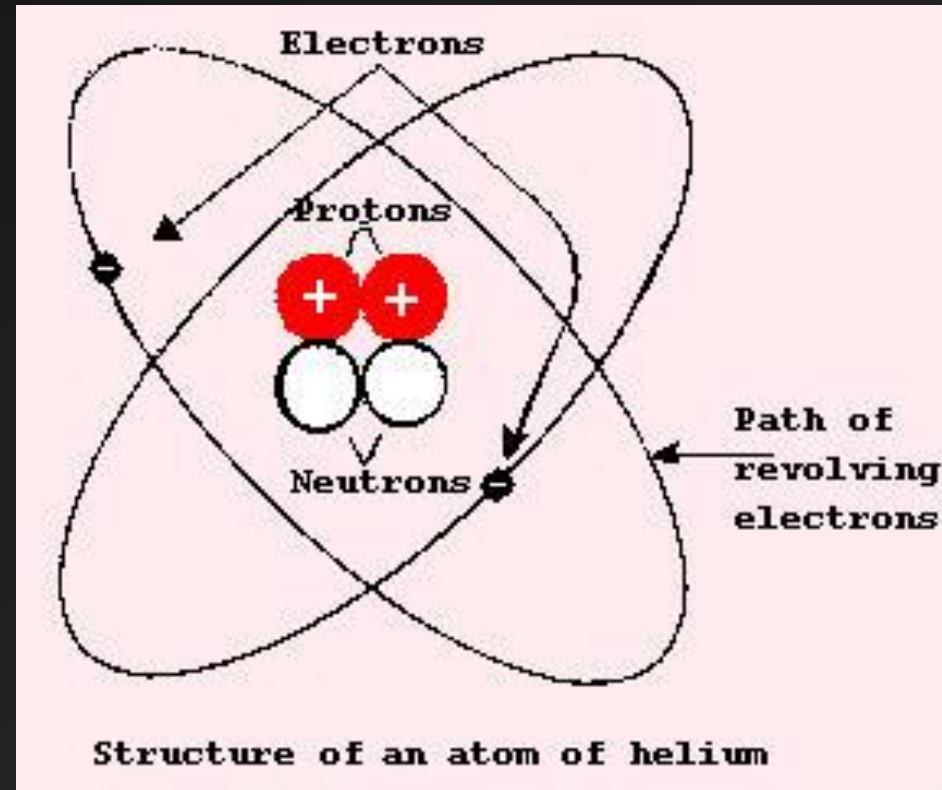- Due to charged subatomic particles
 - Proton
 - Electron
 - but not Neutron
- The Law:
 - Unlike Charges Attract
 - Like Charges Repel



Free Electrons


➤ Some electrons can be easily displaced

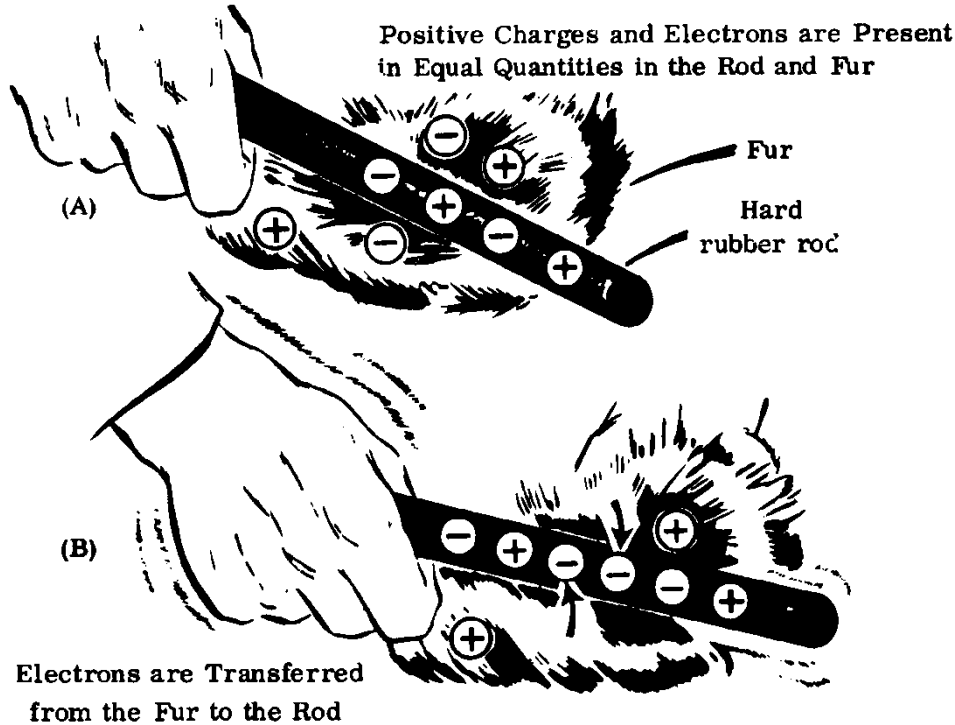


Static Electricity

- Friction with Poor Conductors
- Electrons displaced from one substance to the other (e.g Hair to comb, carpet to body)
- Leads to voltage potential (i.e., difference)

Basic Electricity by Analogy

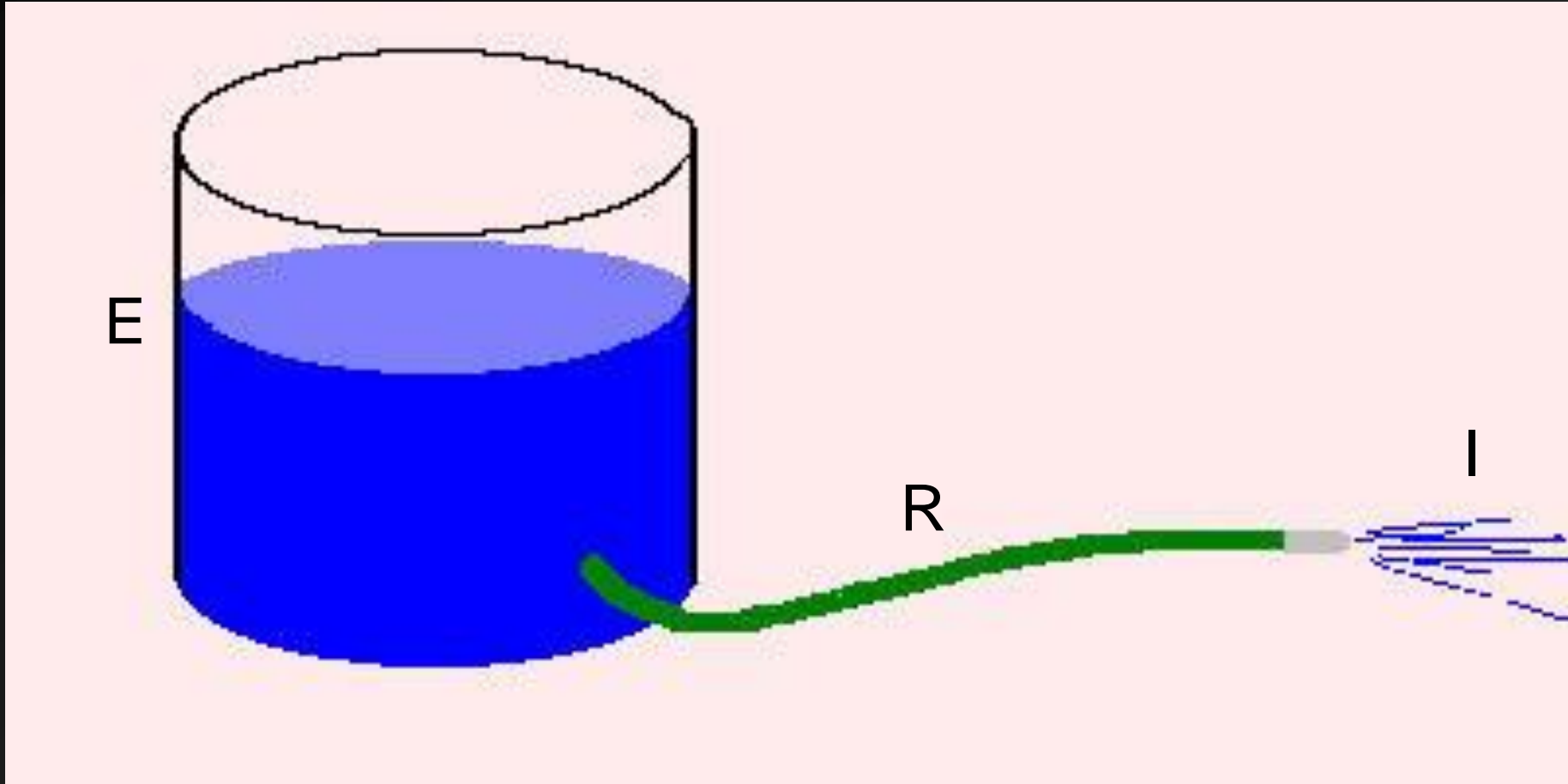

← Direction of Electron Movement

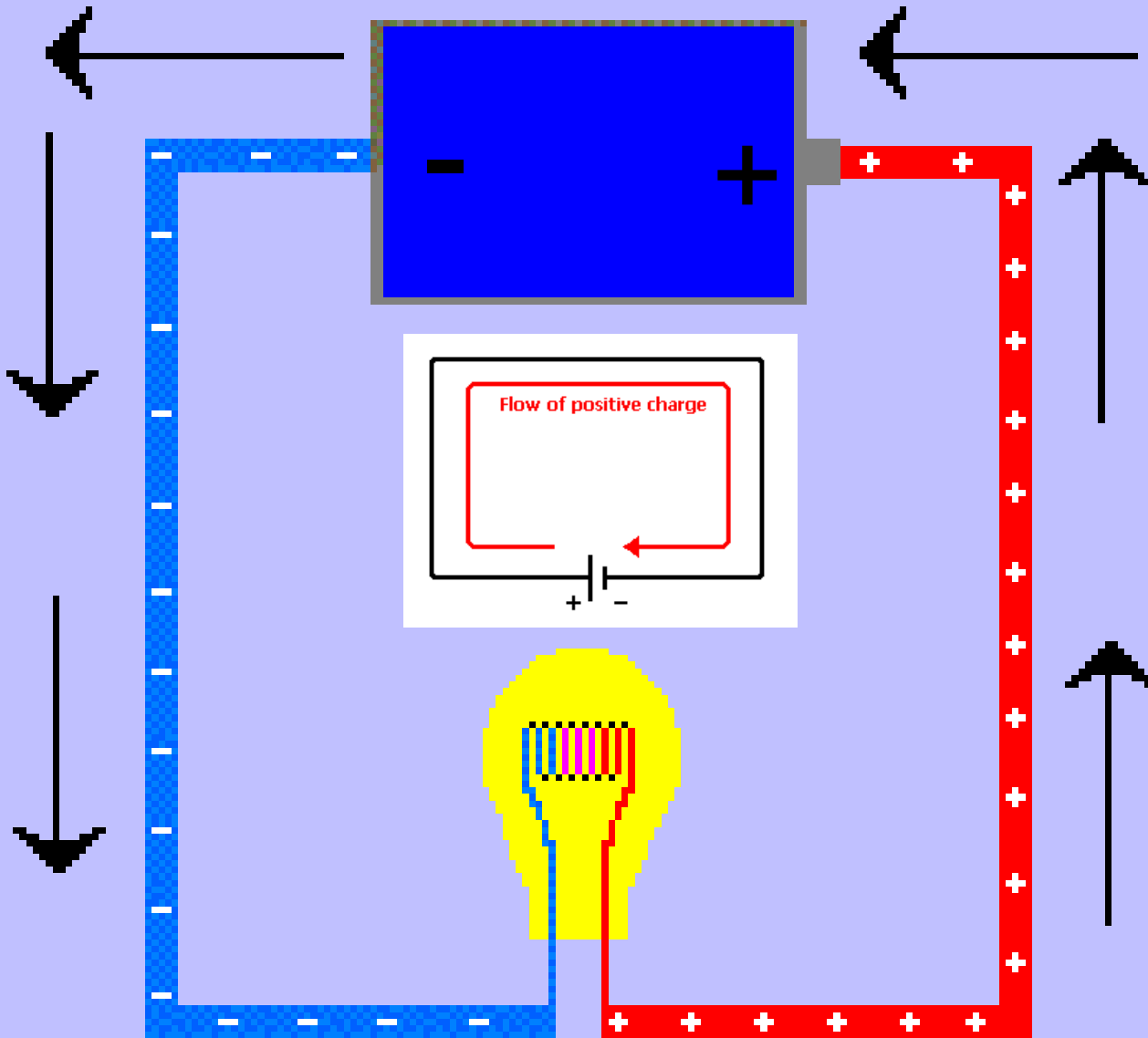

DC
Anyway!

Details Details


Symbol	Term	aka	Unit
E	Voltage	Electromotive Force	Volts (V)
I	Current	Rate of Flow	Amperes (A)
R	Resistance	--	Ohm (Ω)
P	Power	Rate of work	Watt (w)
W	Energy	Ability to do work	Watt-Second (Joule)

Ohm's Law

$$I = \frac{E}{R}$$

$$E = IR$$

$$R = \frac{E}{I}$$

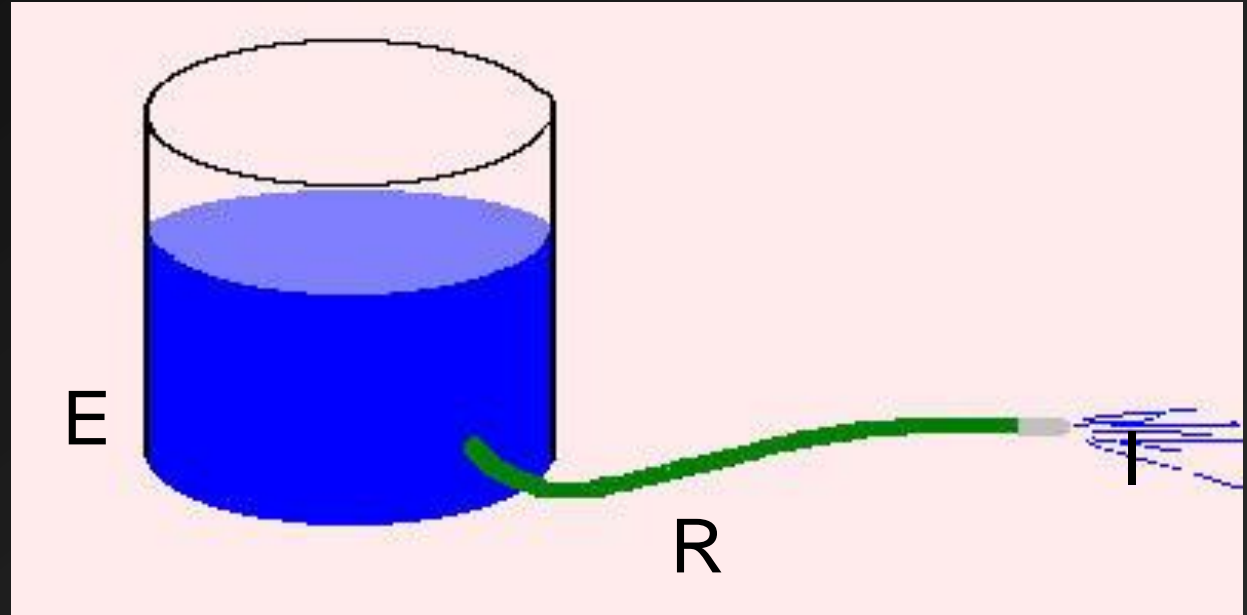


See also: <http://www.falstad.com/circuit/e-ohms.html>


Ohm's Law

$$I = \frac{E}{R}$$


$$E = IR$$

$$R = \frac{E}{I}$$

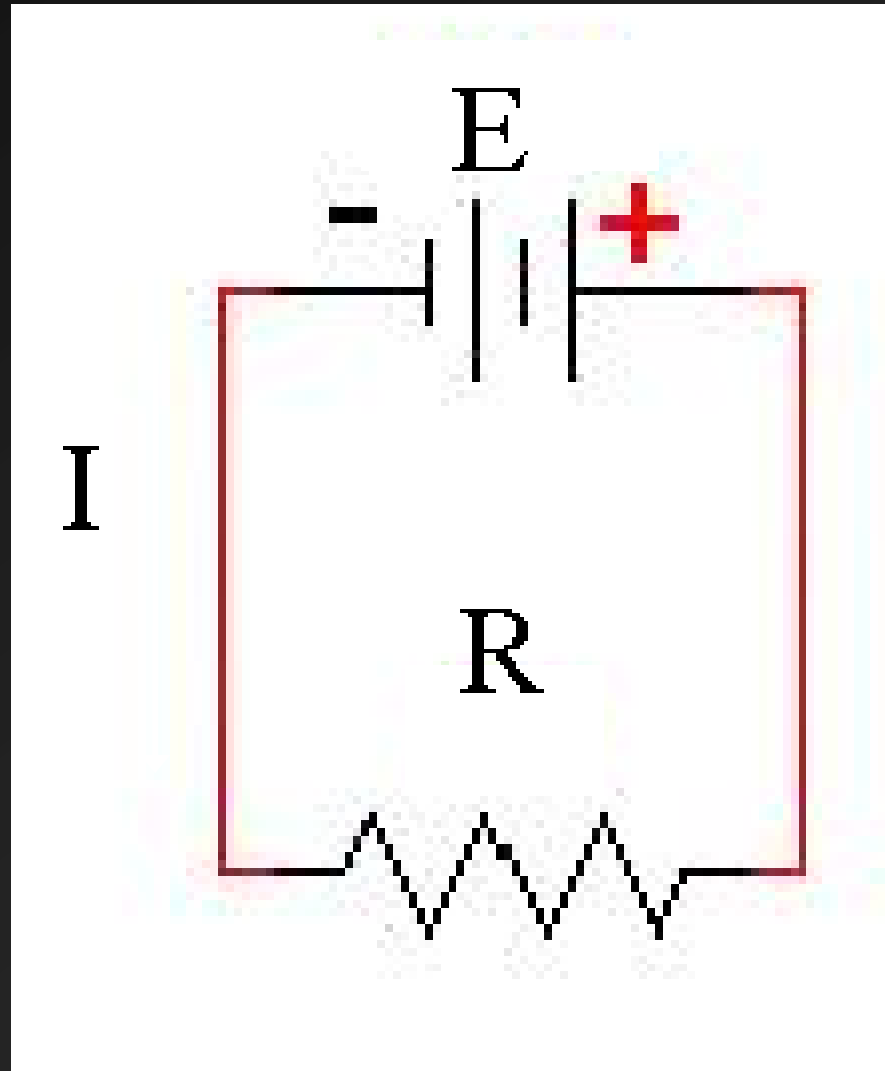

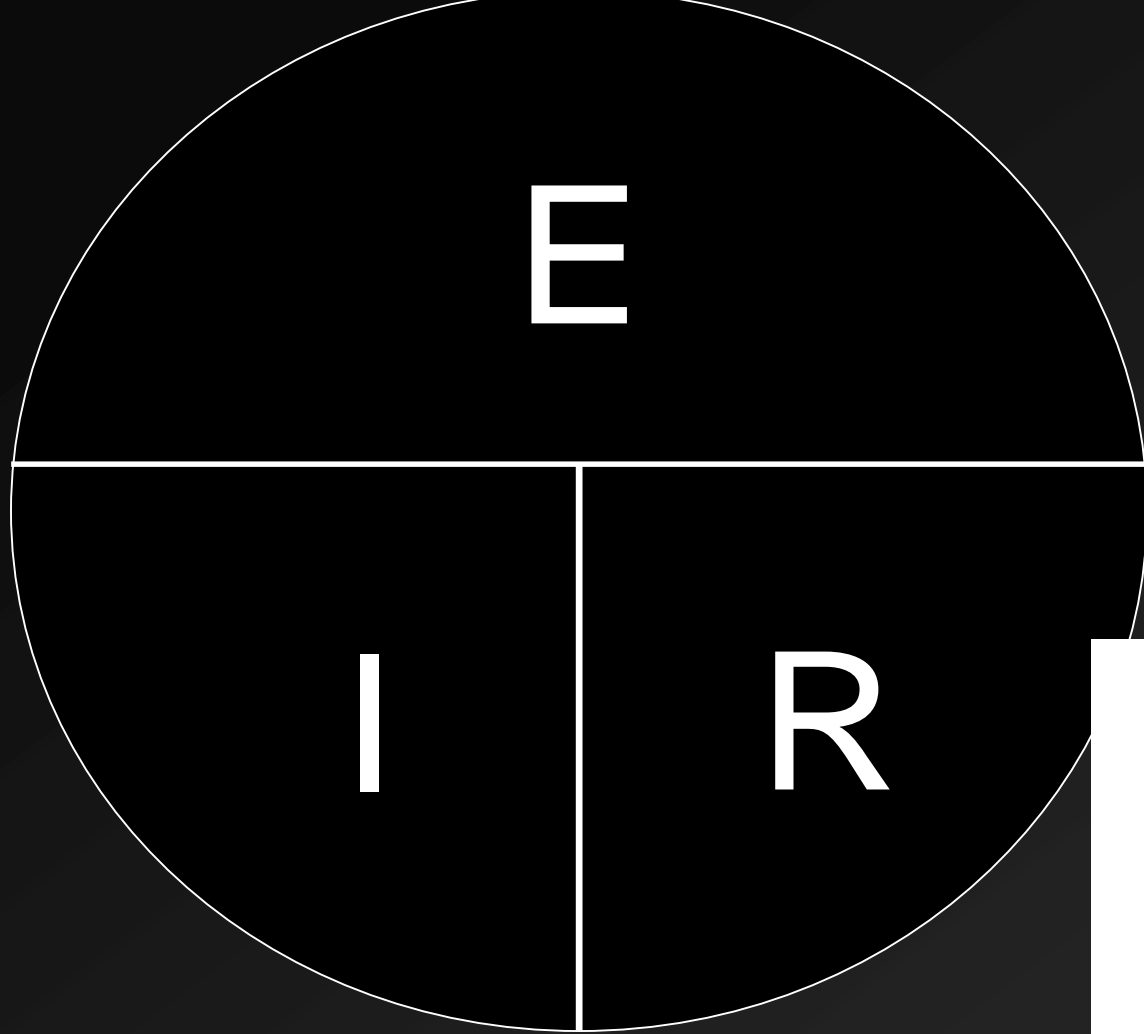

Ohm's Triangle

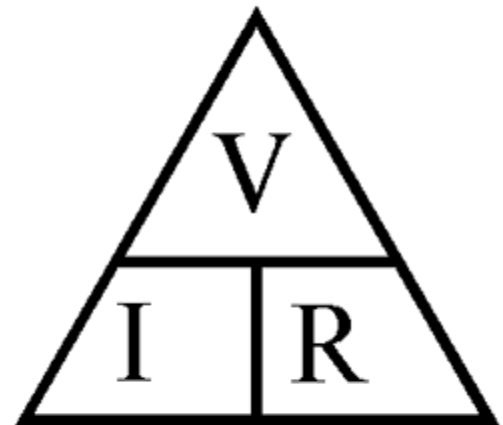

Cover the variable you want to find and perform the resulting calculation (*Multiplication/Division*) as indicated.

A black t-shirt is laid flat against a white background. The t-shirt has a crew neck and short sleeves. In the center of the chest, there is a white text design consisting of two lines of bold, sans-serif capital letters.



**RESISTANCE IS NOT FUTILE.
IT'S VOLTAGE DIVIDED BY CURRENT.**

Why are we talking about this stuff?

- We will be recording electrical signals!
- Spoiler alert: Neurons communicate using electrical principles
- Lab Safety




Basic Circuit

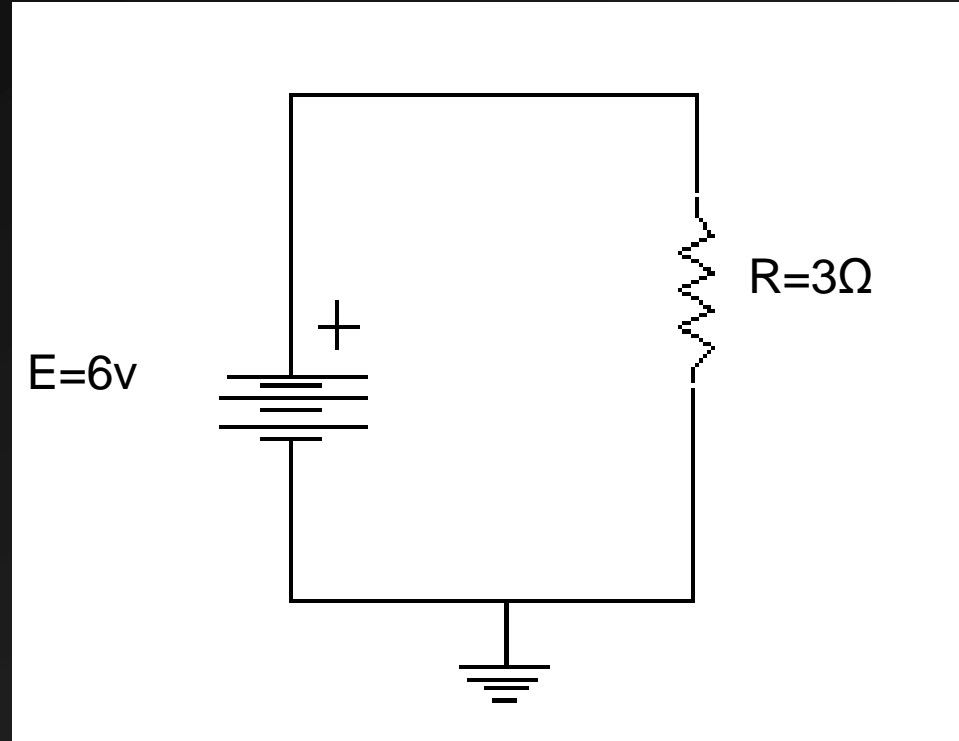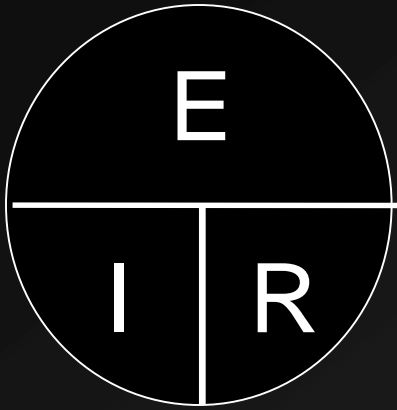

$$I = ?$$

Volt-Ohm Meter Demo

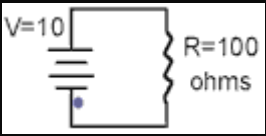


Series Circuit

$$R_T = R_1 + R_2$$


$$I = ?$$

$$E_{R1} = ?$$


$$E_{R2} = ?$$

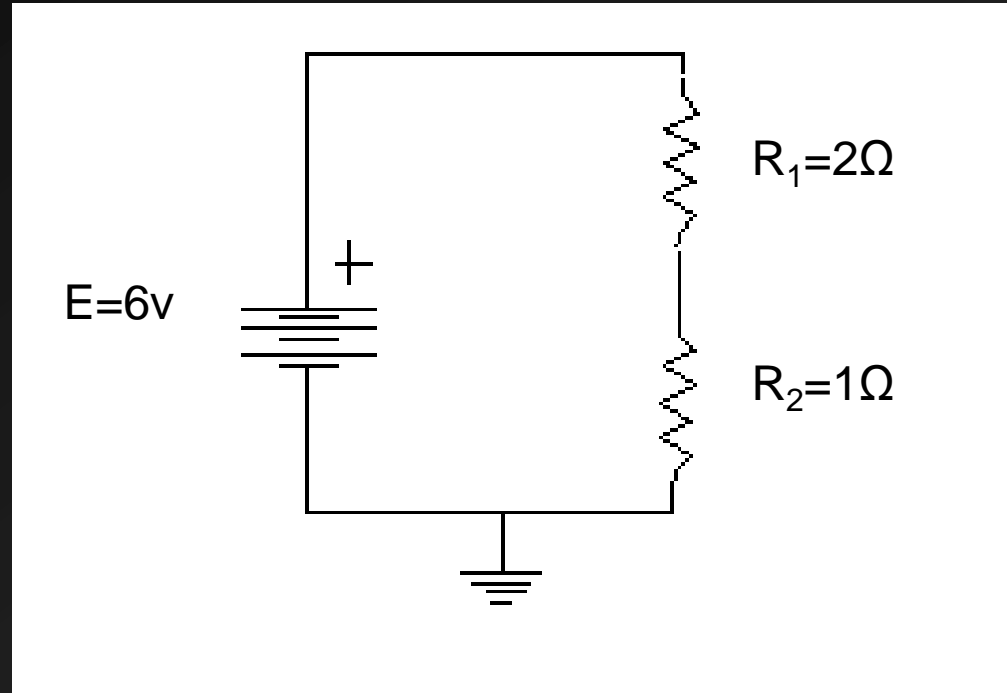


By Analogy: Series Vs Parallel

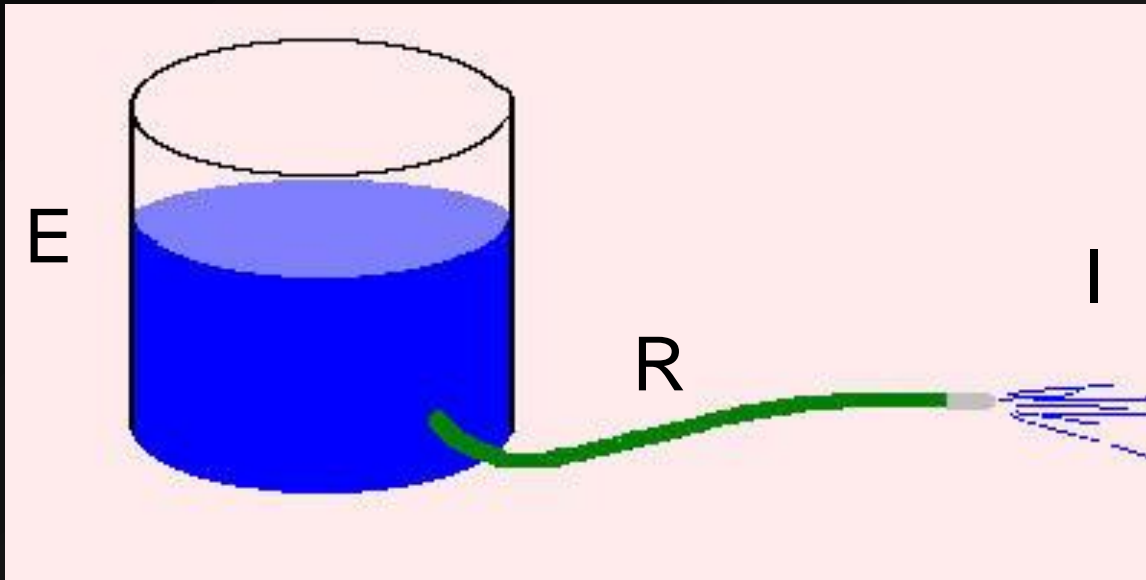
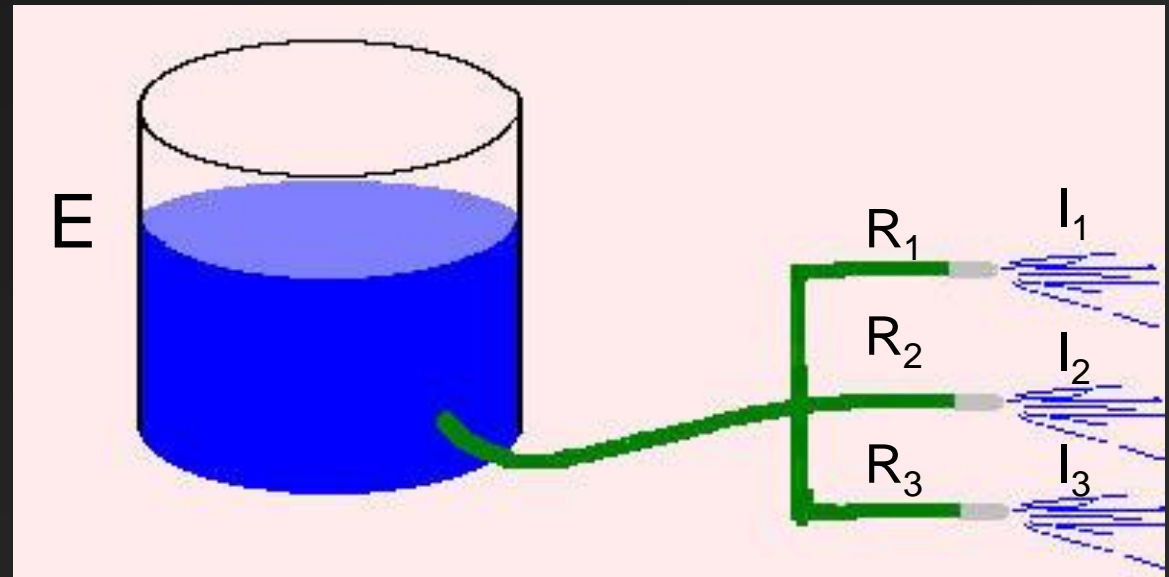
$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$



Parallel Circuit

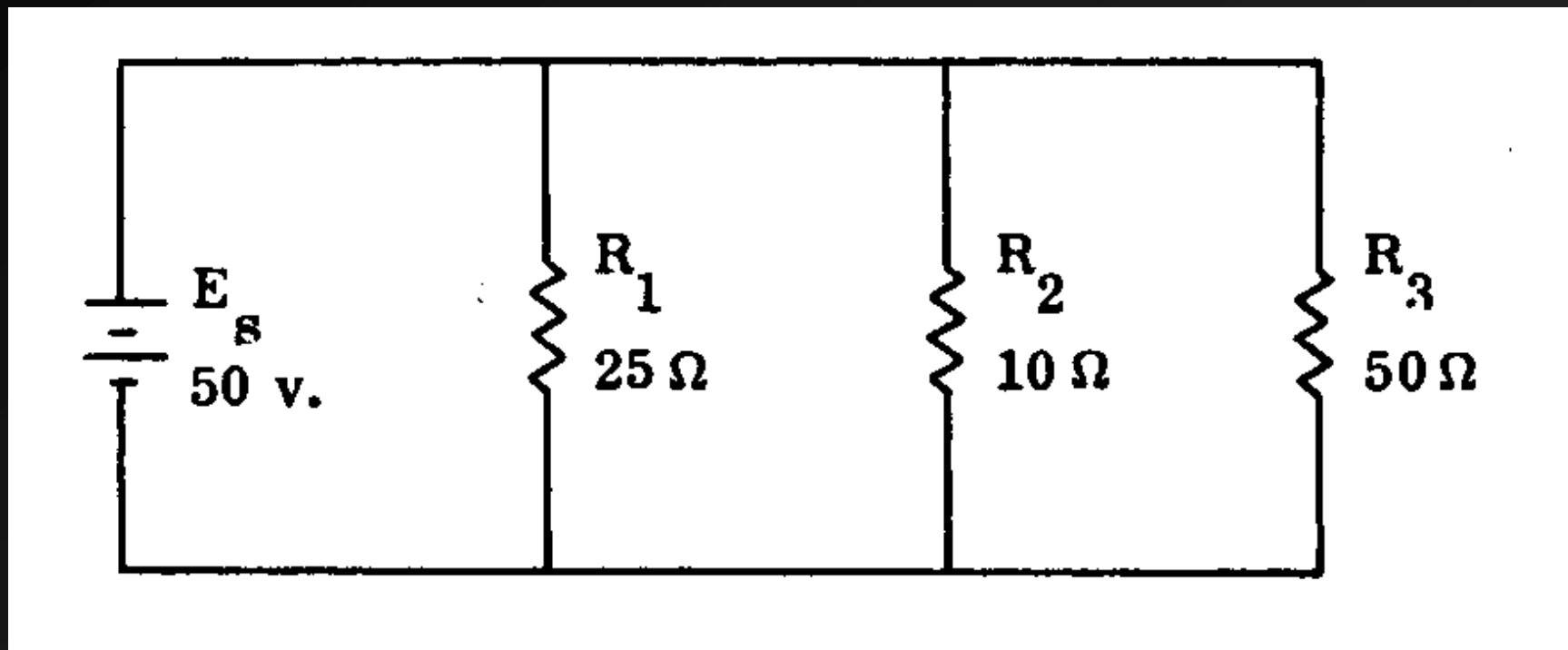

$$R_T = ?$$

$$I_1 = ?$$


$$I_3 = ?$$

$$I_T = ?$$

$$I_2 = ?$$

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

Complex Circuits

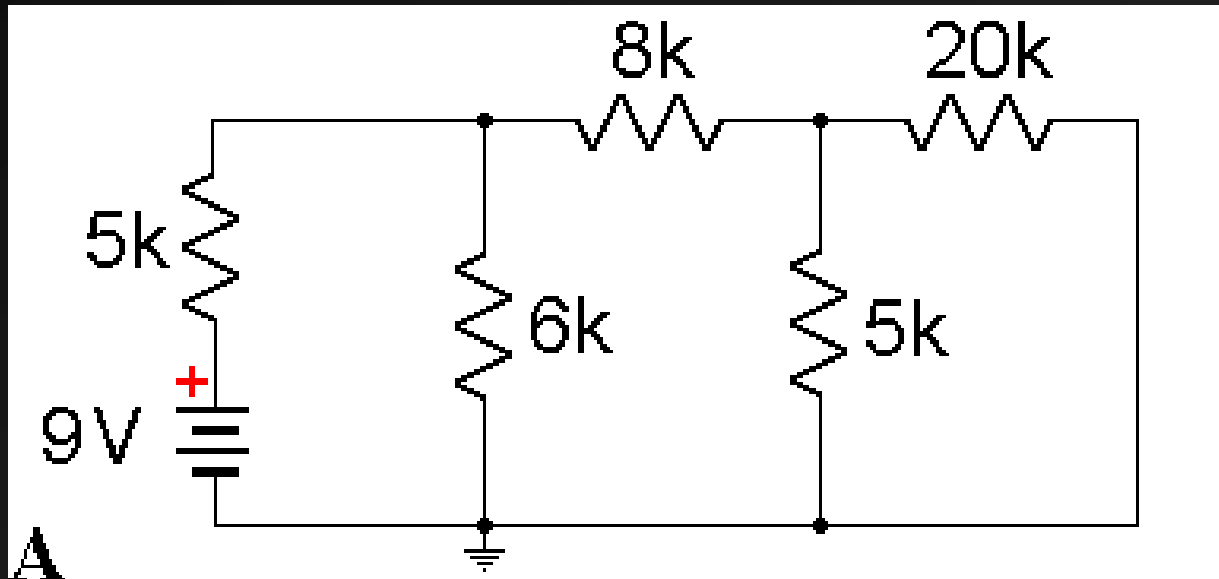

Find the current flowing in the circuit, and the voltage drops.


YIKES! Need to reduce. Start at the parallel combination of 20k and 5k resistors; it is replaced with its effective resistance of 4k

$$[1/R_{\text{equiv}} = 1/20 + 1/5 = 1/20 + 4/20 = 5/20 = 1/4].$$

This and subsequent slides on this circuit adapted from:

"<http://www.physics.udel.edu/~watson/phys345/examples/effective-circuit.html>"

Slightly less Complex Circuit

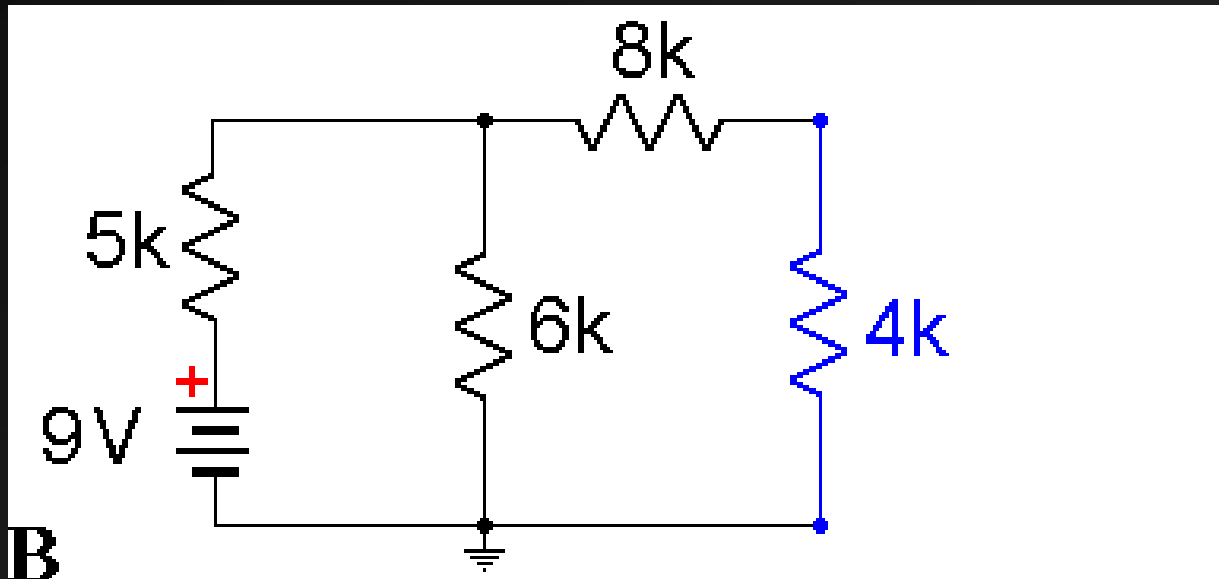


B

Looking Better. The effective resistance of 4k is in series with the actual resistance of 8k, leading to replacement by its effective resistance of 12k.

$$[R_{\text{equiv}} = 4k + 8k]$$


Less Complex Still

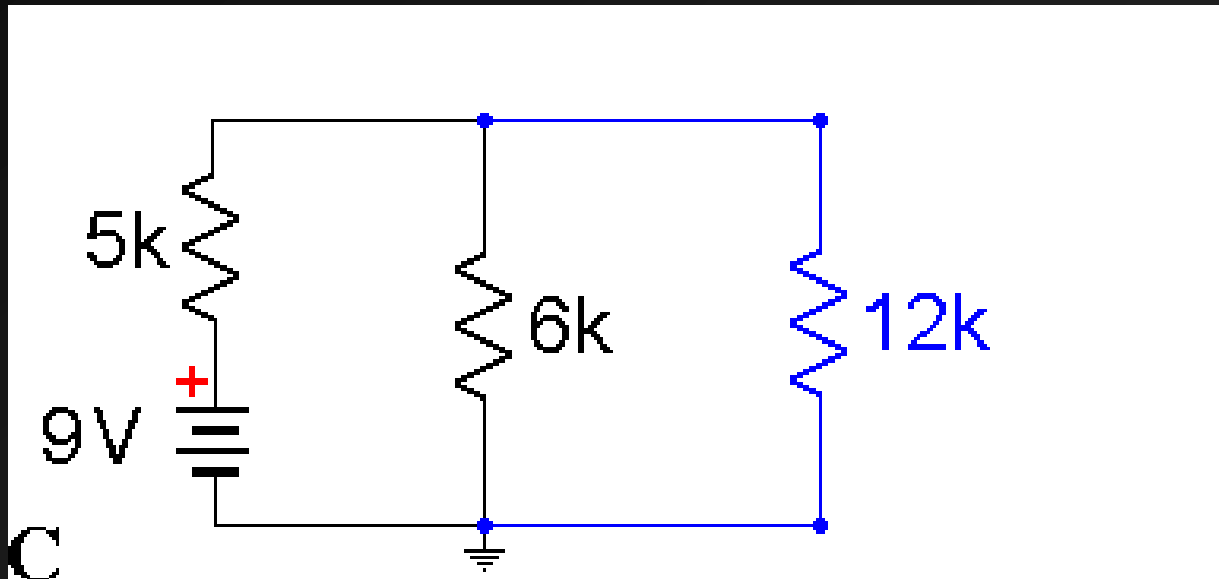

Better Still. Now there is a parallel combination of 12k and 6k resistors; it is replaced with its effective resistance of 4k

$$[1/R_{\text{equiv}} = 1/12 + 1/6 = 1/12 + 2/12 = 3/12 = 1/4].$$

Now Series: Almost Simple

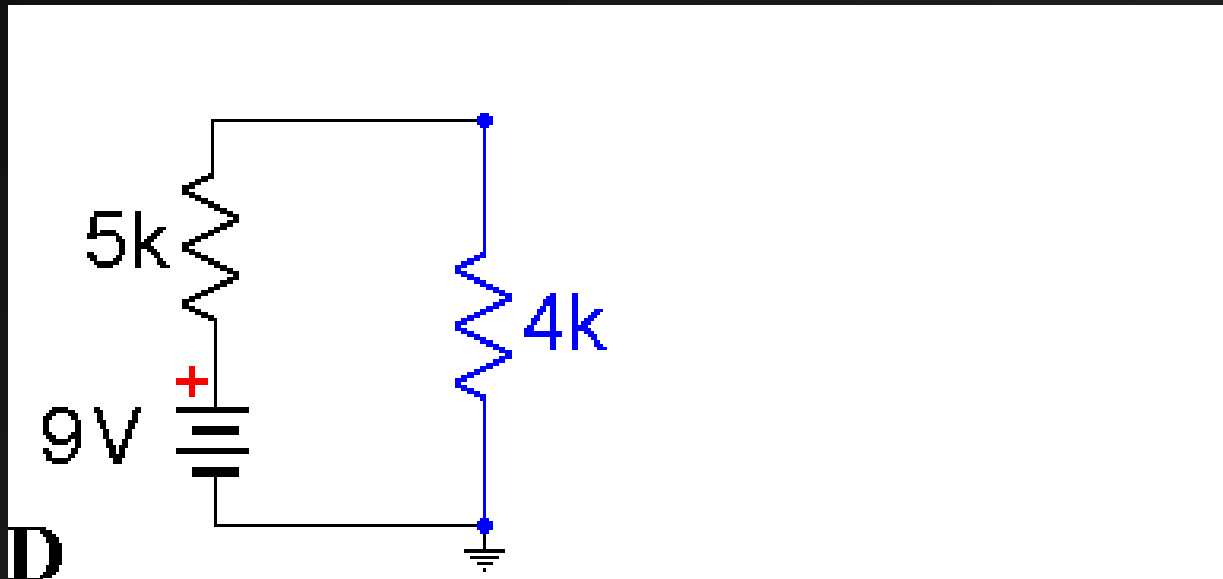


Now we have a simple series circuit!

Finally, the equivalent resistance for the entire circuit is 9k.

$$[R_{\text{equiv}} = 4k + 5k].$$


Now Series: Almost Simple

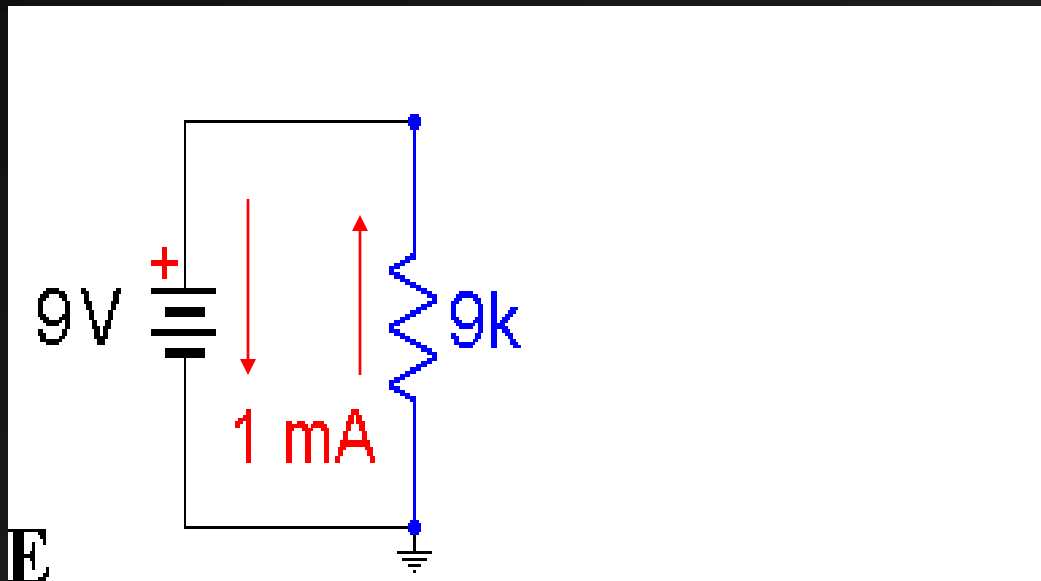

$I = ?$


$$[I = E/R = 9 \text{ V}/9 \text{ k} = 1 \text{ mA}]$$

Working Back: Voltage Drops and Current

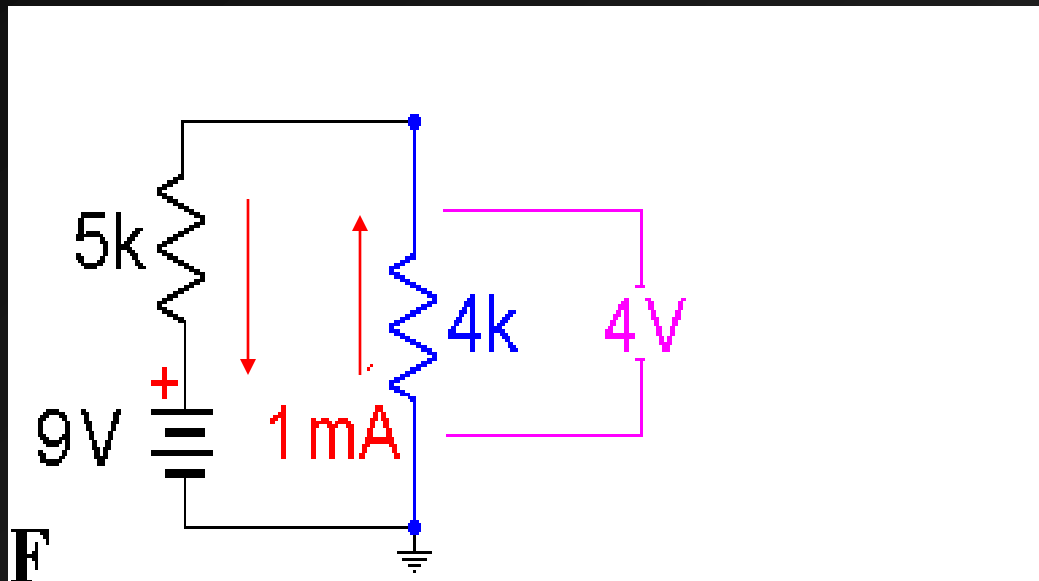

The real 5k resistor and the effective 4k resistance each have 1 mA of current since they are in series. Thus the 4k resistance has 4V of voltage difference across it (by Ohm's law).

Working Back: Voltage Drops and Current

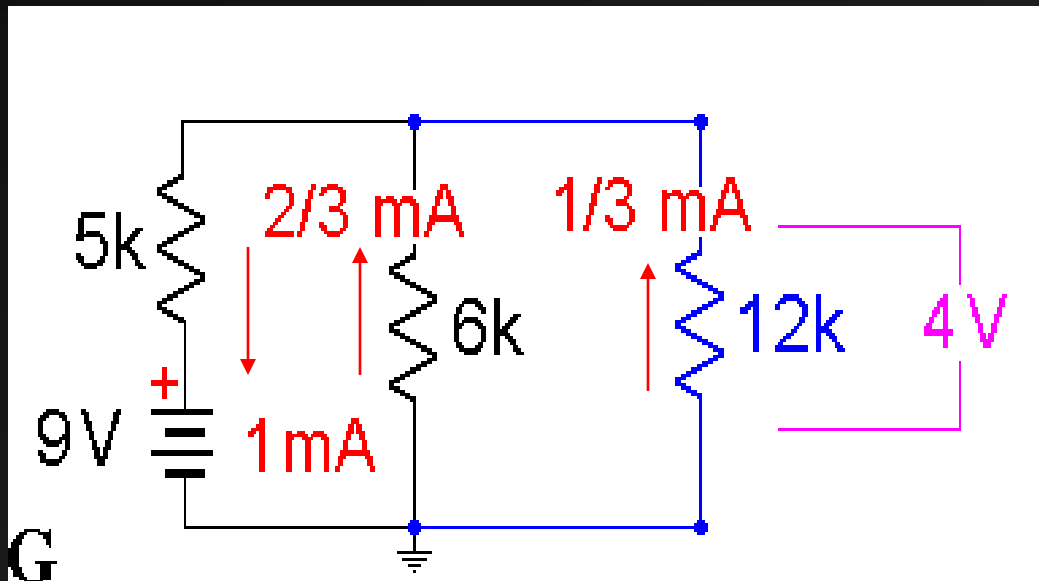


Breaking the 4k resistance into its component parts (in parallel), we find that 2/3 mA of current flows in the 6k resistor and 1/3 mA flows in the effective resistance of 12k.

$$I = E/R = 4/6K = 2/3 \text{ mA}$$

$$I = E/R = 4/12K = 1/3 \text{ mA}$$

Working Back: Voltage Drops and Current

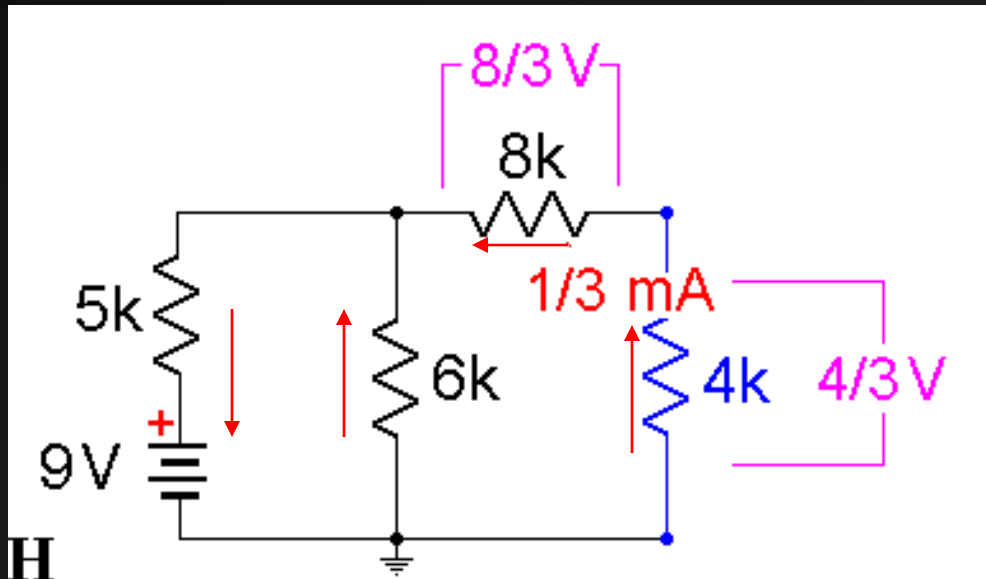


Breaking the 12k resistance into its component parts (in series), we find that there is $8/3 \text{ V}$ across the 8k resistor and $4/3 \text{ V}$ across the effective resistance of 4k.

$$E = IR = 4\text{K}\Omega * 1/3 \text{ mA} = 4/3 \text{ V}$$

$$E = IR = 8\text{K}\Omega * 1/3 \text{ mA} = 8/3 \text{ V}$$

Working Back: Voltage Drops and Current

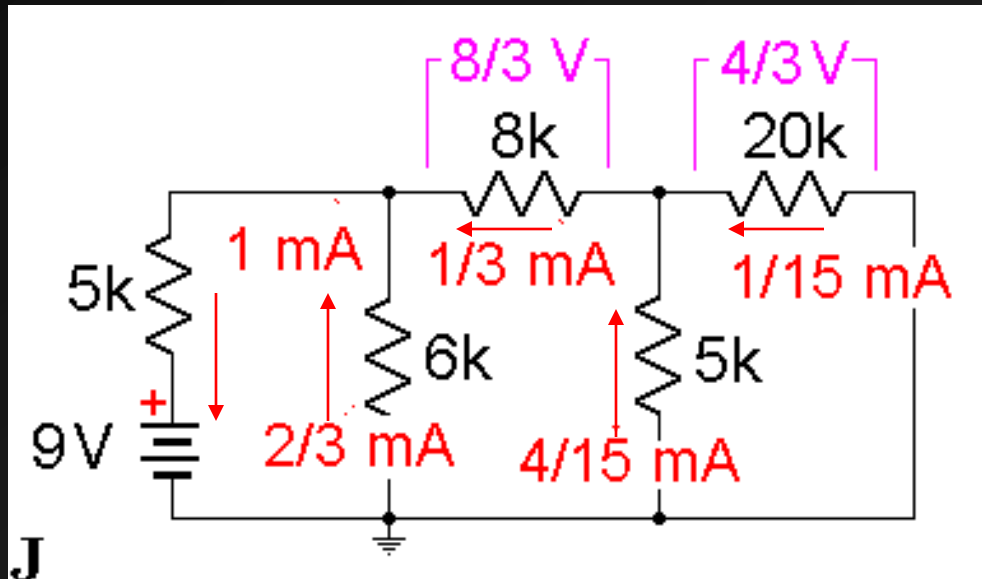


Finally, breaking the 4k resistance into its component parts (in parallel), we find that 1/15 mA of current flows in the 20k resistor and 4/15 mA flows in the 5k resistor.

$$I = E/R = (4/3V)/20K\Omega = 4/60 \text{ mA} = 1/15 \text{ mA}$$

$$I = E/R = (4/3V)/5K\Omega = 4/15 \text{ mA}$$

Working Back: Voltage Drops and Current

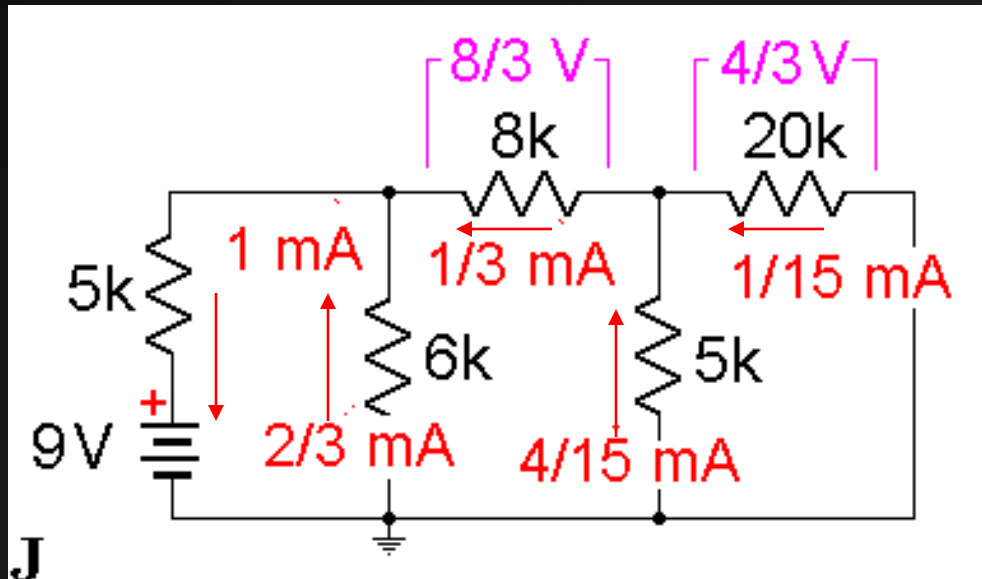


Summarizing:

- | | |
|--|--------|
| 1. Current through the battery? | 1 mA |
| 2. Current through the 8k resistor? | 1/3 mA |
| 3. Voltage difference across the 20k resistor? | 4/3 V |


In Real Life...

B. MARSHALL-GOODELL, L. TASSINARY, AND J. CACIOPPO




a) Series Circuit

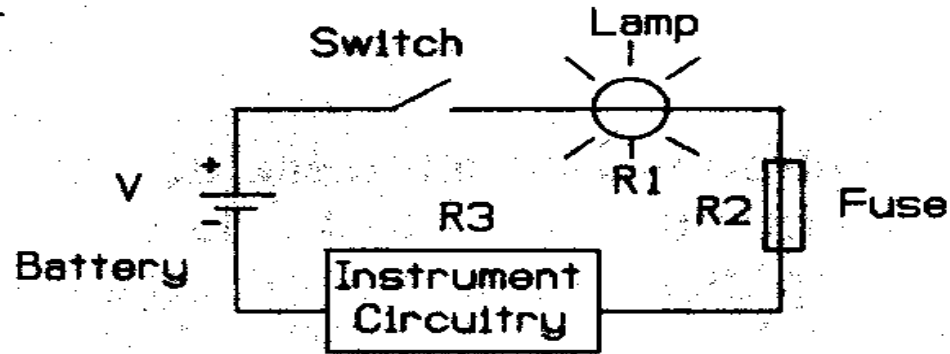

b) Parallel Circuit

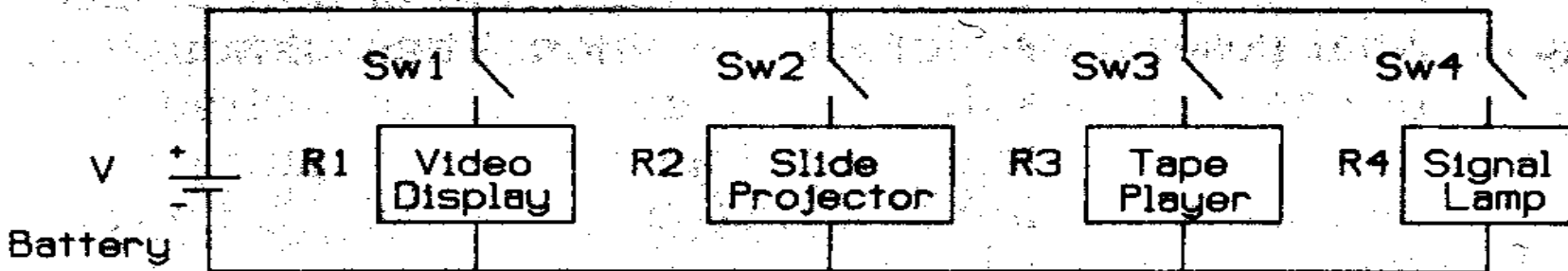

Capacitance

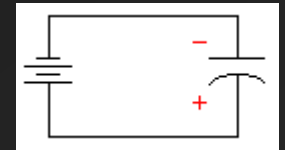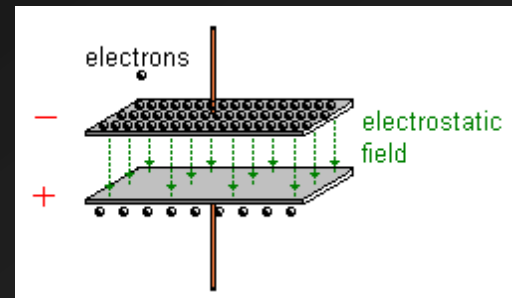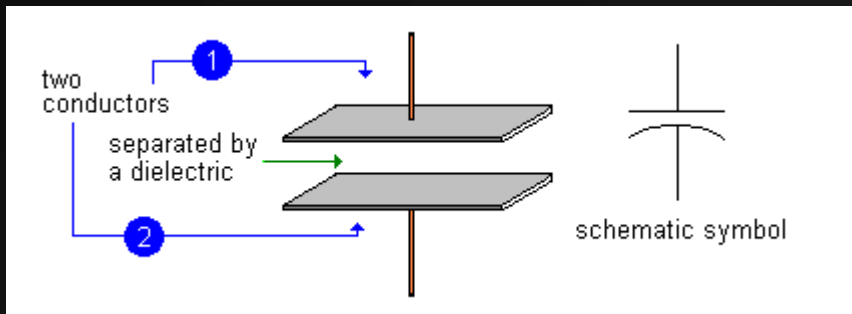

Capacitor = two conductors separated by a dielectric.

Dielectric = material that is a good insulator (incapable of passing electrical current), but is capable of passing electrical fields of force. Examples include glass, porcelain.

Charged Capacitor = more electrons on one conductor plate than on the other.


Capacitance

- Two closely spaced plates – offer essentially no resistance




- As negative charge built up on first plate due to flow of electrons, a positive charge would build up on second plate
 - The current **charges** the plates of the capacitor, **but does not flow through the capacitor**, itself.

Capacitance

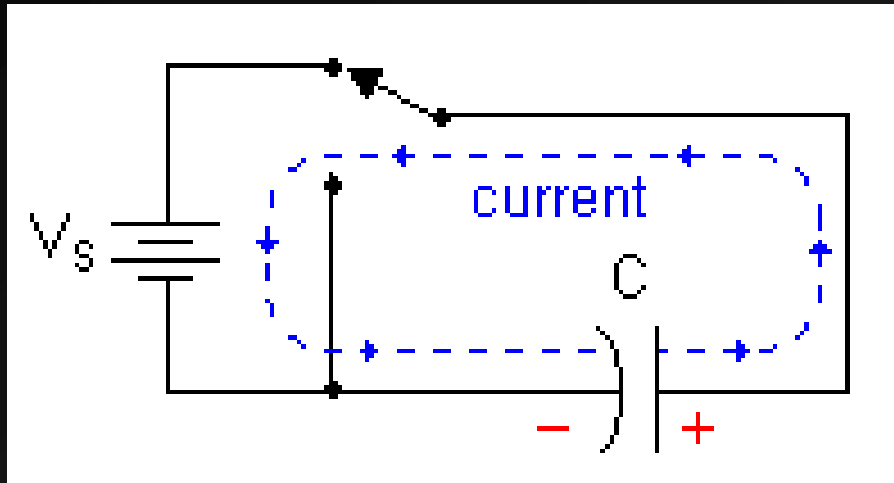

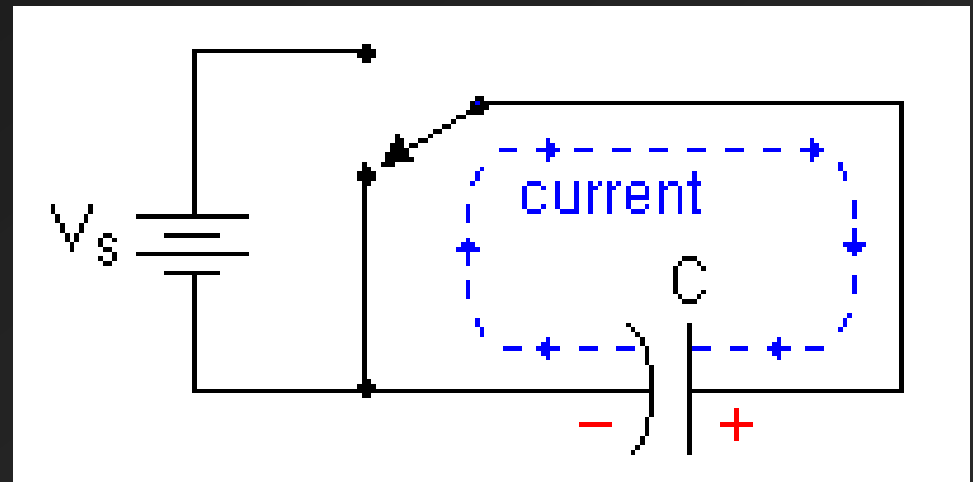Charging – current flows until capacitor is fully charged, then stops



Discharging – current flows in reverse direction until capacitor fully discharged



Capacitance – Size Matters

➤ Which has more capacity?



➤ More capacity, more current flows before capacitor is fully charged

Capacitor Time Constants

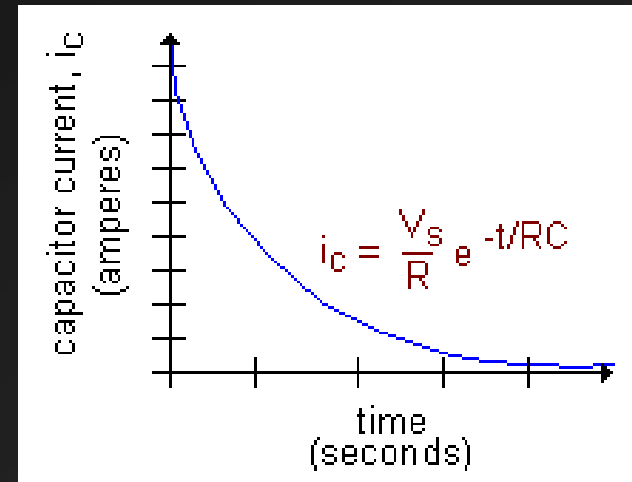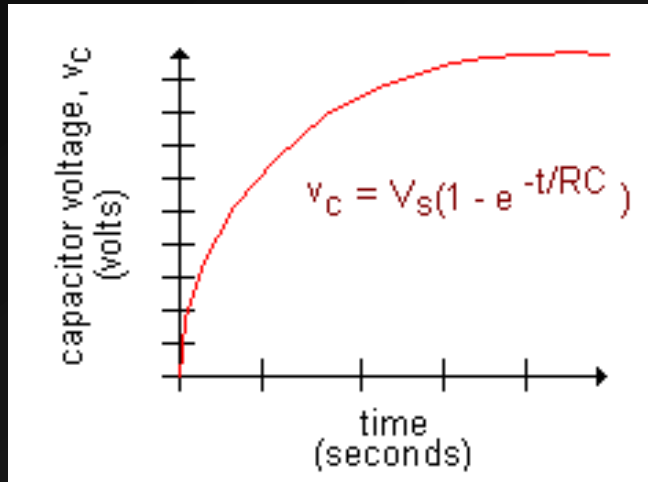

Over time...


Capacitor's voltage increases

Current flow grinds to a halt

The capacitor's time constant $TC =$

- The time in seconds for it to become 63.2% charged
- The time in seconds for current flow have slowed by 63.2% from its starting value


AC Circuits

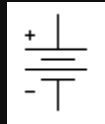

DC Circuit: Current Flow is unidirectional, from
– to +



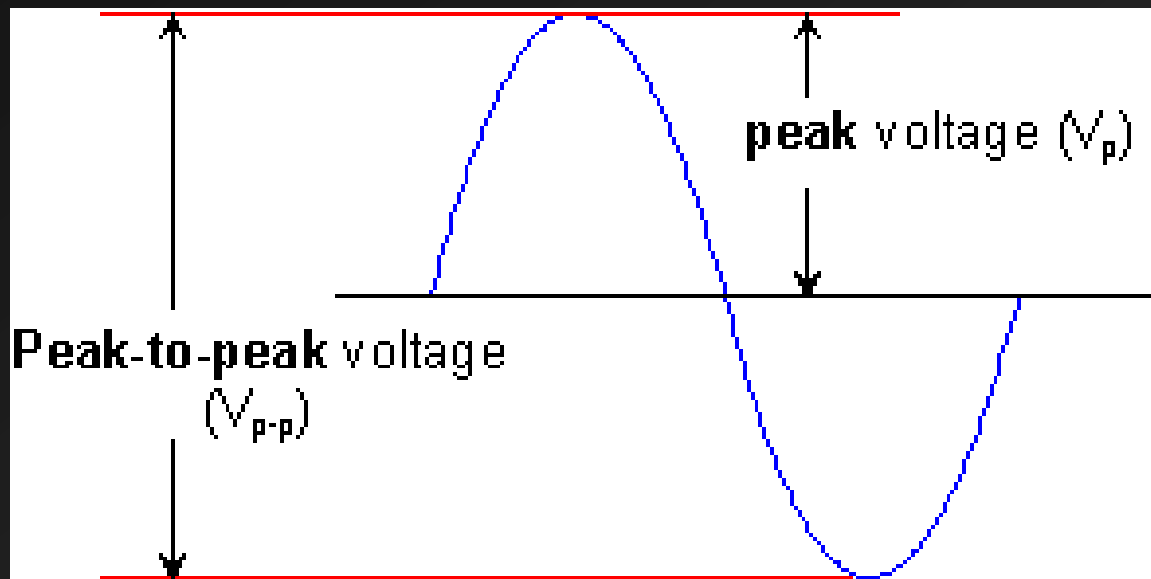AC Circuit: Current Flow switches direction
periodically (at a given frequency in Hz)



AC Circuits and Capacitance


- Slowly alternating signals
 - will fully charge capacitor, and signal will be impeded
- Rapidly alternating signals
 - will not fully charge the capacitor before the direction of flow reverses, allowing signals to pass unimpeded

<http://micro.magnet.fsu.edu/electromag/java/capacitor/>

http://www.vjc.moe.edu.sg/academics/dept/physics_dept/applet/rc/rc.htm


Backup Plan: <https://www.youtube.com/watch?v=aolH0aTnOhk>

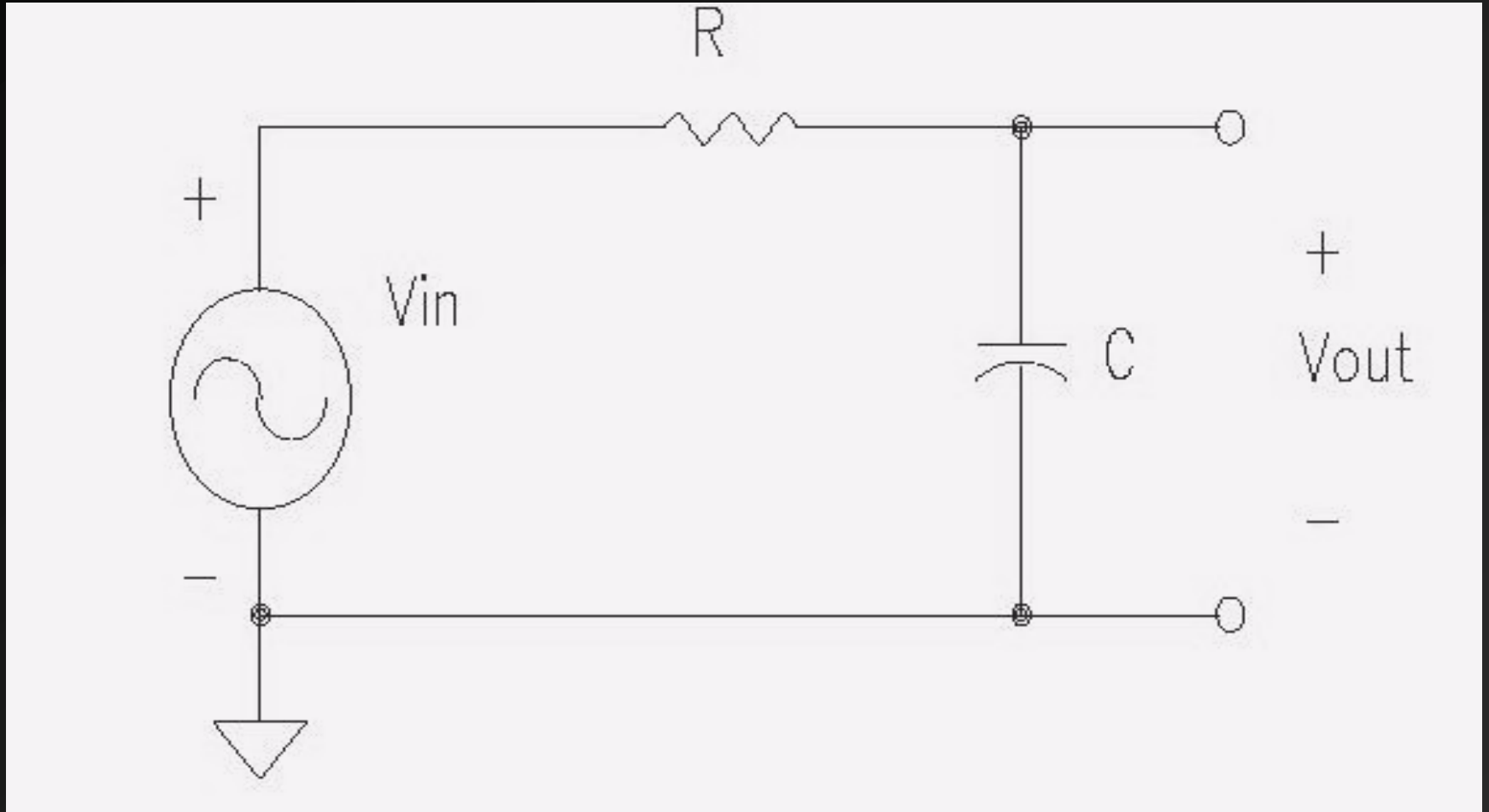Using Capacitors to make Low Pass Filters





What will happen to fast signals; slow signals?

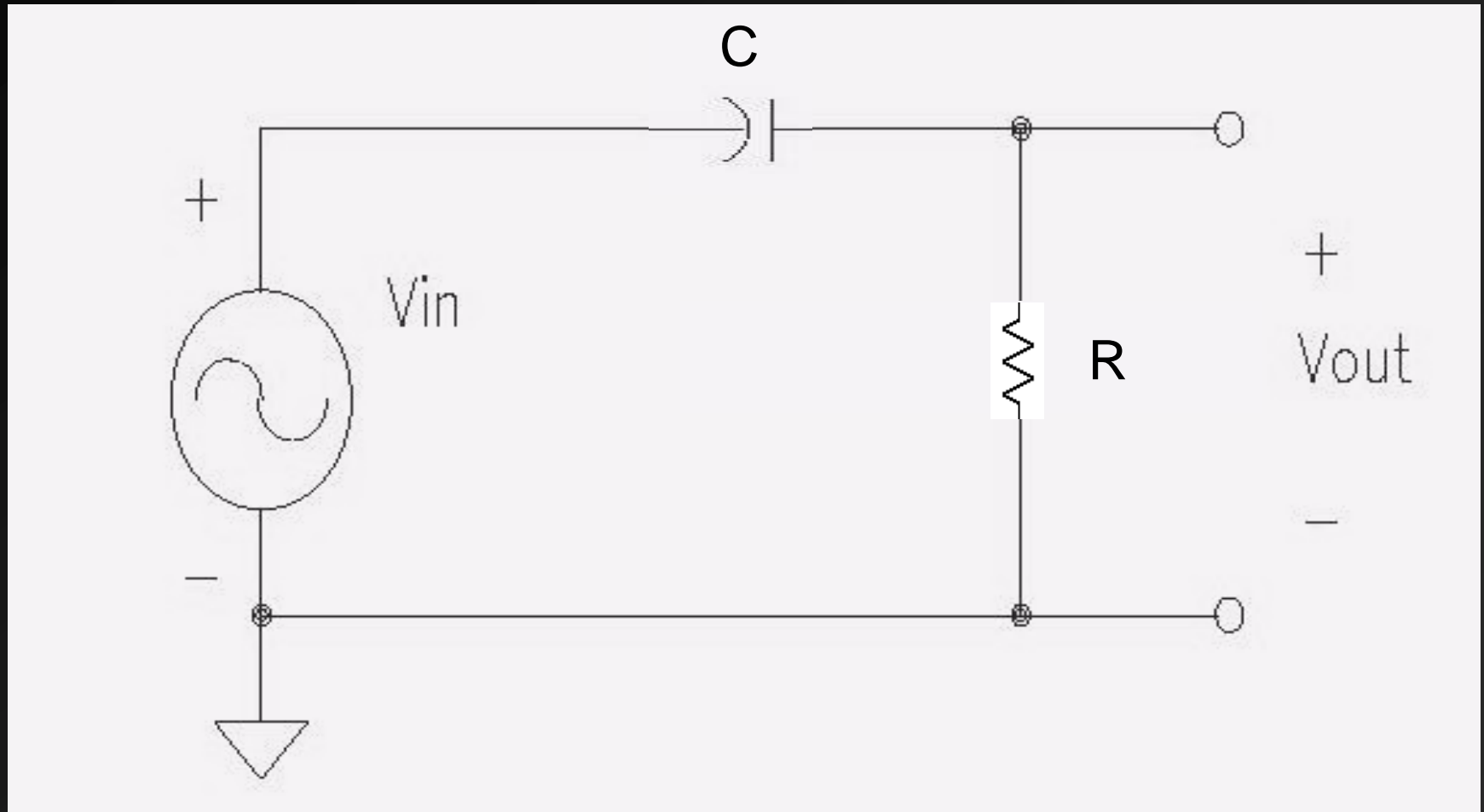Using Capacitors to make High Pass Filters




What will happen to fast signals; slow signals?

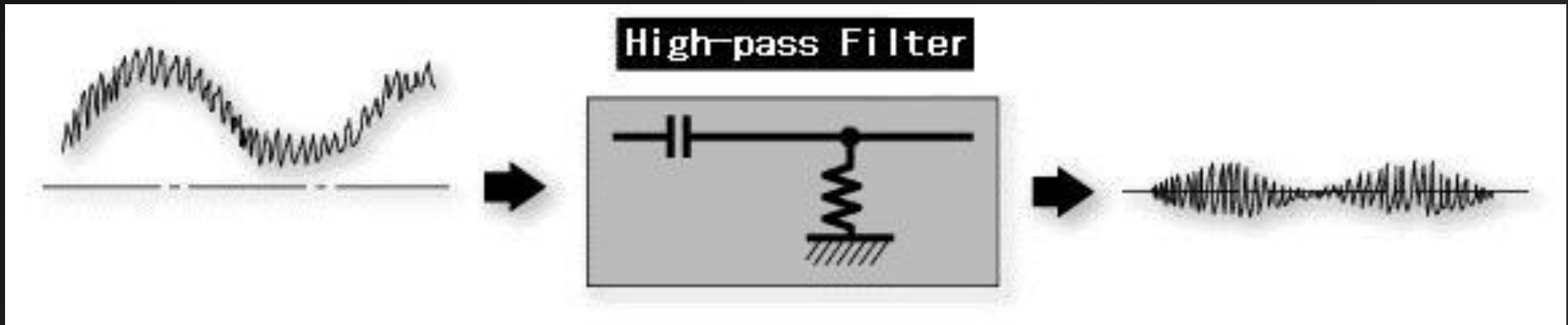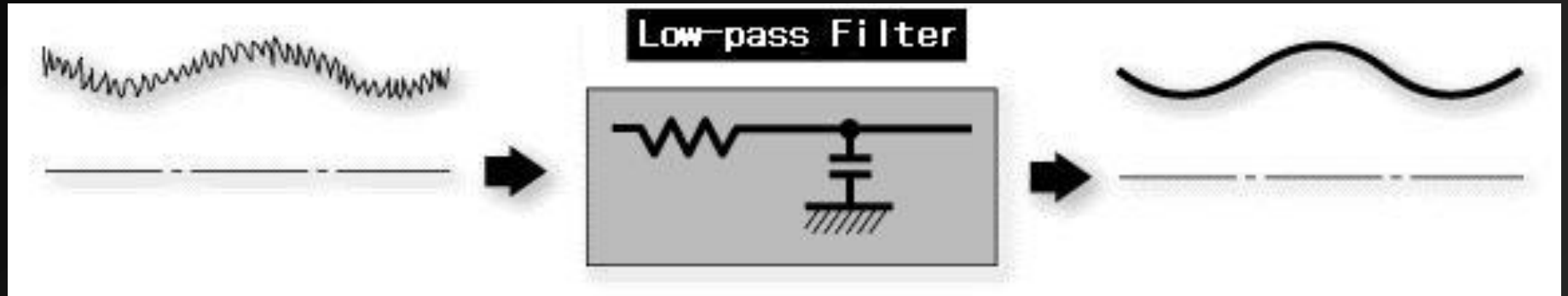

Part II: Basic Neurophysiology

- Three basic units inside the brain
 - Glial cells
 - Extracellular space: not really space
 - The neuron
 - Three types:
 - Sensory
 - Motor
 - Interneuron


Withdrawal Reflex

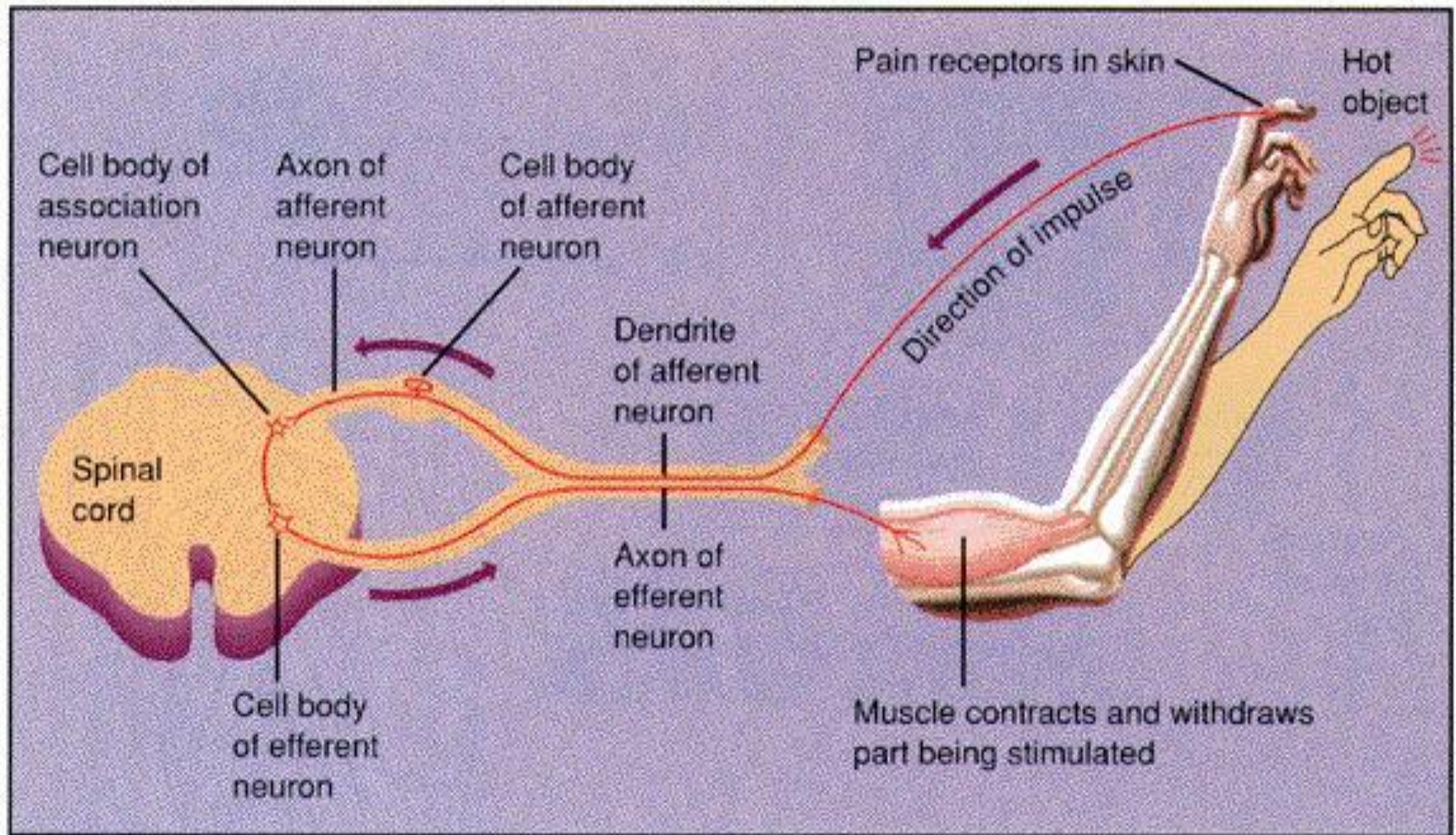


The Common Household Neuron

- Vary widely, but all have:
 - Cell body (soma)
 - Dendrites
 - Axon
 - Myelin sheath
 - Nodes of Ranvier
 - Microtubules
 - Terminal buttons (AKA synaptic knob)
- Nerve = a bundle of axons


[Jump to Next](#)

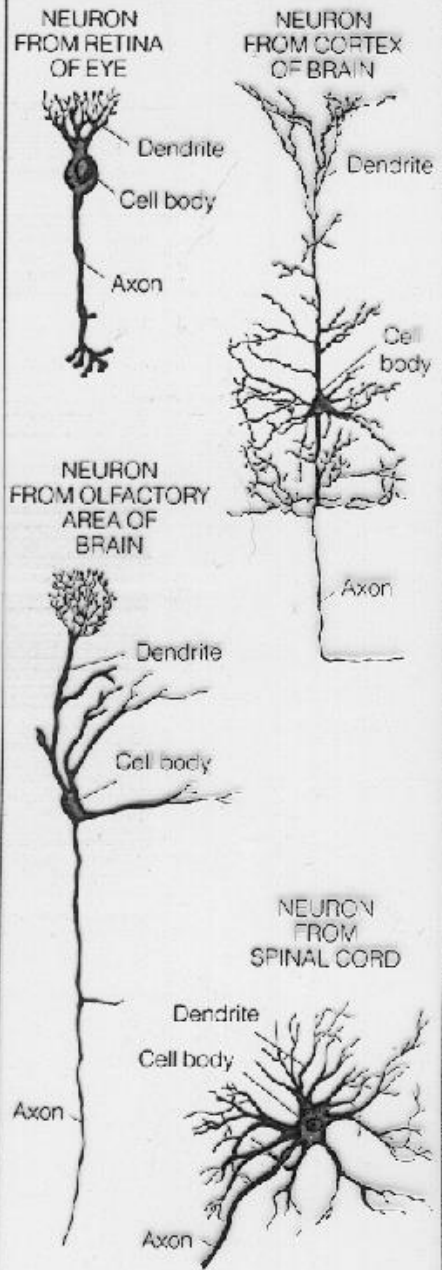


Neuron Structure

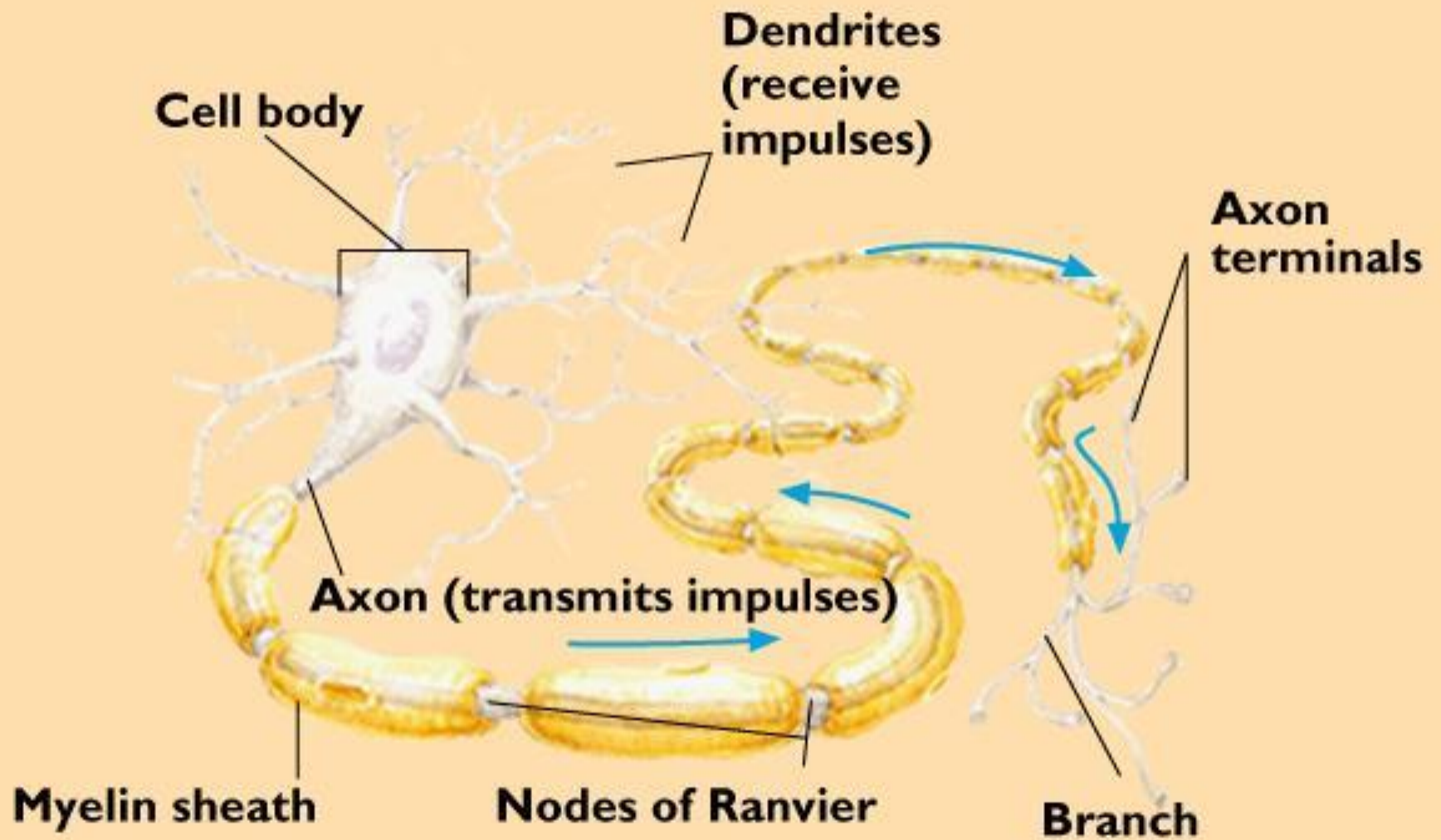

Myelin Sheath

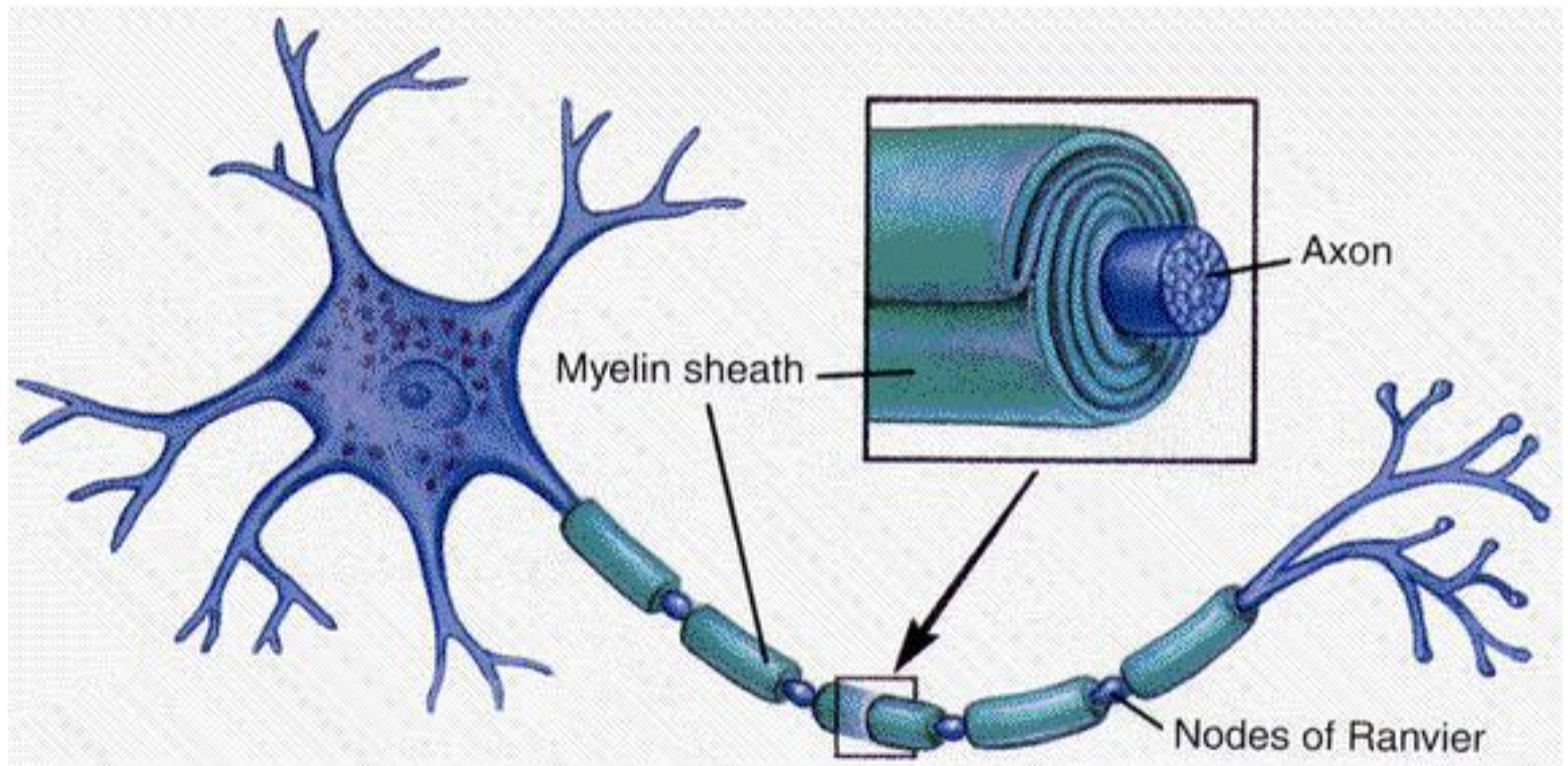

The Synapse

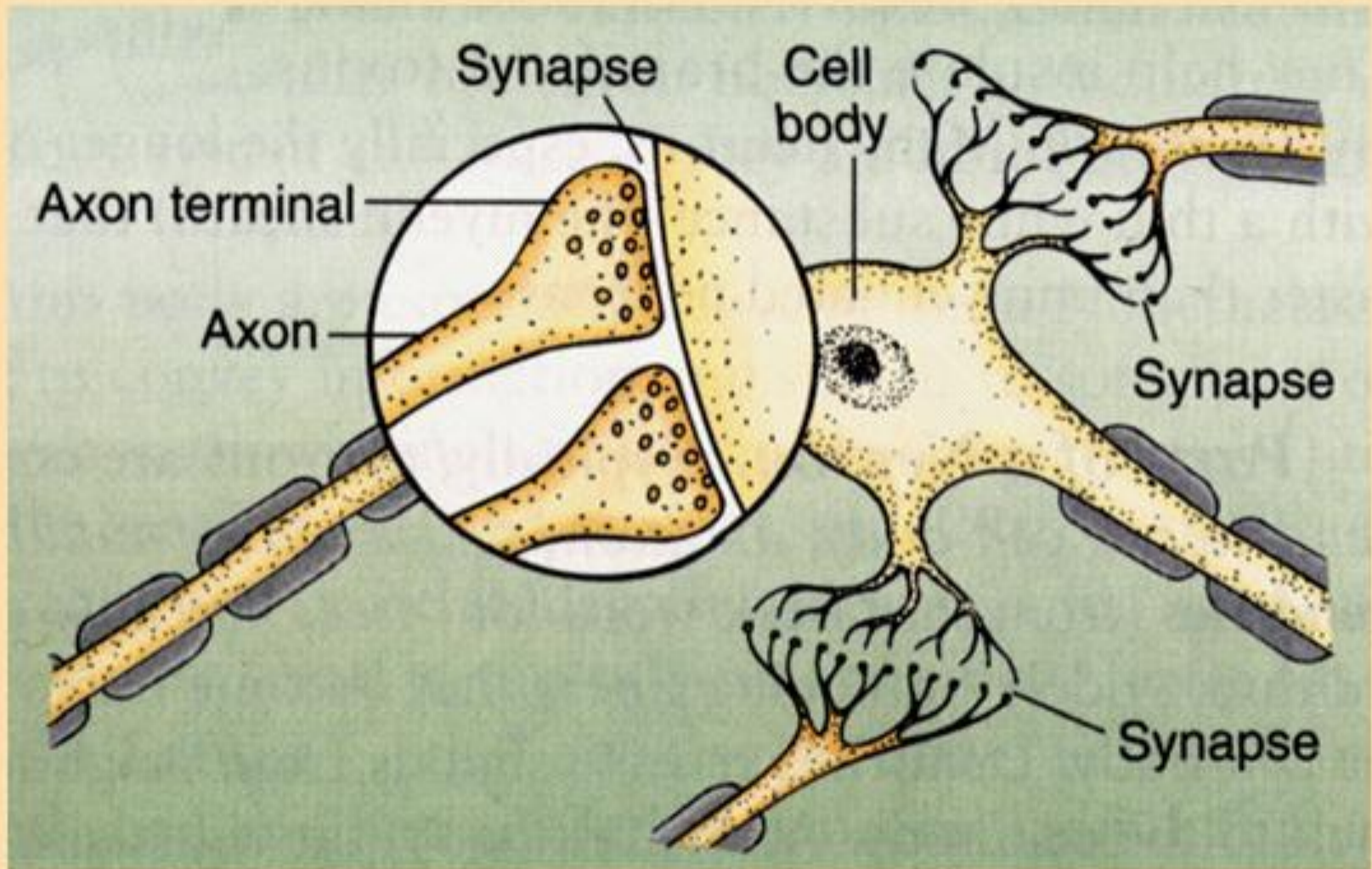

Neural Communication

- Axonal Conduction (electro-chemical)
- Synaptic Transmission (chemico-eletrical)

Axonal Conduction

➤ Resting potential

- Inside of cell slightly negative
- Two forces act upon these ions
 - Concentration gradient--osmotic force
 - Electromotive force
- Equilibrium potential:
 - $E_{ion} = (R*T/z*F) * \ln(\text{Conc}_{Ex}/\text{Conc}_{In})$
 - where R is gas constant, T is temperature, z is ionic valence, and F is Faraday's constant.

➤ The Hodgkin & Huxley Model

Axonal Conduction

➤ Depolarization

➤ Threshold

➤ Axon Hillock

➤ Na ions rush in resulting in:

➤ Action potential;

➤ All or none phenomenon, high frequency


➤ Afterpotentials; hyperpolarizing, depolarizing; slow frequency

➤ Changes in membrane permeabilities

➤ Propagation

➤ Refractory period

[Jump to Next](#)

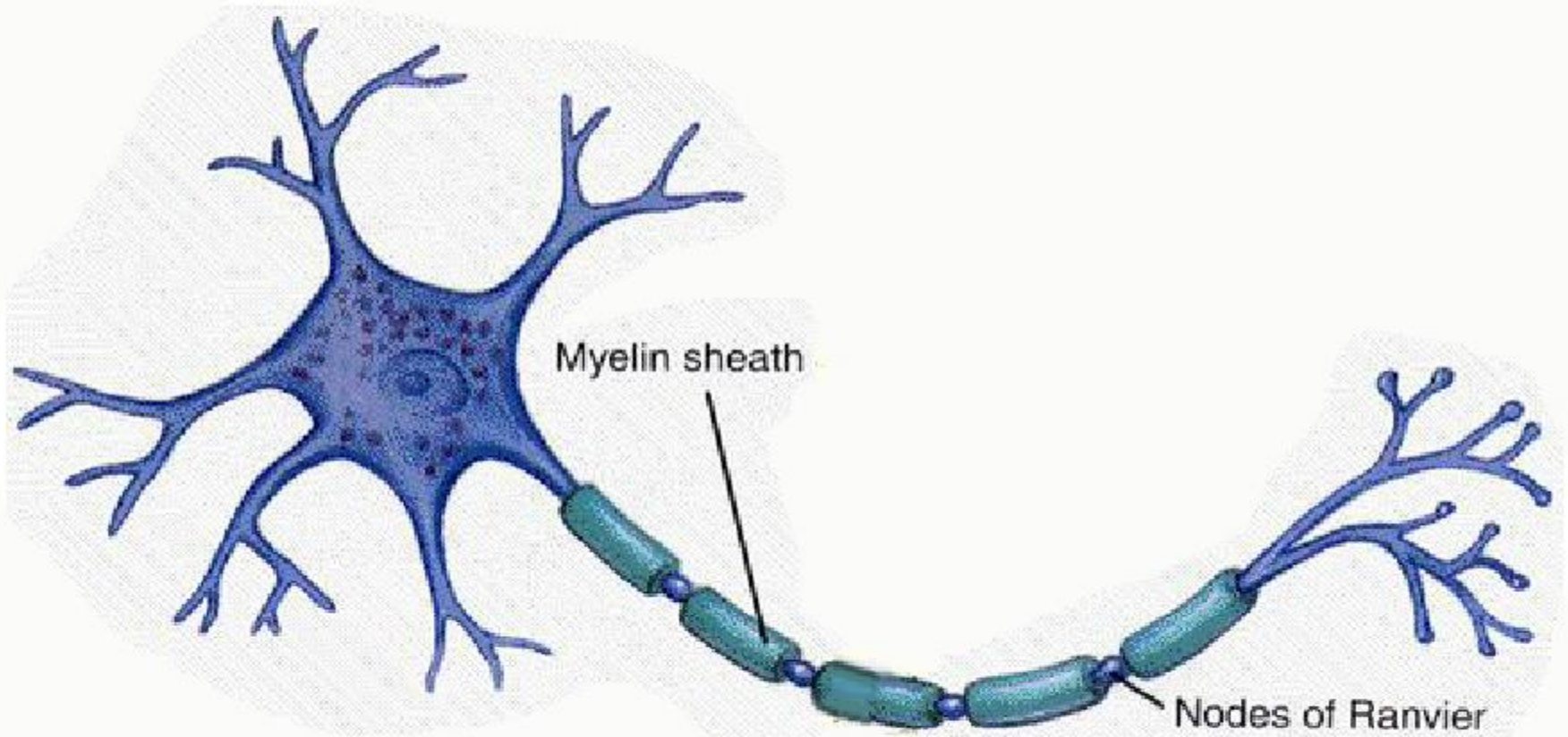




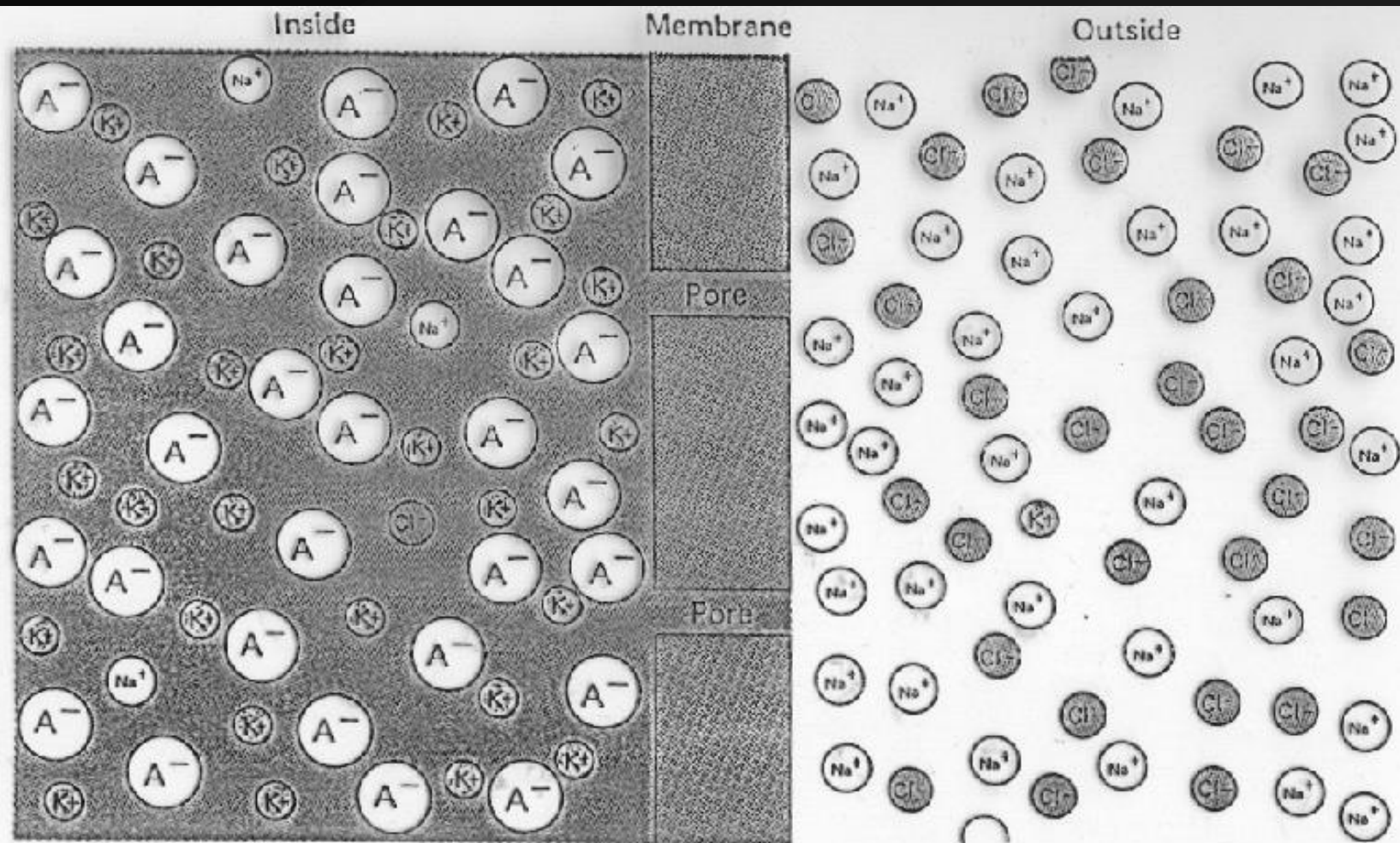



Fig. 2-3. Intra- and extracellular distribution of the ions. On both sides of the membrane, the different ions are indicated by *circles of different diameter*, proportional in each case to the diameter of the (hydrated) ion. A⁻ designates the large intracellular protein anions. The passages through the membrane, the "pores," are just large enough to permit the K⁺ ions to diffuse through.

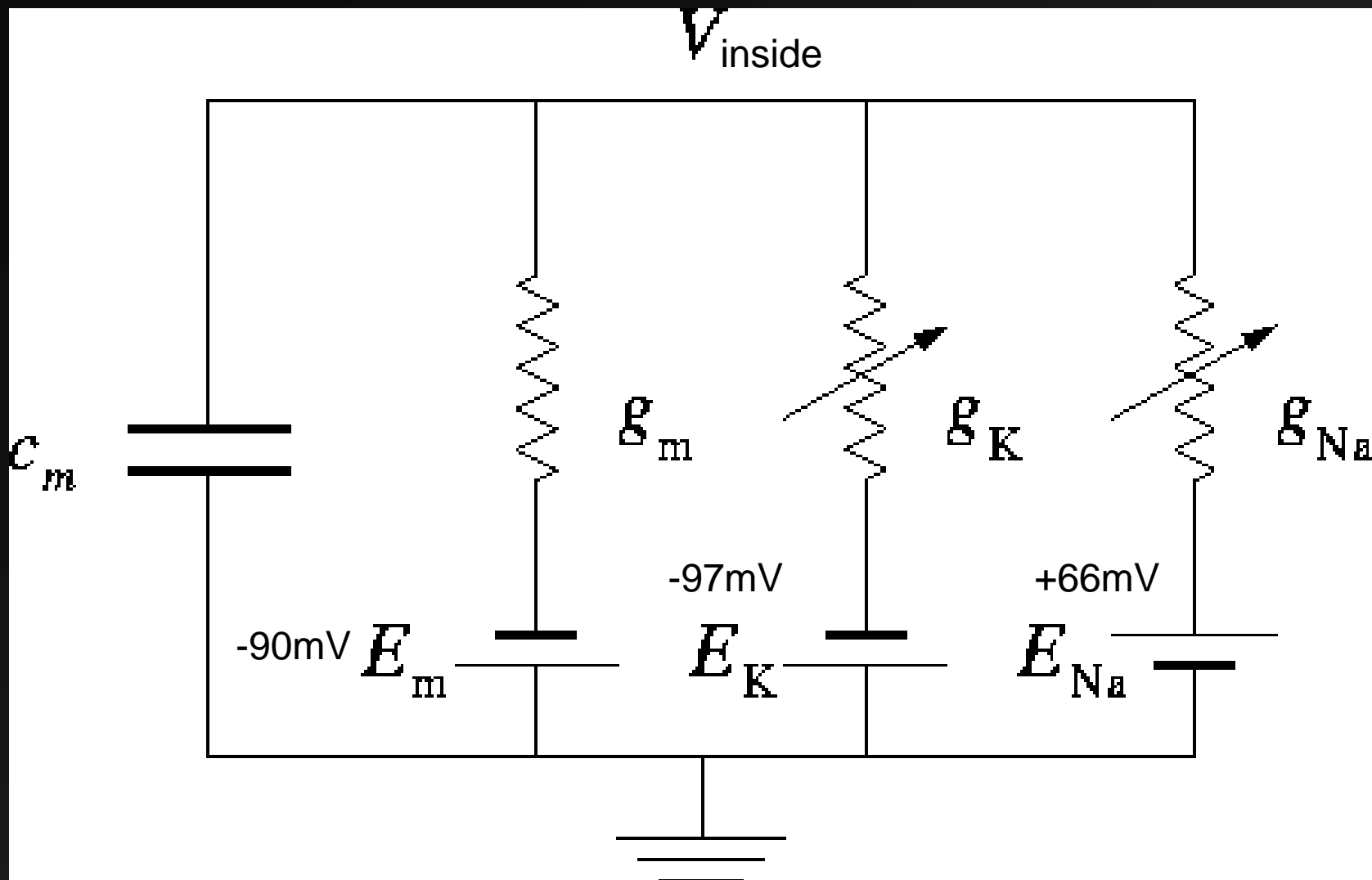

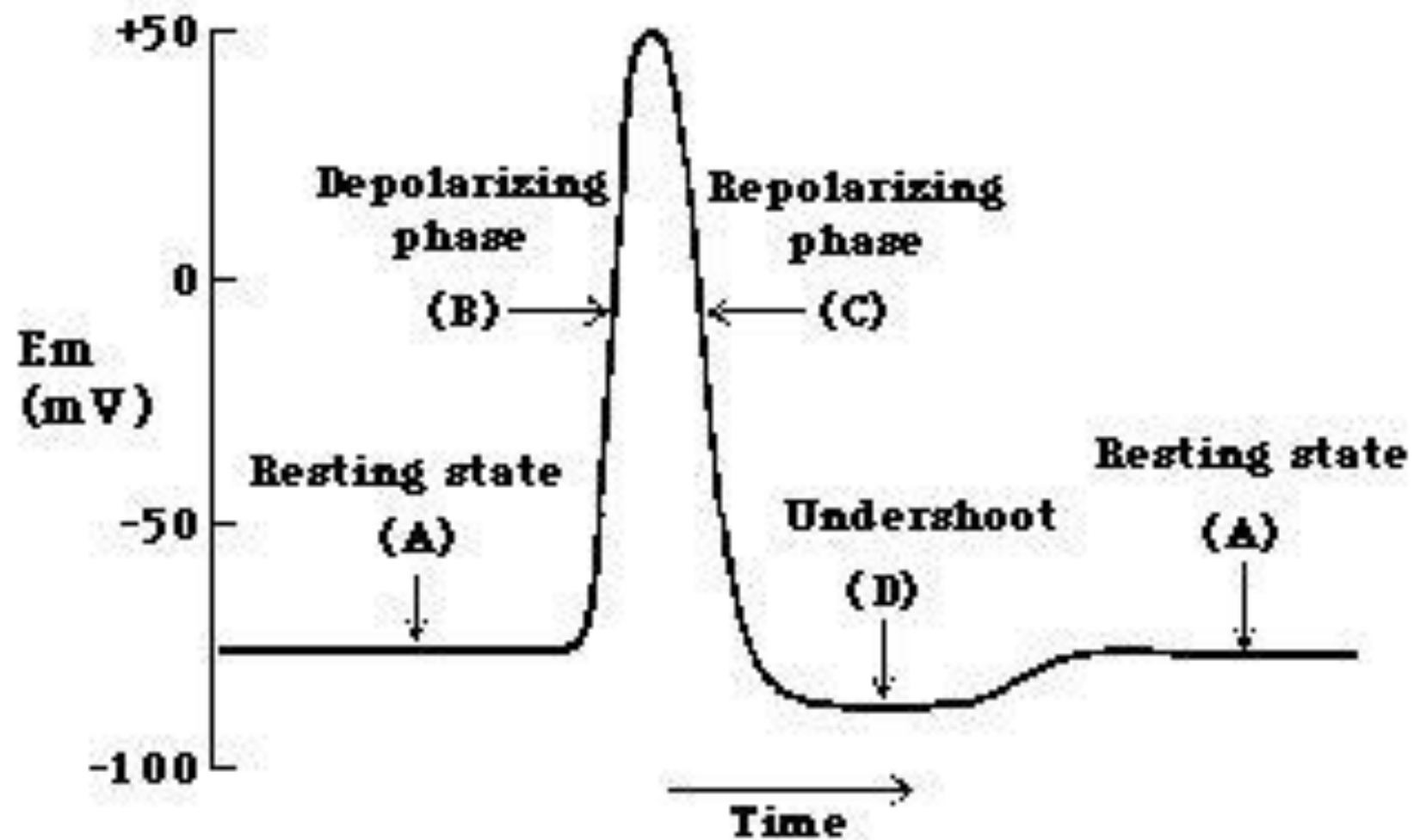For interactive link: <http://ssd1.bme.memphis.edu/icell/squid.htm>



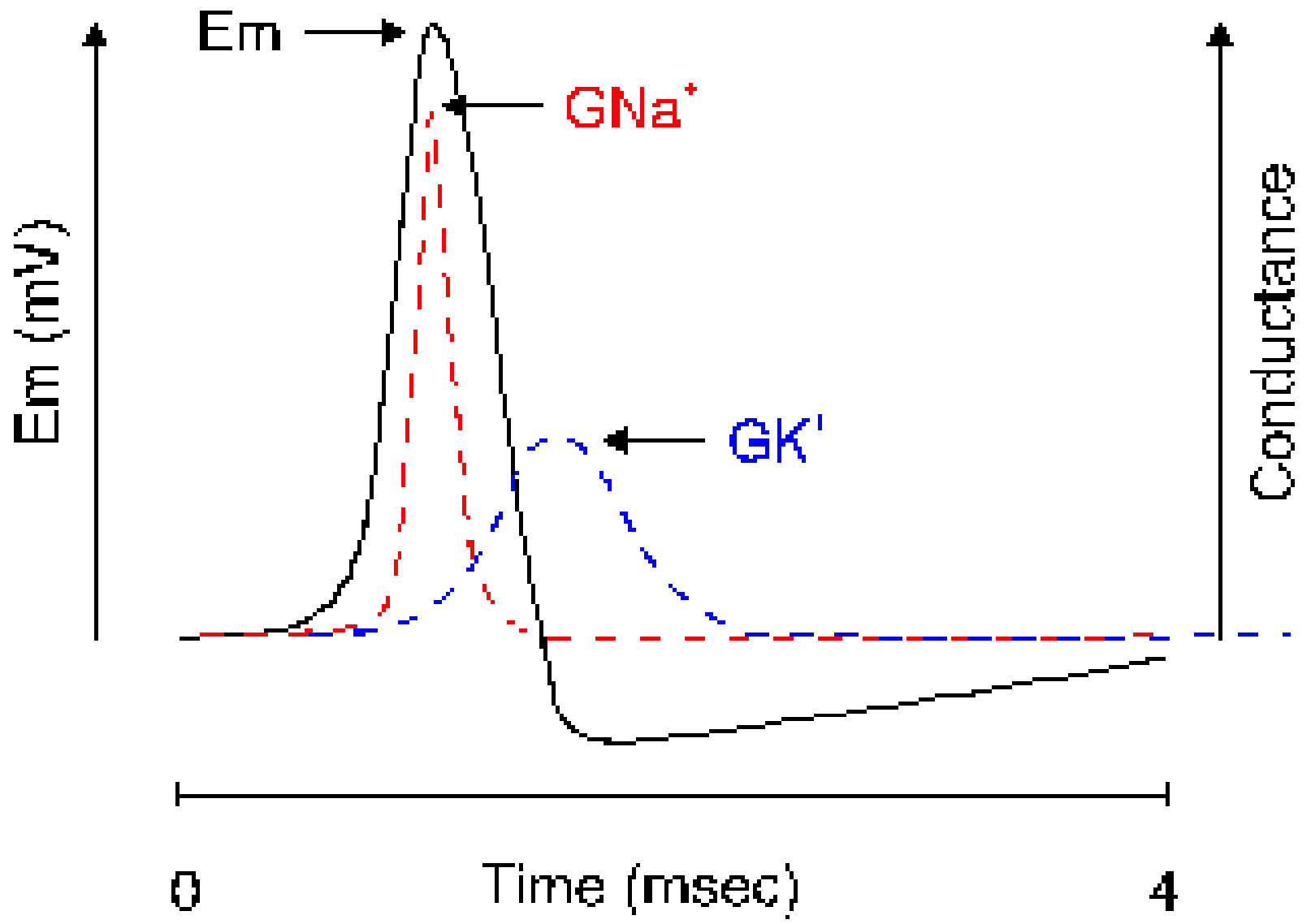


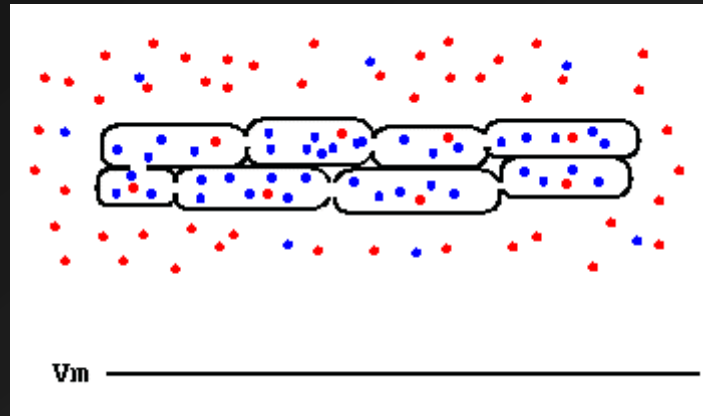

Synaptic Transmission

- Not an all-or-none phenomenon
- Synaptic gap or cleft at the synaptic junction
- Single axon splits near end--**terminal arborization**
- As action potential arrives
 - Synaptic vesicles migrate to cell membrane fuse and release
 - Neurotransmitters diffuse across the synaptic cleft
 - combine with **post-synaptic receptors**
 - When neurotransmitter binds to a receptor on the post-synaptic cell, a slow electrical potential (**post-synaptic potential**) is generated:
 - 5 to 20 mV at peak amplitude
 - 20-150 msec in duration (50 to 6 Hz)

Presynaptic Axon Terminal

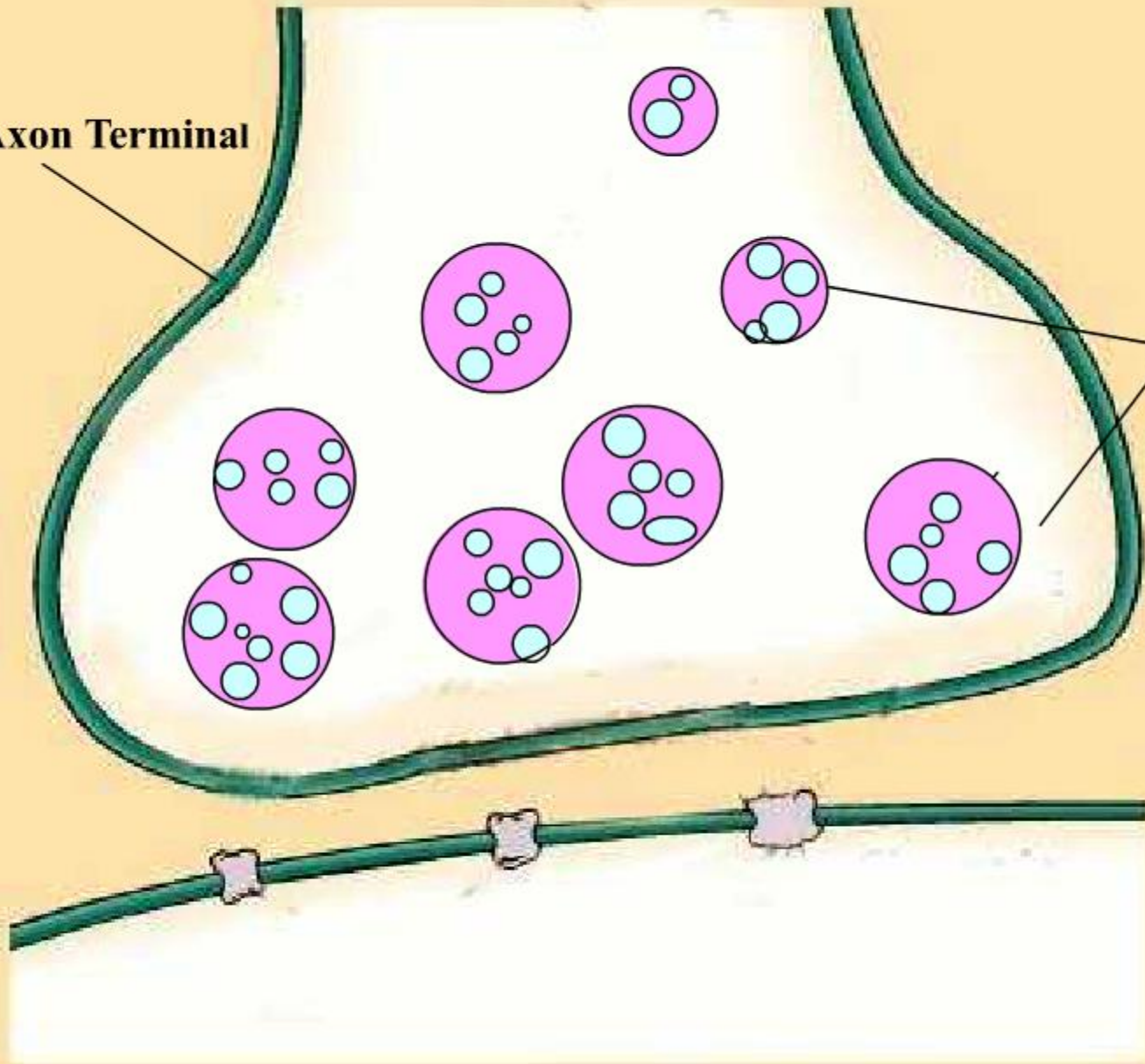

Synaptic Vesicles

Synaptic Transmission


- Post-synaptic potentials (PSP's);
 - Excitatory
 - Inhibitory
 - Interaction
- **Summation/Integration**
 - temporal
 - spatial
 - **decremental conduction** on dendrites and soma
 - axon hillock is critical area at which threshold must be reached
- After release of neurotransmitter,
 - reuptake
 - degradation
- **Functional Synaptic Units**



Synaptic Transmission

1. Within the axons of the neuron are neurotransmitters, which are held in storage-like vesicles until they are released when the neuron is stimulated.

2. The small space between the axon terminal and the dendrite of the next axon is called the synapse. An action potential stimulates the release of neurotransmitters across the synapse.

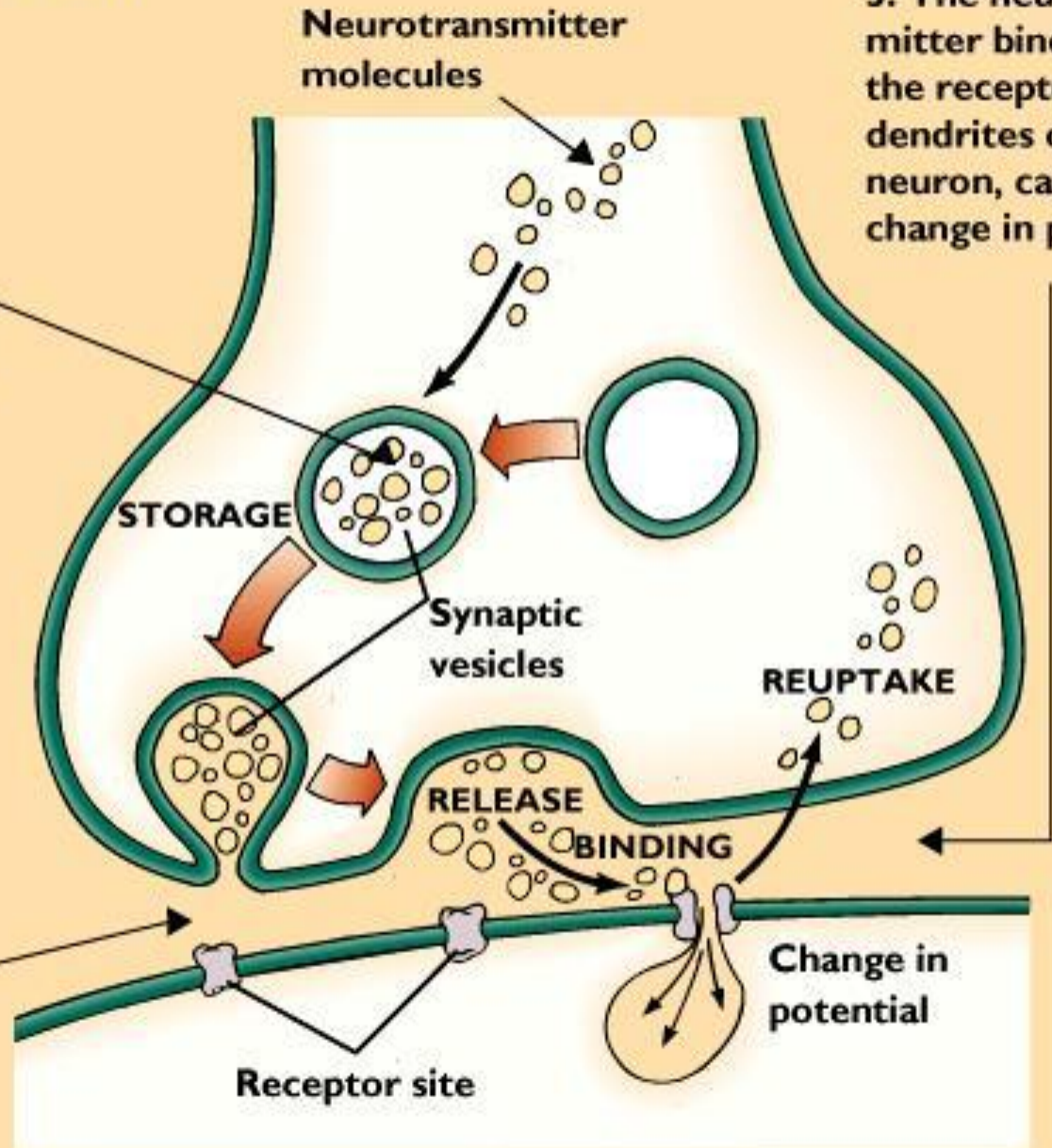3. The neurotransmitter binds itself to the receptor sites on dendrites of the next neuron, causing a change in potential.



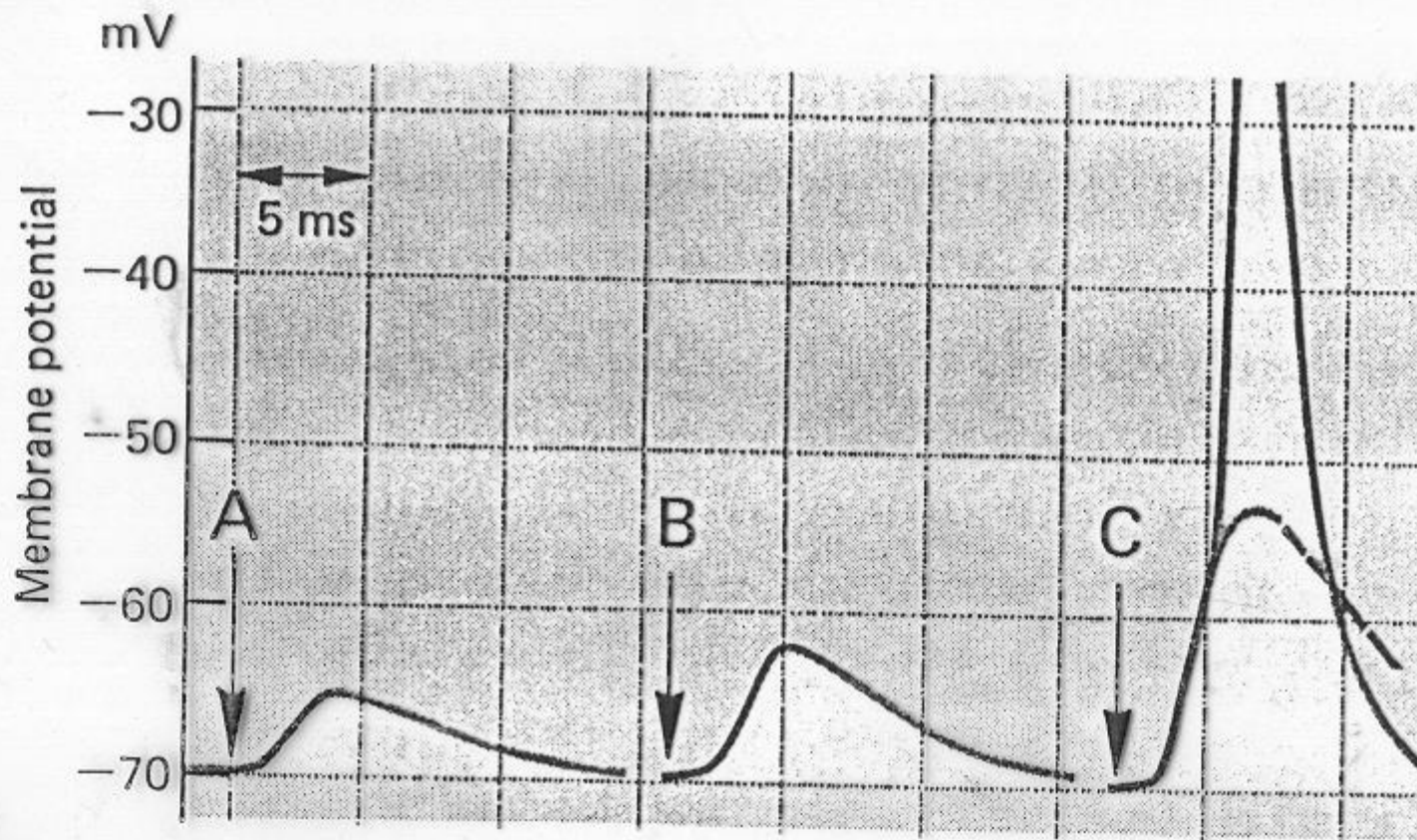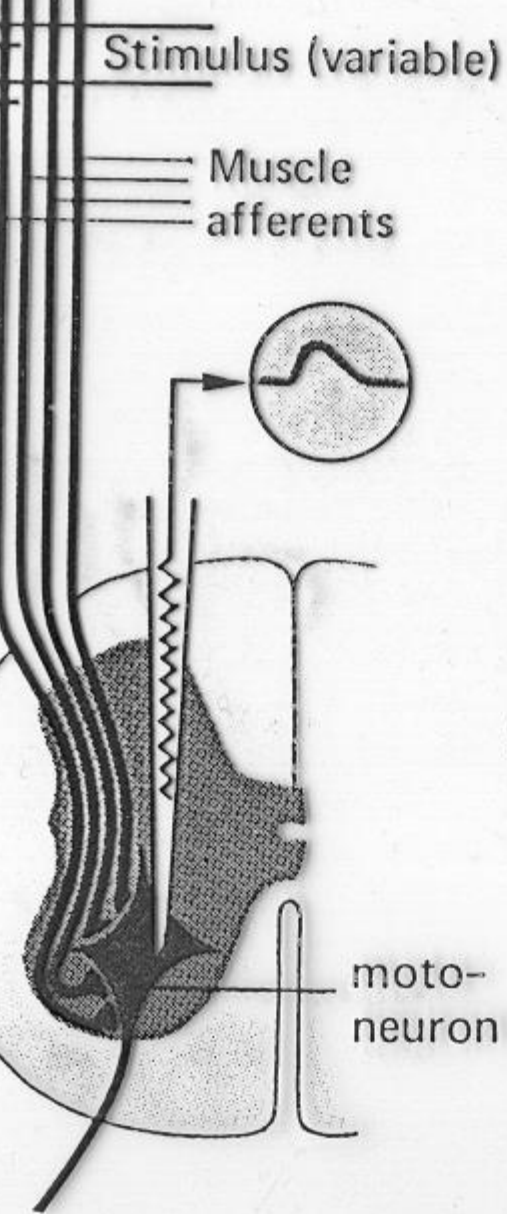

3-10. Excitatory postsynaptic potentials, recorded intracellularly from a moto-neuron. When muscle afferents in the peripheral nerve from the associated muscle are stimulated electrically, the membrane potential of the moto-neuron is depolarized. The depolarization is the EPSP. The EPSP is followed by an action potential (AP) if the EPSP is large enough to reach the threshold for AP initiation.

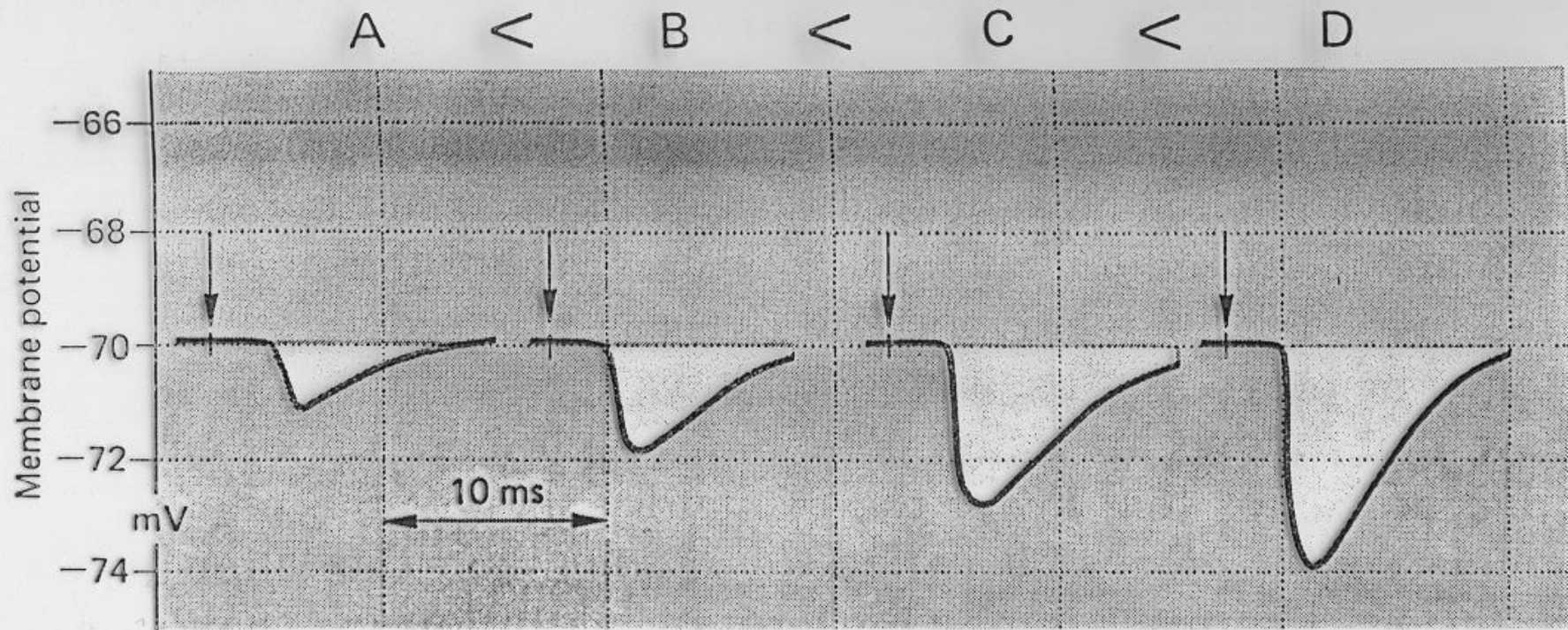


Fig. 3-11. Inhibitory postsynaptic potentials. Experimental arrangement as in Fig. 3-10, except that here an antagonist nerve is stimulated.



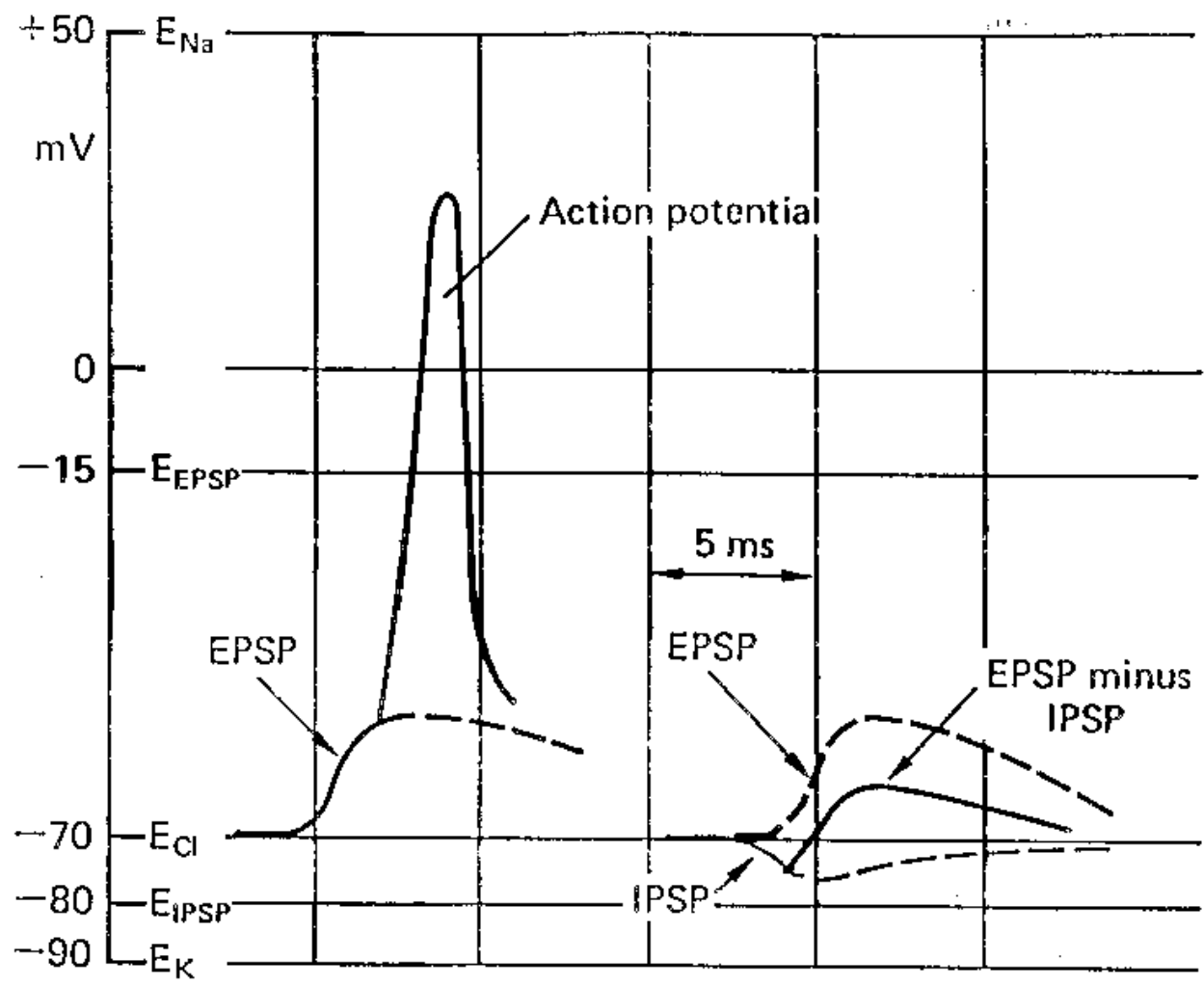


Fig. 3-14. The effect of an IPSP on the action potential; experimental arrangement as in Fig. 3-13. The homonymous nerve is stimulated strongly enough to produce a supra-threshold EPSP (left). On the right, the antagonist nerve is stimulated about 3 ms before the homonymous nerve. The equilibrium potentials of Na^+ , K^+ , Cl^- , EPSP, and IPSP are shown.


Spatial Summation. Figure 5.11

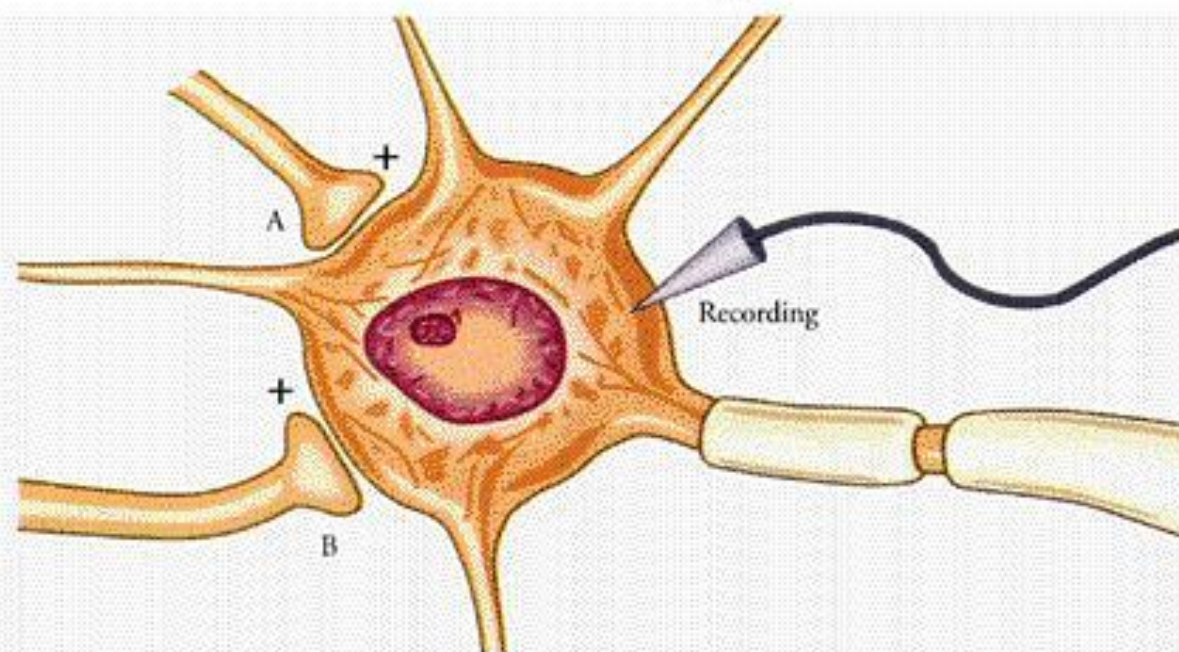


Spatial summation

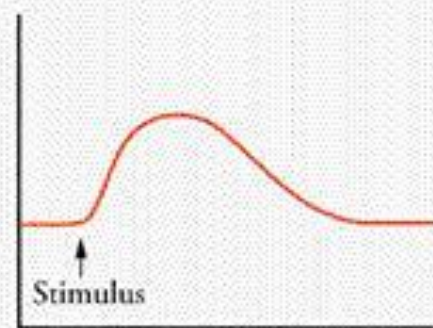

A only

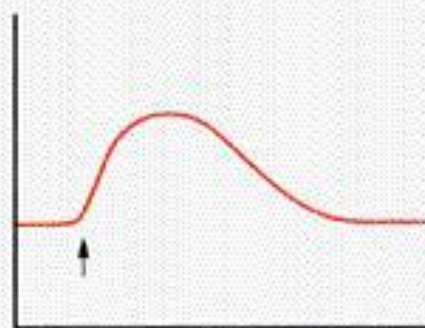

B only

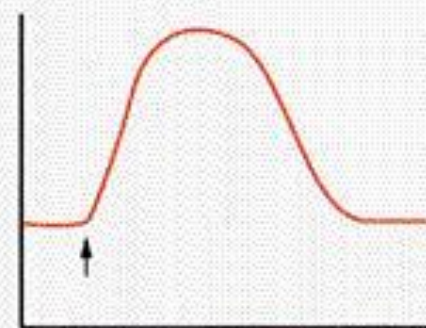

A + B

Temporal Summation. Figure 5.11

